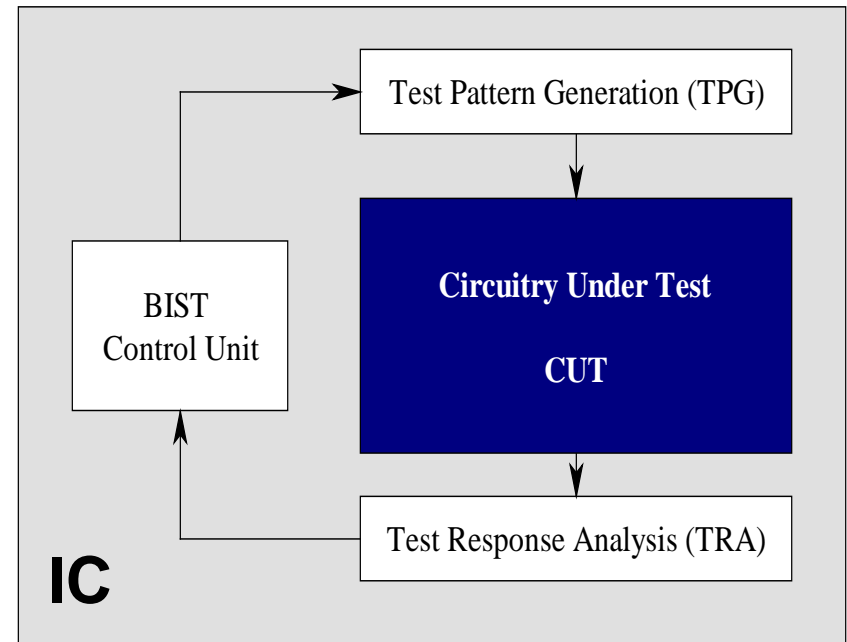


Course Work. Design of a Circuit with BIST


- **Design of a given circuit**
- **Evaluation of the testability of the circuit**
- **Redesign for testability**
 - **Control points selection, optimization**
 - **Scan path, optimization**
- **Design of BIST solutions for the given circuit**
- **Experimental research**

Course Work. Introduction to BIST

- **In-circuit**
 - Test pattern generation
 - Response verification
- **Pseudorandom test generation**
(very long tests)
- **Hybrid test solutions**
- **Response compression**



Course Work. Description of the Circuit

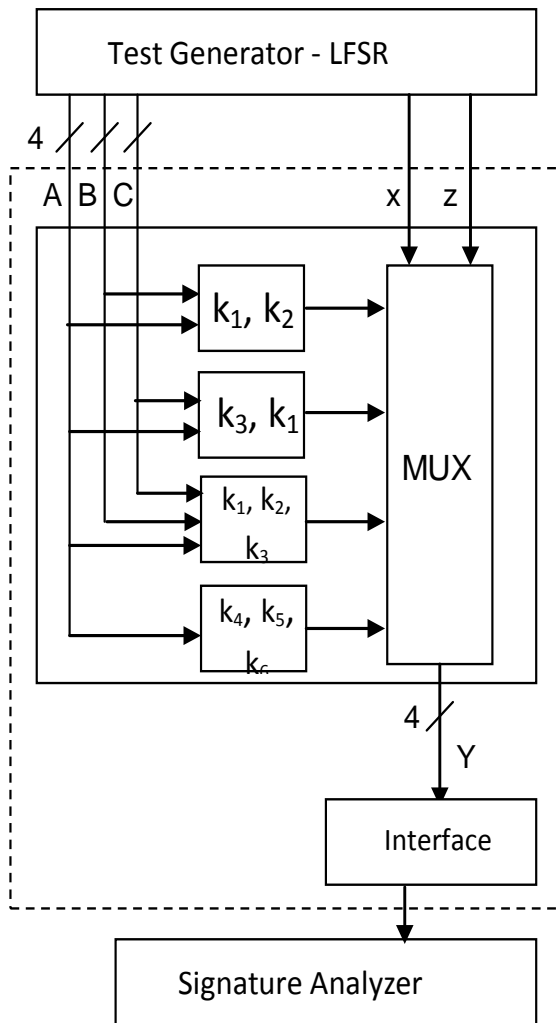

1. Design of a combinational circuit for the following functionality

If $x = 0, z = 0$, then $Y = k_1A + k_2B$, else

if $x = 0, z = 1$, then $Y = k_3A - k_1C$, else

if $x = 1, z = 0$, then

$$Y = (k_1A \vee k_1B \wedge k_2C) \oplus (k_3C \vee \text{NOT}(k_3A) \wedge k_1B),$$

if $x = 1, z = 1$, then $Y = k_4A^2 + k_5A + k_6$


Coefficients k_i can be found on the next slide

Coefficients for the Course Work Versions


Vers. No.	k ₁	k ₂	k ₃	k ₄	k ₅	k ₆	Vers no.	k ₁	k ₂	k ₃	k ₄	k ₅	k ₆
1	1	1	1	0,1	0,2	0,5	8	1	1	1	1,5	0,1	0,5
2	1	1	0	0,1	0,2	1,0	9	1	1	0	1,5	0,1	1,0
3	1	0	1	0,1	0,2	2,0	10	1	0	1	1,5	0,4	2,0
4	1	0	0	0,1	0,2	3,0	11	1	0	0	1,5	0,4	3,0
5	0	1	1	0,1	1,0	0,5	12	0	1	1	1,5	0,8	0,5
6	0	1	0	0,1	1,0	1,0	13	0	1	0	1,5	0,8	1,0
7	0	0	1	0,1	2,0	2,0	14	0	0	1	1,5	1,5	2,0

Course Work. Design of Interface Versions

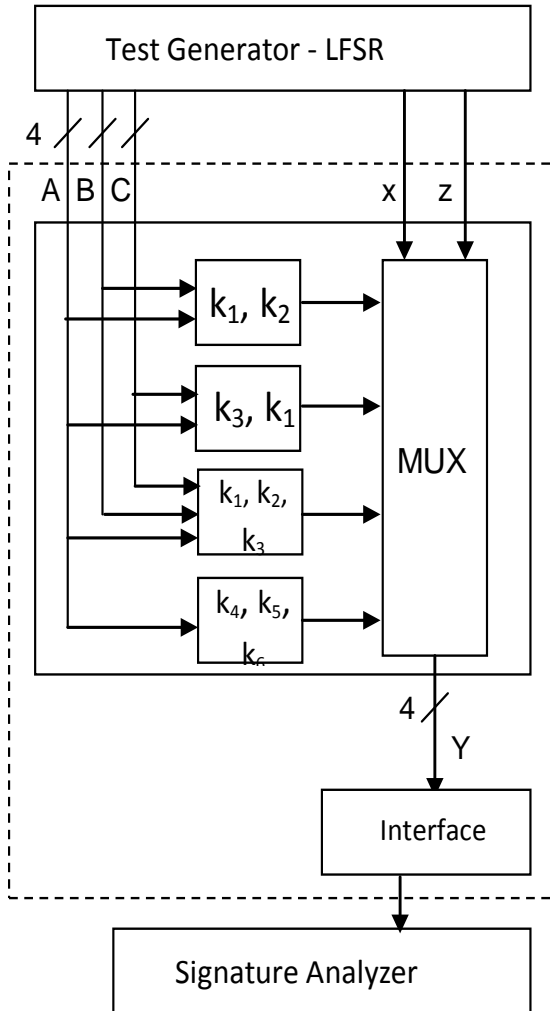2. Use three different interface versions for experiments: 1 bit, 2-bit and 4- or more bit interfaces for respective n-bit Signature Analyzers




The types of interface:

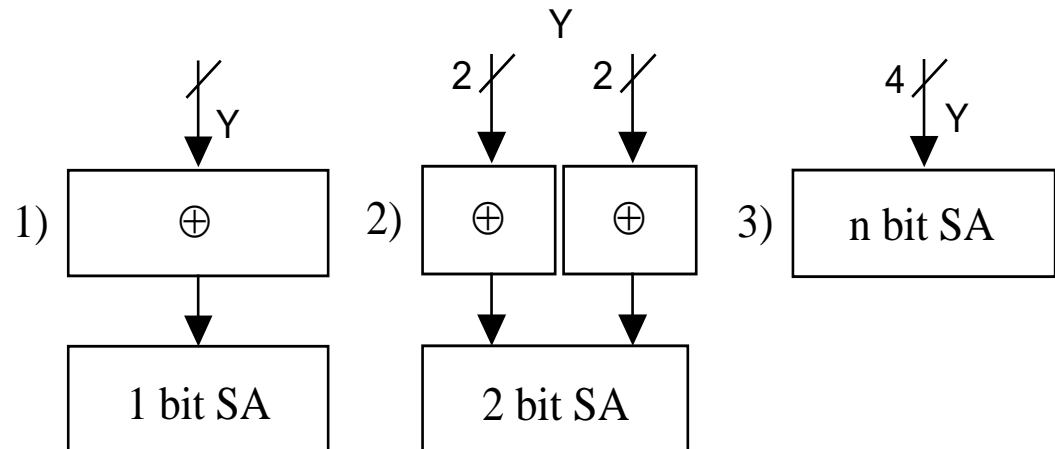

Course Work. Design of a Testable Circuit

 3. Enter the designed gate-level (AND, OR, NOT combinational circuit into the computer with CADENCE circuit editor
4. Generate test patterns with Turbo-Tester (TT) ATPG. If the fault coverage is 100%, remove one or more patterns from the test set, so that at least two faults remain undetected
5. **Improve the testability of the circuit** to reach again 100% fault coverage with the updated test set




1- controllability:
CP = 0 - normal working mode
CP = 1 - controlling Block 2
with signal 1

Course Work. Observability Investigation

 6. Analyze two different testability improvement solutions:

- Separate pins for all observability points
- Single joint pin for all observability points

Draw the graphics for both cases for the function $P = f(T)$ where P is fault coverage, and T is test length



Course Work. Design of a Test Generator

**BILBO - Built- In Logic
Block Observer:**

LFSR - Test Pattern Generator

Combinational circuit

LFSR - Signature analyzer


7. **Generate test patterns by the BILBO tool for 10 different **polynomials**, and find the best structure for the LFSR**

Report for all 10 experiments the maximum achievable fault coverage, and fix the minimum test length needed for that

Calculate the increase of the circuit size (in number of 2-input gates) due to adding of the self-test circuitry



Course Work. Design of a Test Generator

CSTP - Circular Self-Test Path:

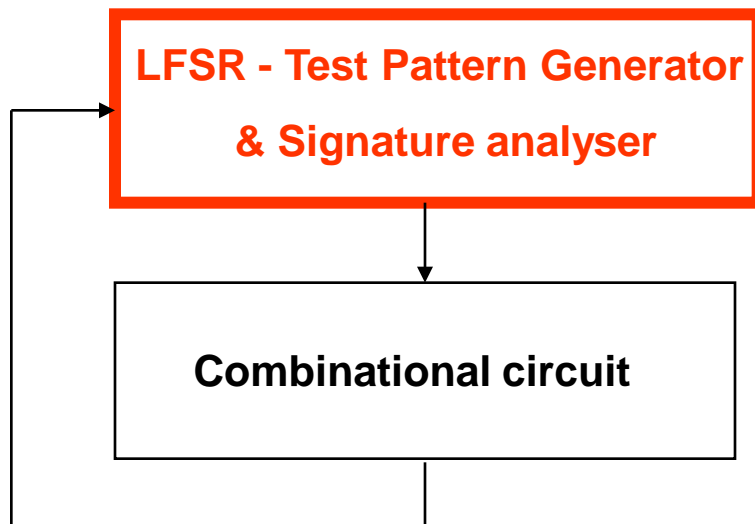

 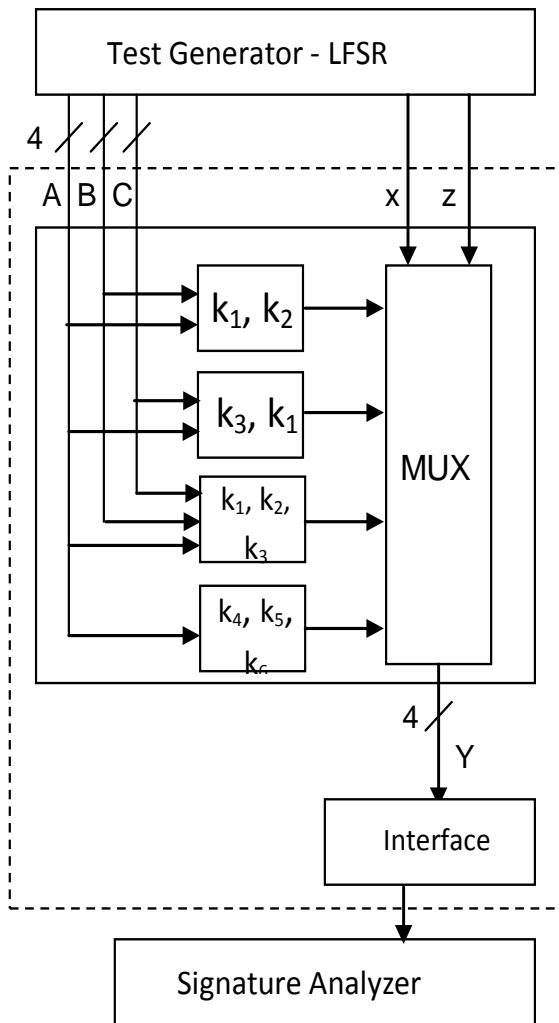8. Repeat the previous task for the case of using CSTP ("Circular Self Test Path") for self-test purposes

Course Work. Design of a Signature Analyzer



9. Carry out experiments with the best test set found in task 7 for 4 different Signature Analyzers: 1-bit, 2-bit, 4-bit, and 8-bit

Calculate the fault coverages


Draw the graphic $P = f(\text{SA})$, where P is the fault coverage, and SA – is the number of bits in the Signature Analyzer

Draw 4 graphics $P = f(T)$, for 4 SA cases, where T – is the test length 5, 10, 15, 20 etc. up to $P = 100\%$
Explain the graphics

Course Work. Store-and-Generate BIST

The main motivations to use random patterns:

 
- low generation cost
- high initial efficiency



Problem: **low fault coverage**


Long PR test:

Pseudorandom test:

 


Using many seeds:

Pseudorandom test:

 

Course Work. Store-and-Generate BIST

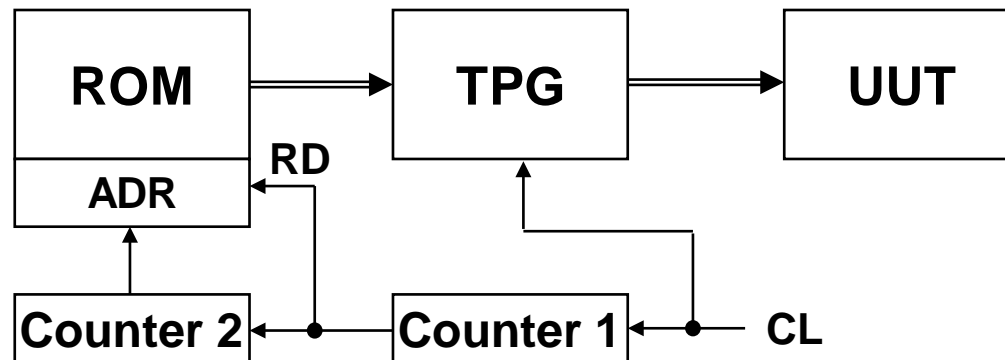10. Synthesize an optimal BIST, using "store & generate" architecture. Choose for that the best BILBO structure and do the 100% test with length N. Minimize the number of seeds to be stored in the memory



11. Compare the results in tasks 4, 5, 7, 8 and 10. Which solution is the best and why? Draw the block-level final structure of the selected best BIST solution.
12. Present a report of the course work.