


# ELECTRONICS

## Practical work 1

### BIPOLAR TRANSISTOR AMPLIFIERS

#### 1. Study of bipolar transistor amplifiers.

1.1. Compose the CE amplifier as in Fig. 1.

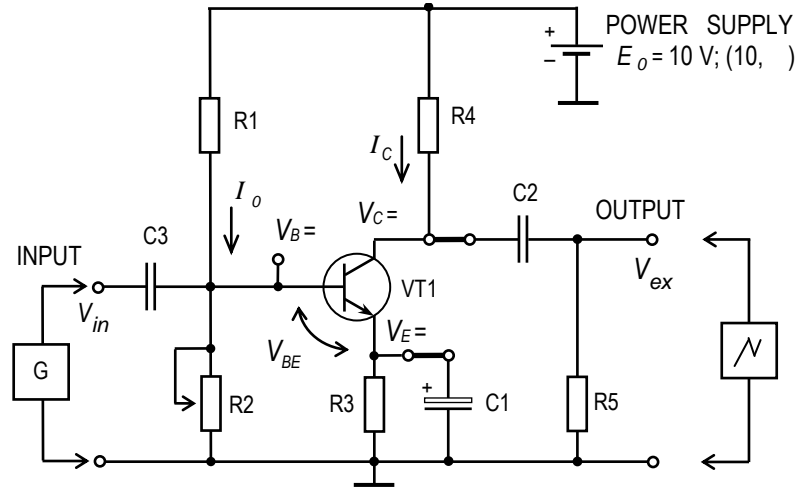

**Fig. 1 Diagram of the CE transistor amplifier.**

Connect the function generator at  $f = 400$  Hz and adjust the level of the sine wave input for a maximum undistorted signal at the output.

Measure the following voltages:

- $V_C =$  [V];
- $V_B =$  [V];
- $V_E =$  [V];

Calculate: current through resistor R1:  $I_0 = \dots\dots\dots = \dots\dots\dots = \dots\dots[\mu A]$  ;  
 collector current of transistor:  $I_C = \dots\dots\dots = \dots\dots\dots = \dots\dots[mA]$  ;  
 voltage drop  $V_{BE} = \dots\dots\dots = \dots\dots\dots = \dots\dots\dots[V]$  ;

1.2. Take the relationship  $V_{ex\ m} = f(V_{in\ m})$  for amplifier by voltmeter and write the results into the Table 1 and Fig. 2.

Find the voltage gain  $A_v$  for the circuit from Table 1:

$$A_v = \frac{V_{ex}}{V_{in}} = \dots\dots\dots = \dots\dots\dots ;$$

Calculate theoretical voltage gain  $A_{v\ th}$  for the circuit:

$$A_{v\ th} = - \frac{h_{21}}{h_{11}} \cdot R_4 \parallel R_5 = \dots\dots\dots = \dots\dots\dots ,$$

where:  $h_{21}$  is the current gain for transistor in common emitter (CE) configuration (a value between 30 and 200; use in the following calculations  $h_{21} = 100$ );

$h_{11}$  is the input impedance for transistor in CE configuration and calculates as

$$h_{11} = V_T / I_B = V_T h_{21} / I_E = \quad = \quad [\Omega],$$

where emitter current  $I_E = \quad = \quad = \quad$  [mA].

and  $V_T$  is the thermal voltage:  $V_T = \quad$  [mV].

Table 1

$V_{in}$ [V]	$V_{ex}$ [V]	$V_{in} \sqrt{2}$ [V]	$V_{ex} \sqrt{2}$ [V]	$A_v = \frac{V_{ex} \cdot \sqrt{2}}{V_{in} \cdot \sqrt{2}}$

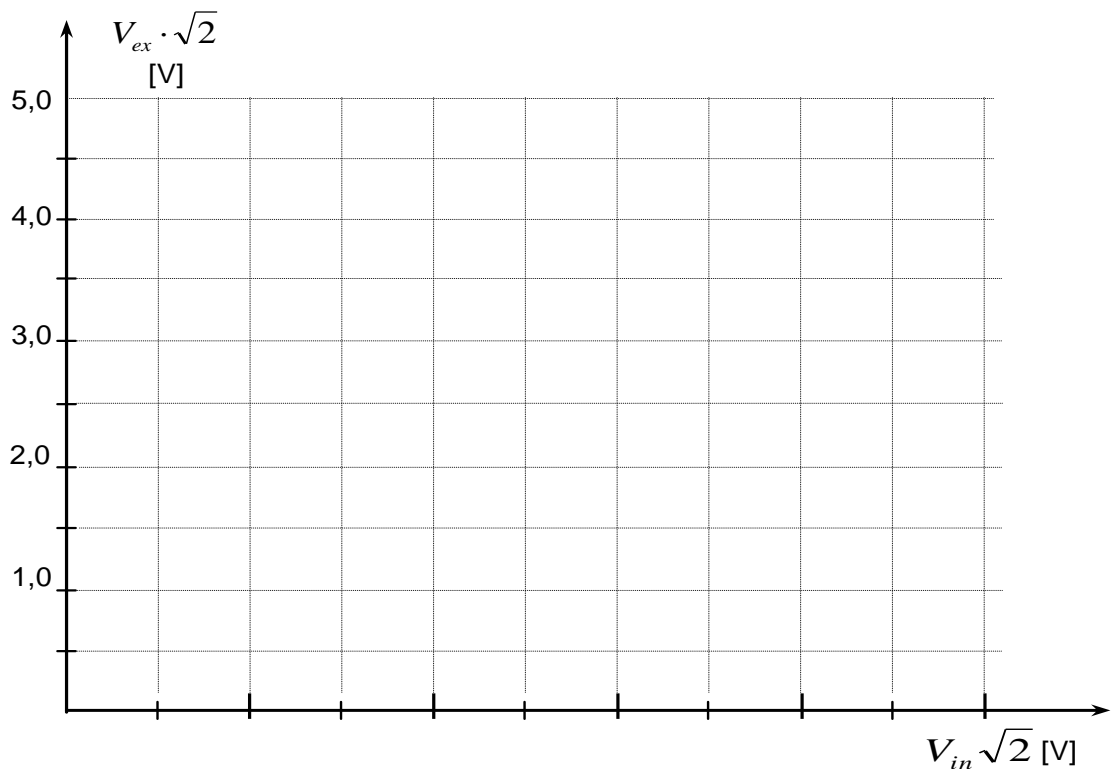


Fig. 2 Transfer relationship  $V_{ex m} = f ( V_{in m} )$  for CE amplifier.

1.3. Find the logarithmic gain - frequency response.

For it calculate:

- voltage gain  $A_o$  for passband frequencies (e.g. at 400 Hz)

$$A_o = 20 \lg V_{ex m} / V_{in m} = 20 \lg \dots\dots\dots / \dots\dots\dots = \dots\dots\dots [\text{dB}], \text{ and}$$

- lower cutoff frequency (by multimeter) :  $f_b = \dots\dots\dots [\text{Hz}]; \lg f_b = \dots\dots\dots [\text{Hz}];$


- upper cutoff frequency (by oscilloscope):  $f_h = \dots\dots\dots [\text{kHz}]; \lg f_h = \dots\dots\dots [\text{kHz}];$  where:  $f_b$  and  $f_h$  are - 3 dB frequencies for amplifier.

Write the results into the Table 2 and use for Fig. 3.

Construct the straight-line approximation and corrected smooth curve for logarithmic gain - frequency relationship.

Table 2

$f [\text{Hz}]$	$V_{in} [\text{dB}]$	$V_{ex} [\text{dB}]$	$A_v [\text{dB}] = V_{ex} [\text{dB}] - V_{in} [\text{dB}]$
$f_b =$			
400			$A_o [\text{dB}] =$
$f_h =$			

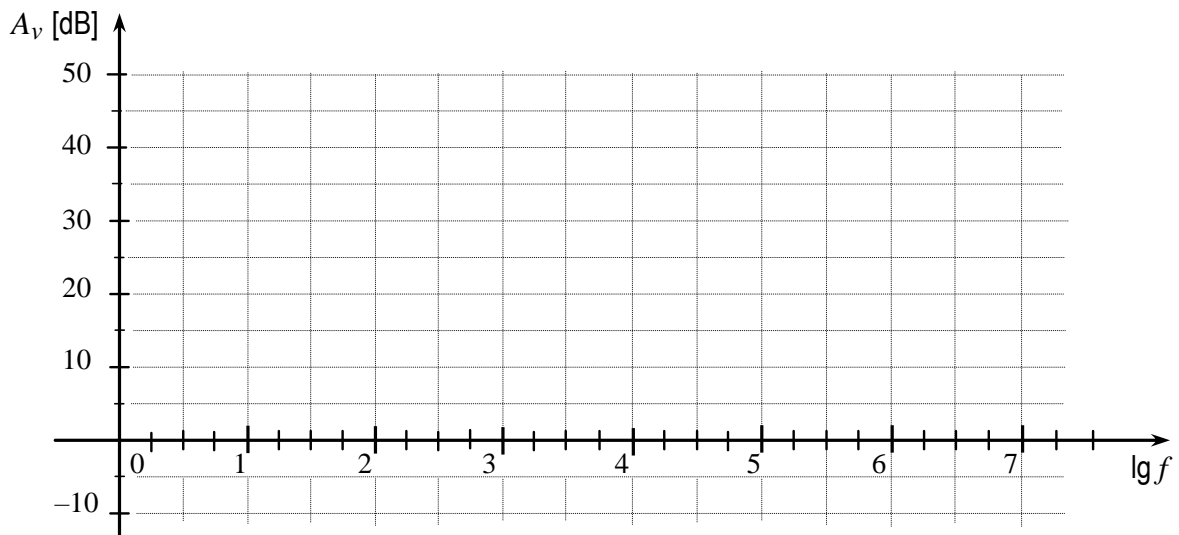

**Fig. 3 Logarithmic gain - frequency relationship for CE amplifier.**

The horizontal axis is scaled logarithmically, in decades of frequency;  
the dB gain is assigned to the vertical axis.

Explain the reasons for the frequency distortions of CE amplifier:

.....

.....

.....

.....


.....

1.4. Assume, you apply the incoming square-wave signal  $v_{IN}$  for frequency  $f_I = 400$  Hz. Draw the output voltage  $v_{EX}$  curves in Fig. 4. Determine the phase shift  $\varphi$  for input and output voltages and explain it:

$\varphi = \dots\dots\dots^\circ$ ; .....

Explain the reasons for the output voltage distortion: .....

.....

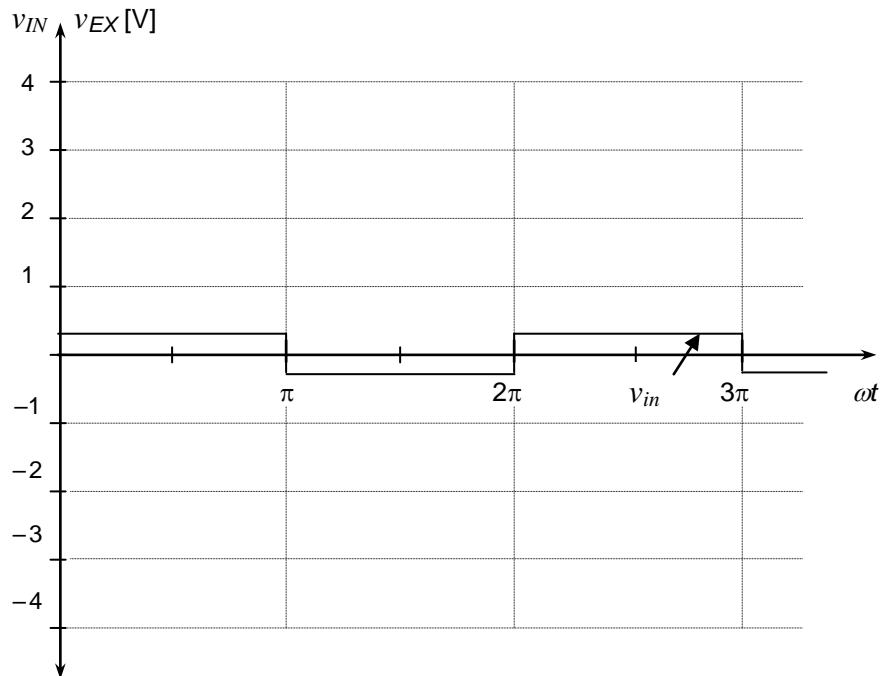

**Fig. 4** Input voltage  $v_{IN}$  and output voltage  $v_{EX}$  curves.

1.5. Design the CE amplifier configuration without emitter capacitor and determine the voltage gain  $A_v$  for 400 Hz sine wave input:

$$A_v = \frac{V_{ex}}{V_{in}} = \dots\dots\dots = \dots\dots\dots ;$$

Compare the result with the theoretical gain value  $A_{v th}$ :

$$A_{v th} \approx \frac{R_4 \parallel R_5}{R_3} \approx \dots\dots\dots \approx \dots\dots\dots ;$$

1.6. Design the common collector (CC) configuration amplifier (emitter follower). The CC amplifier diagram is shown in Fig. 5.

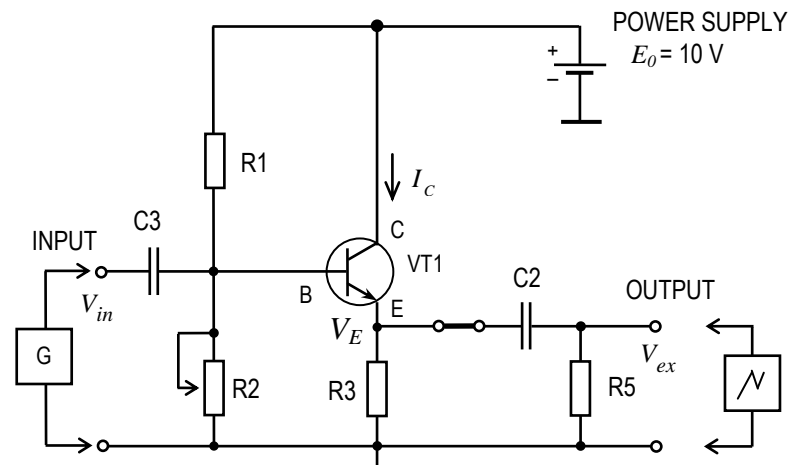


Fig. 5 Diagram of the CC amplifier ( emitter follower ).

Apply the 400 Hz sine wave input.

Adjust by input signal the maximum undistorted output signal.

Find the voltage gain for CC amplifier:

$$A_v = \frac{V_{ex}}{V_{in}} = \frac{\quad}{\quad} = \quad ;$$

Measure the DC voltage:

$V_E = \dots\dots\dots[V]$  ;

Calculate the following DC currents:

$I_E = \dots\dots\dots = \dots\dots\dots = \dots\dots [mA]$  ;

$I_C = \dots\dots\dots = \dots\dots\dots = \dots\dots [mA]$  .

Determine the phase shift  $\phi$  for the input and output voltages and explain it:

$\phi = \quad^\circ, \dots\dots\dots$

Conclusions:.....  
 .....  
 .....  
 .....  
 .....  
 .....  
 .....