



MICROPROCESSOR SYSTEMS (IAS0430)

Department of Computer Systems
Tallinn University of Technology

10.12.2021

COMPUTER ARITHMETIC

▪ Operations on Binary

▪ Addition:

- Addition is a simple operation to perform on integers.
- The binary addition table is

- $0 + 0 = 0$
- $0 + 1 = 1$
- $1 + 0 = 1$
- $1 + 1 = 0$ and 1 as carry out

- Simply put, adding a 1 to 1 is in fact 2 in binary
 - 2_{10} is 10_2 in binary
 - Which means that one bit value of 1 is carried to the next power of 2 magnitude
- Addition is a very simple operation that can be performed using a full adder

+	0	1
0	0	1
1	1	0/1 c

COMPUTER ARITHMETIC

▪ Operations on Binary

▪ Subtraction

- Subtraction is a simple operation to perform on integers.
- The binary subtraction table

- $0 - 0 = 0$
- $1 - 0 = 1$
- $1 - 1 = 0$
- $0 - 1 = 1$ and 1 as borrow

- Simply put, subtracting a 1 from 0 is not possible, so we use the value found in the higher magnitude to raise the value of the 0 to 10.
- Subtraction can be done using 2 methods:
 - Direct subtraction if the minuend is larger than the subtrahend
 - Or using addition $\rightarrow (4 - 10)$ is equivalent to $(4 + (-10))$
- No need to build a subtractor if you can build a Positive to Negative and an adder.

-	0	1
0	0	1
1	1/1 b	0

COMPUTER ARITHMETIC

- **Addition – Example**

$$\begin{array}{r} & 0011000. \quad \text{carry} \\ \begin{array}{r} 13 \\ + 24 \\ \hline 37 \end{array} & \begin{array}{r} 00001101 \\ + 00011000 \\ \hline 00100101 \end{array} \quad \text{result} \end{array}$$

- **Subtraction – Examples**

$$\begin{array}{r} & 1110000. \quad \text{borrow} \\ \begin{array}{r} 13 \\ - 24 \\ \hline -11 \end{array} & \begin{array}{r} 00001101 \\ - 00011000 \\ \hline 11110101 \end{array} \quad \text{result} \\ & [A - B] \end{array}$$



$$\begin{array}{r} & & & 1 \\ & 00001101 & 00001101 & 00001101 \\ & + 11101000 & + 11100111 & + 11110101 \\ \hline & 11110101 & [A + -B] & [A + (\sim B) + 1] \end{array}$$

COMPUTER ARITHMETIC IN HARDWARE

- Adding & Subtracting

$$O = A - B = A + (\sim B) + 1$$


$$O = n ? (A - B) : (A + B)$$

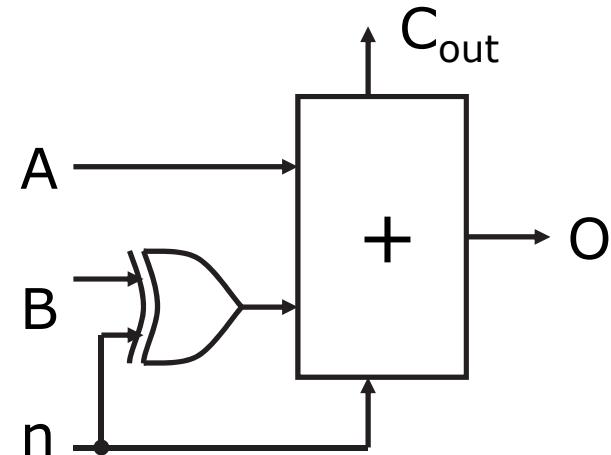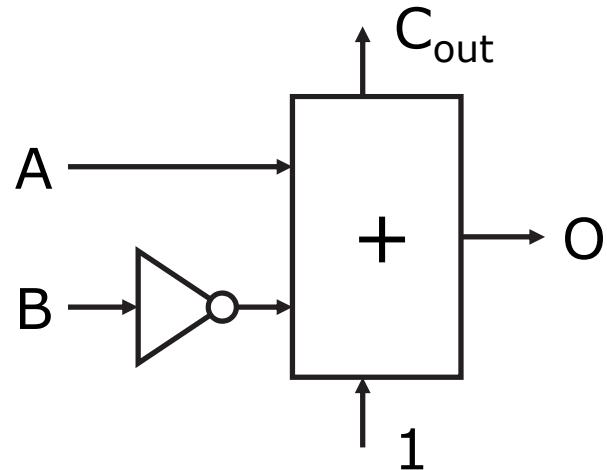

COMPUTER ARITHMETIC IN HARDWARE

▪ Half adder

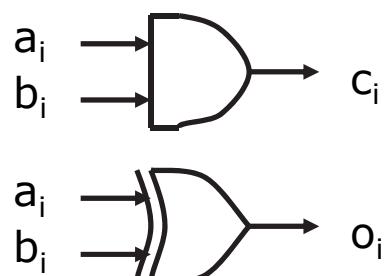
- $(c_i, o_i) = a_i + b_i$
- $o_i = a_i \oplus b_i ; c_i = a_i \cdot b_i$



a + b		c	o
0 + 0		0	0
0 + 1		0	1
1 + 0		0	1
1 + 1		1	0

▪ Full adder == two half adders

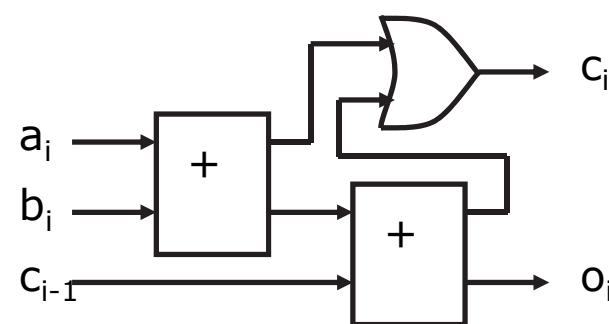- $(c_i, o_i) = a_i + b_i + c_{i-1}$
- $o_i = a_i \oplus b_i \oplus c_{i-1} ; c_i = a_i \cdot b_i + a_i \cdot c_{i-1} + b_i \cdot c_{i-1}$




a + b + c		c	o
0 + 0 + 0		0	0
0 + 0 + 1		0	1
0 + 1 + 0		0	1
0 + 1 + 1		1	0
1 + 0 + 0		0	1
1 + 0 + 1		1	0
1 + 1 + 0		1	0
1 + 1 + 1		1	1

COMPUTER ARITHMETIC IN HARDWARE

- Adders




- Ripple-carry adder

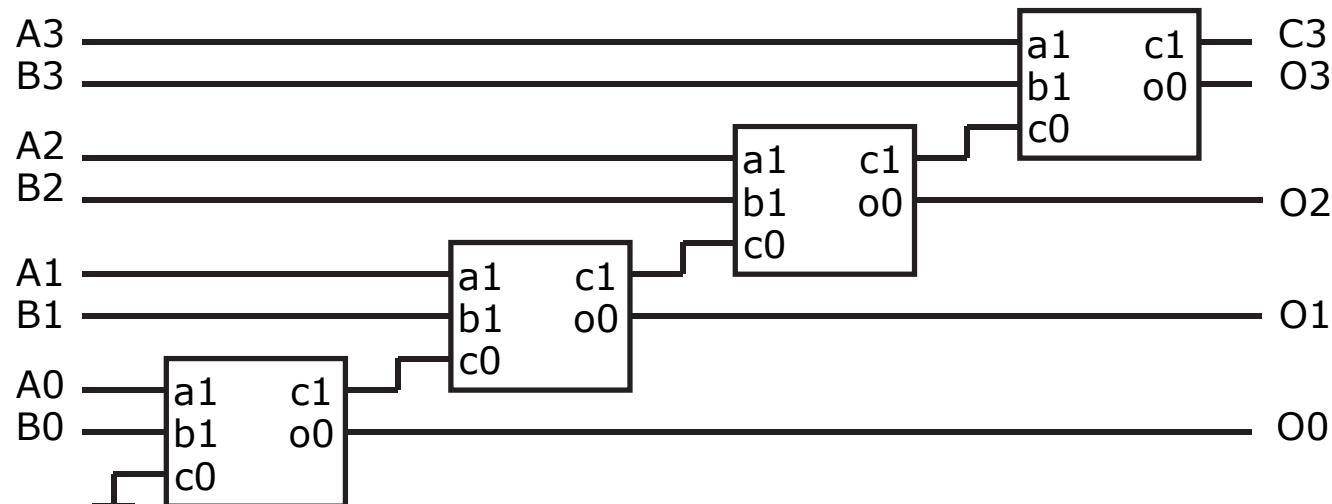- The carry bits are propagated through the adder by connecting the carry out bit from a full adder to the carry in to the next full adder.
 - The carry propagation is slow



COMPUTER ARITHMETIC IN HARDWARE

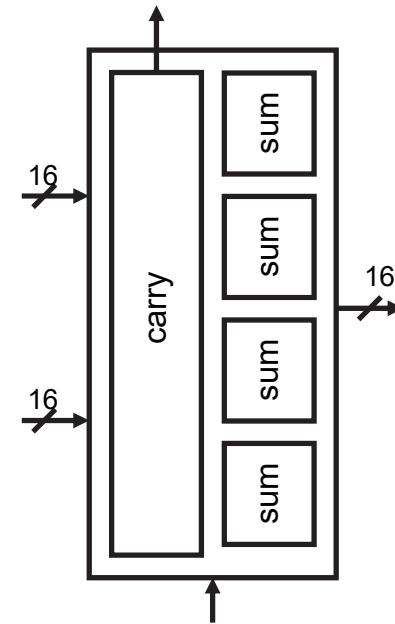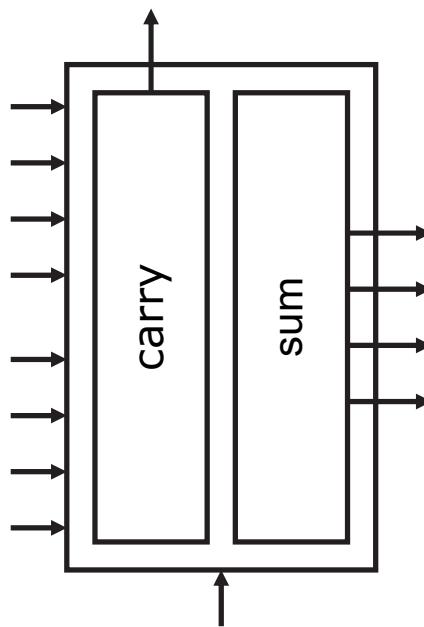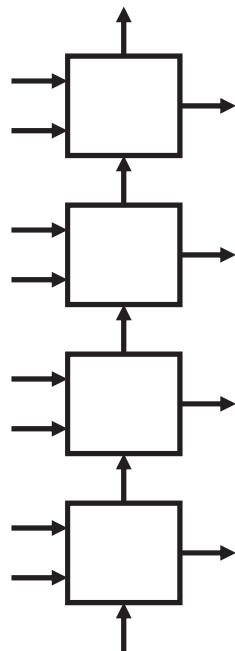- Adders
 - Making carry propagation faster?




COMPUTER ARITHMETIC

▪ Adders

▪ Carry Look-ahead Adder

- This adder type performs calculation of the carry bit. The Propagate (P) and the Generate (G) bits are used explicitly to generate each of the carry out of the adder.
- Each carry out from any adder requires knowledge of the **P** and **G** values.
 - If a carry is **propagated (P)** = 1 and **Carry in** = 1 then Carry out must be 1
 - **OR** if a carry is **generated (G)** then **Carry out must be 1**
- This can be all performed in one cycle if **P** and **G** are generated for all the adders.
- This will give us:
 - Carry in of 0th adder (C_0) will be the value of Carry in (C_i) to the 0th adder
 - $C_0 = C_i$
 - Carry in of 1st adder (C_1) will be 1 **if** 0th adder generated a Carry (G_0) **OR** (0th adder propagated a P_0 a carry and its C_0 was 1
 - $C_1 = G_0 + P_0 \cdot C_i$

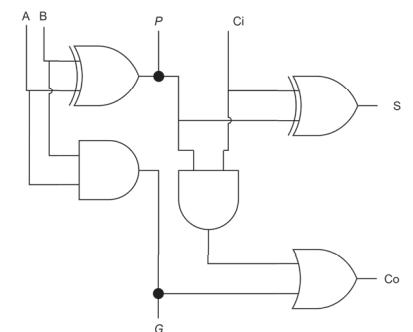

COMPUTER ARITHMETIC

▪ Adders

▪ Carry Look-ahead Adder

- Following the logic from previous slide:

- A 4-bit Carry Look-ahead Adder will have the following Carry bits:

- $C_0 = C_i$
 - $C_1 = G_0 + P_0 C_0$
 - $C_2 = G_1 + P_1 C_1$
 - $C_3 = G_2 + P_2 C_2$

- Since each of the carry bits are dependent on the carry bit from previous adder, the equations can be unpacked to produce the logical expression of the circuit:

- $C_0 = C_i$
 - $C_1 = G_0 + P_0 C_i$
 - $C_2 = G_1 + P_1 G_0 + P_1 P_0 C_i$
 - $C_3 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_i$


- A digital circuit can be constructed using the logical expression

COMPUTER ARITHMETIC

▪ Adders

▪ Carry Skip Adder

- This adder type allows prediction of the carry bit.
- Two additional outputs are taken from the adder Propagate (P) and Generate (G)
 - **P** tells us if a carry value needs to be **propagated** to the next adder.
 - **G** tells us if a carry out value was **generated** in the adder regardless of the initial value of the carry in bit.
- Using the value of **P**, we can determine if a carry bit needs to be sent into the next adder.
- By ANDing all the P outputs in an adder series, we can determine the value of the carry bit for the next adder series faster than ripple carry.
- Let us convert an 8-bit ripple carry adder into an 8-bit skip carry adder:

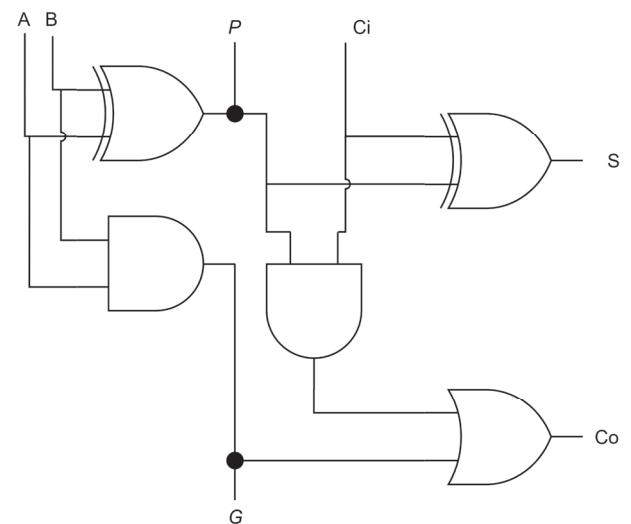


COMPUTER ARITHMETIC

▪ Adders

▪ Carry Skip Adder

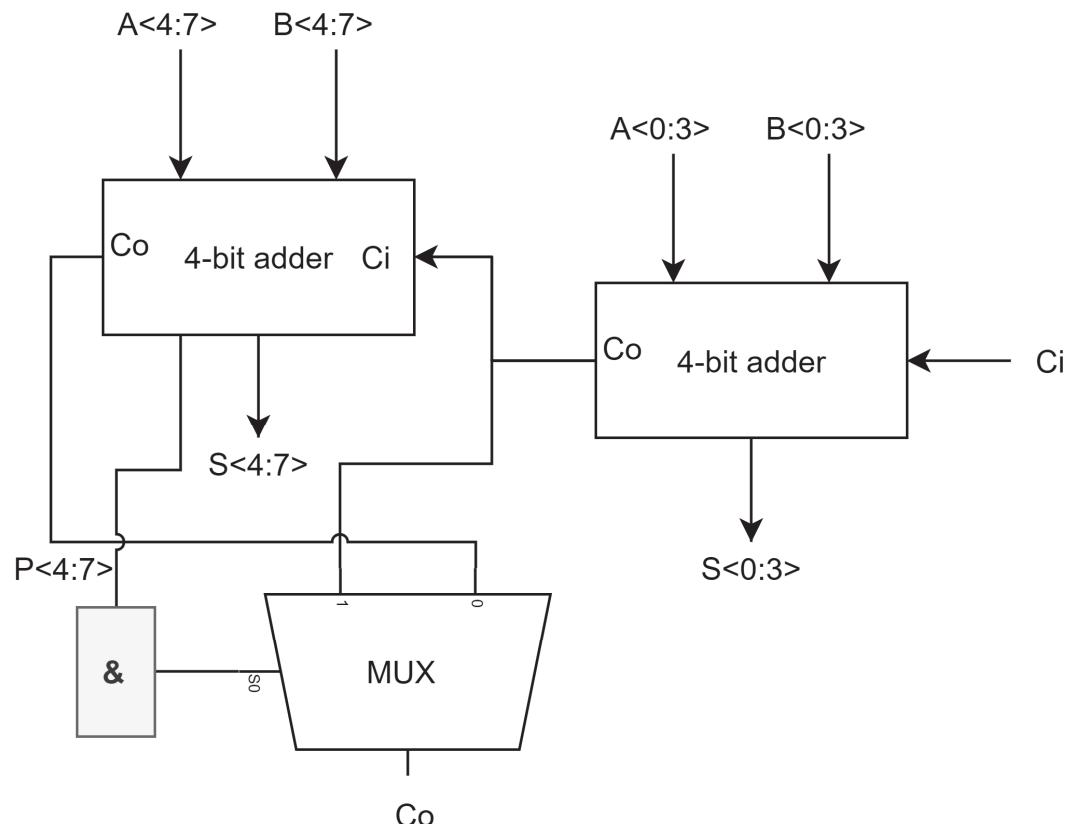- If P values for all the adders on the second series is 1, then the output of the AND gate is 1. The carry from the previous adder is used as carry out.
- If P values for the adders on the second series are not all 1, then the output of the AND gate is 0. The carry from the second adder is used as carry out.




COMPUTER ARITHMETIC

▪ Adders

- **Carry Select Adder**
 - Speculative calculation.


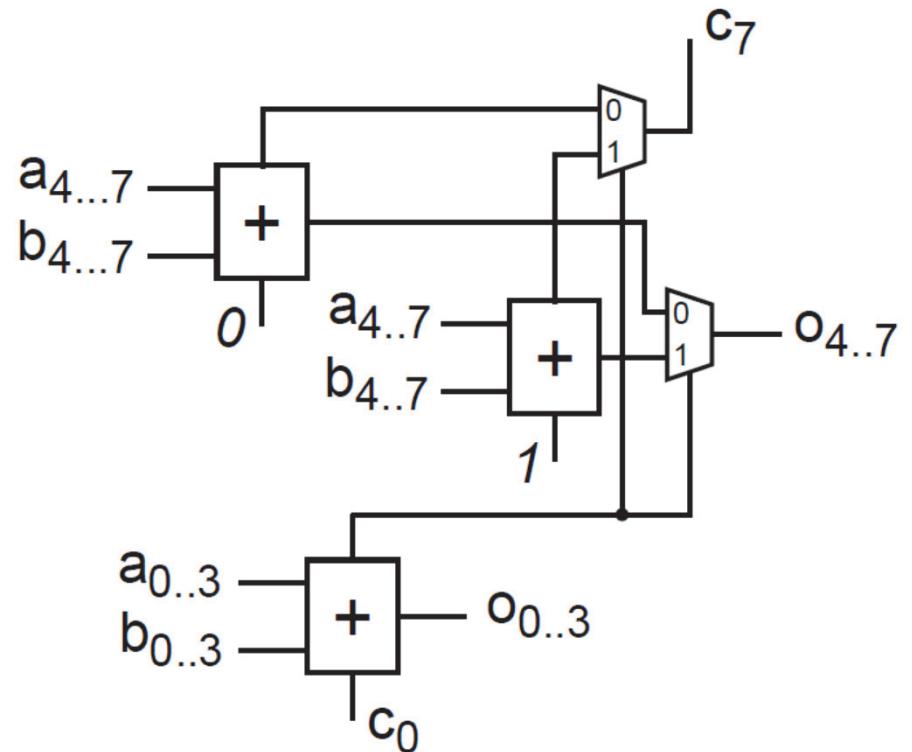
- For every group two sums and carry-outs are calculated – one with carry-in 0 and other with carry-in 1.
- The result is selected when the actual carry-in arrives.



COMPUTER ARITHMETIC IN HARDWARE

▪ Adders

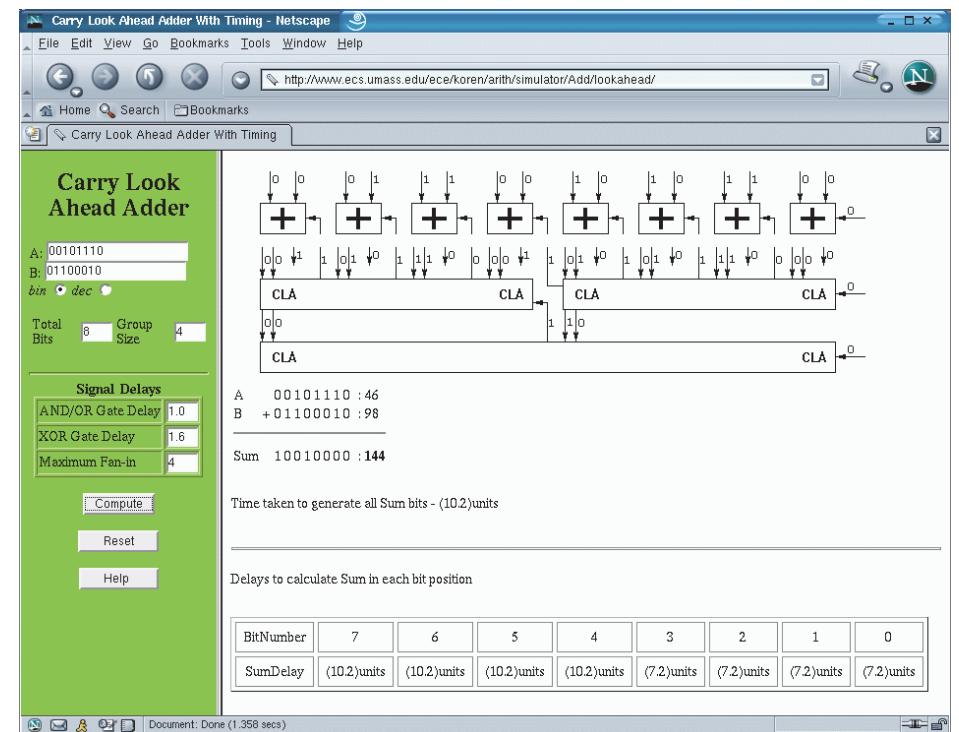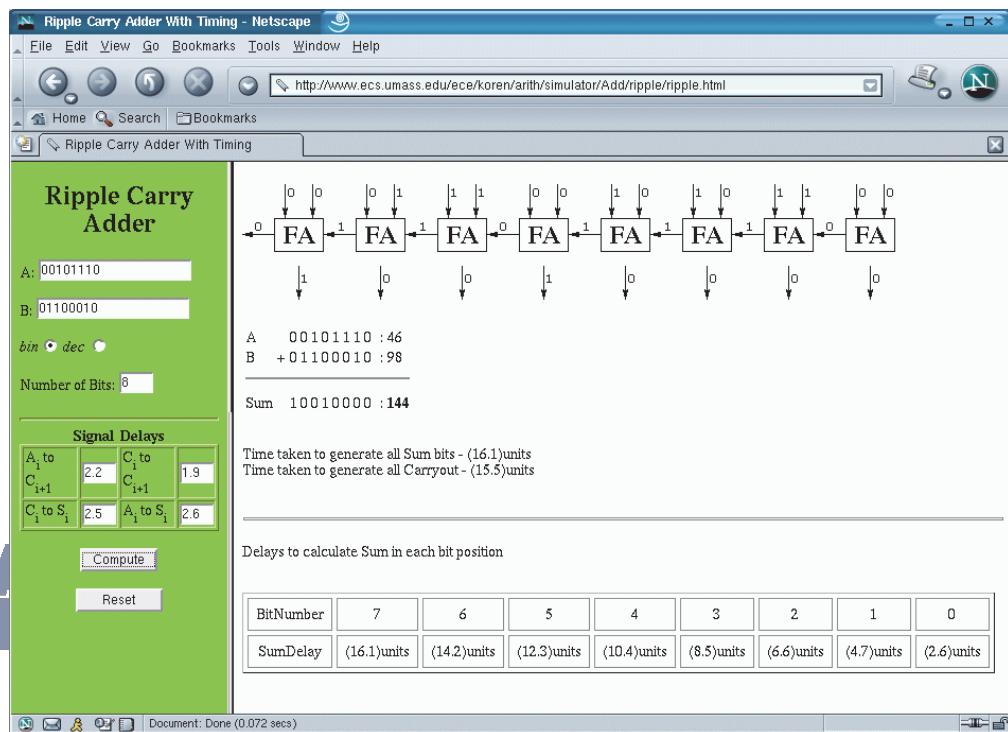
- Ripple-carry – the smallest but slowest.
- Carry look-ahead, carry skip & carry select – faster but larger.
- The size and speed depends on the block sizes and used technology.
- Computer Arithmetic Algorithms Simulator
<http://www.ecs.umass.edu/ece/koren/arith/simulator/>



COMPUTER ARITHMETIC IN HARDWARE

- Multiplication
 - Sequential multiplier
 - Adding & shifting – all implementations are based on this simple algorithm
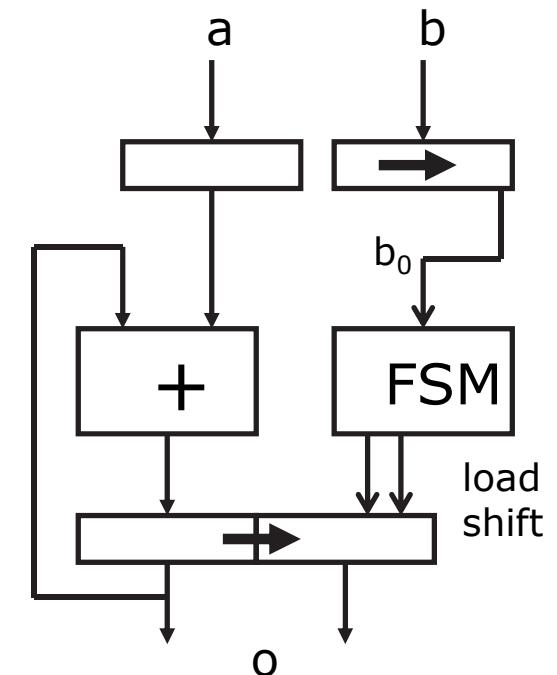
$$\begin{array}{r} 00011000 * 00001101 \quad [24 * 13] \\ \hline 1. \quad 00000000 \\ 2. \quad 00000000. \\ 3. \quad 00000000.. \\ 4. \quad 00001101... \\ 5. \quad 00001101.... \\ 6. \quad 00000000..... \\ 7. \quad 00000000..... \\ 8. \quad 00000000..... \\ \hline 000000100111000 \quad [312] \end{array}$$



COMPUTER ARITHMETIC IN HARDWARE

- Multiplication

- Sequential multiplier

- Making it faster?
 - Radix-4 – two bits at a time

00011000 * 00001101	[24 * 13]

1. 00000000	00011000 == * 0
2. 00011010..	00011000 == * 2
3. 00001101....	00011000 == * 1
4. 00000000.....	00011000 == * 0

00000100111000	[312]

- Adding "+ [0,1,2,3]*a" where $3*a=4*a-a$ – this must be remembered!

COMPUTER ARITHMETIC IN HARDWARE

▪ Multiplication

▪ Sequential multiplier



- Radix-4 – two bits at a time
- Adding "+ [0,1,2,3]*a" where $3*a=4*a-a$ – this must be remembered!
- A special flag is used ~ "carry" from previous iteration
- The flag is 0 (by default in the beginning)
 - $b_{10}=00$? \rightarrow nothing
 - $b_{10}=01$? $\rightarrow o+=a$
 - $b_{10}=10$? $\rightarrow o+=2*a$ [$o+=(a<<1)$]
 - $b_{10}=11$? $\rightarrow o-=a$ [Flag is set to 1]
- The flag is 1 (subtraction in the previous iteration)
 - $b_{10}=00$? $\rightarrow o+=a$ [$4-1==3$]
 - $b_{10}=01$? $\rightarrow o+=2*a$ [$2==1+1$]
 - $b_{10}=10$? $\rightarrow o-=a$ [$3==2+1$, the flag is set to 1 again]
 - $b_{10}=11$? \rightarrow do nothing [$4==3+1$, the flag is set to 1 again]

COMPUTER ARITHMETIC IN HARDWARE

▪ Multiplication

▪ Parallel multiplier

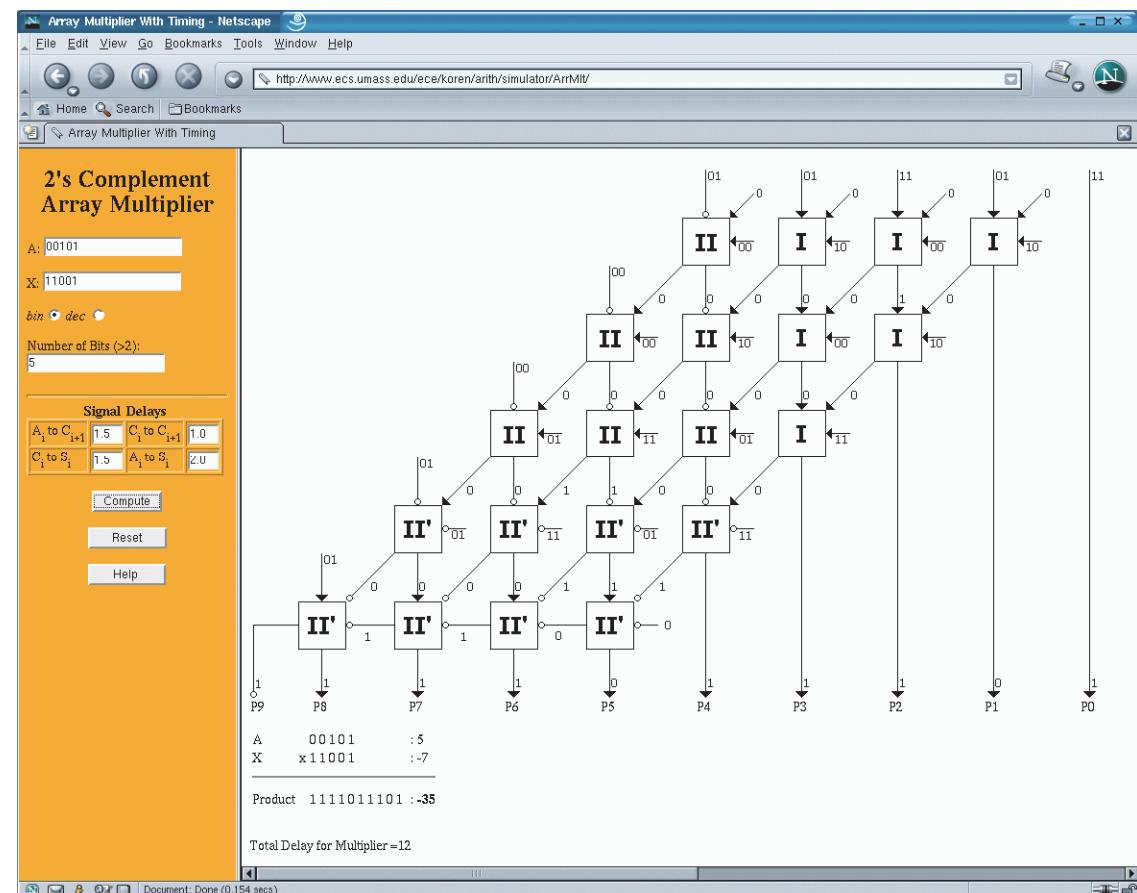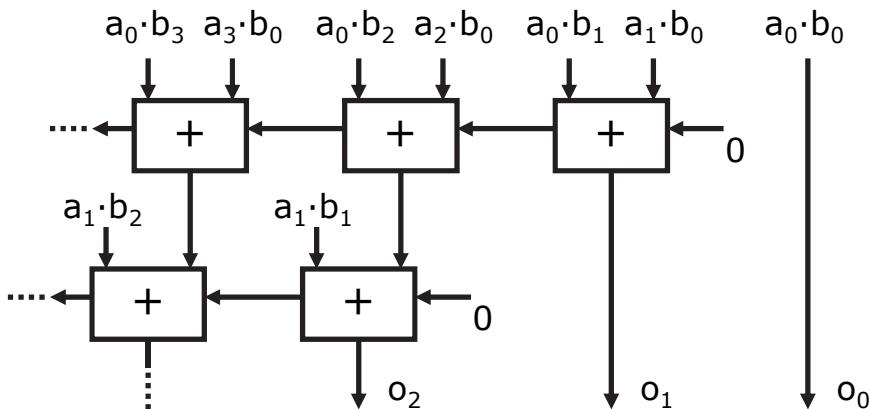- Array multiplier
- AND-gates & full adders
- Good for pipelining



COMPUTER ARITHMETIC IN HARDWARE

- Division

- Sequential divider

$$\begin{array}{r} 312 / 13 = 24 \\ 26 \\ \hline - \\ \hline 52 \\ 52 \\ \hline - \\ \hline 0 \\ \hline \end{array} \quad \begin{array}{r} 0100111000 / 01101 = 011000 \\ - 01101 \\ \hline \dots \\ 0001101000 \\ - 01101 \\ \hline \dots \\ 0000000000 \quad [\text{reminder}] \\ \hline \dots \end{array}$$

- Subtracting, checking & shifting – all implementations are based on this algorithm
 - A binary divider can be implemented using a sequence of subtractions

FINAL EXAM

▪ Topics / Tasks

- Overall setup like in the midterm exam
- Duration 60 minutes
- Tasks are bit more complex because all materials are allowed to use
 - Help from other people is not allowed!
- T/F questions about memories
- Comparison of different memories
- Mapping a short memory access trace into cache
- Short process queue scheduling
- Binary number representations and some arithmetic operations