

Introduction to FPGAs


IAS0600 Digital Systems Design with VHDL

Introduction to FPGAs

- History of FPGAs
- Reconfigurable hardware vs integrated circuits
- FPGA applications
- Inner architecture of FPGAs
- Design flow for FPGA



History. Gate Arrays

 - In the beginning, digital design was done with the '74 series of chips.
- Some people would design their own chips based on Gate Arrays, which were nothing else than an array of NAND gates:




History. PLA/PLD

  - The first programmable chips were PLAs (Programmable Logic Arrays): two level structures of AND and OR gates with user programmable connections.
- Programmable Array Logic devices were an improvement in structure and cost over PLAs. Today such devices are generically called Programmable Logic Devices (PLDs).



History. CPLD/FPGA

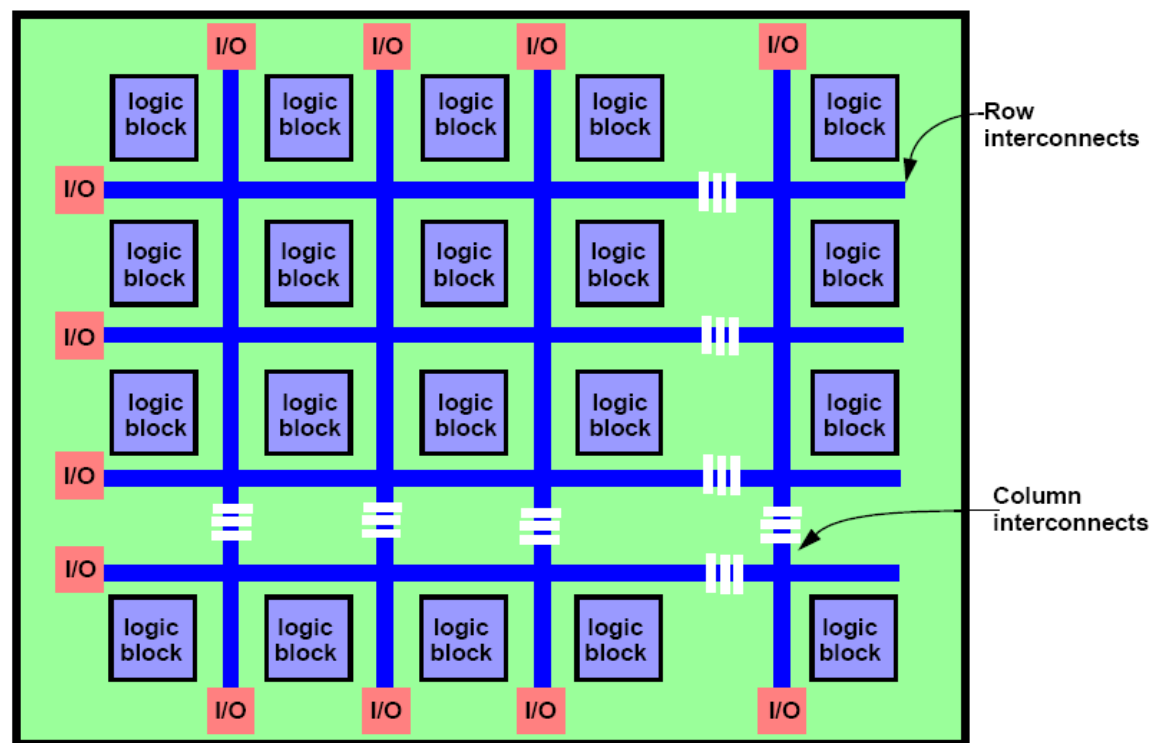
- A complex PLD (CPLD) is nothing else than a collection of multiple PLDs and an interconnection structure.
- Compared to a CPLD, a Field Programmable Gate Array (FPGA) contains a much larger number of smaller individual blocks + large interconnection structure that dominates the entire chip.



Reconfigurable hardware vs ICs

- Traditional IC
 - Once fabricated cannot be changed
 - Examples: CPU, GPU, TPU
- Reconfigurable hardware
 - Does not implement a specific circuit functionality
 - Can be reconfigured to implement any desired functionality/circuit
 - Can be reconfigured many times during the lifetime
 - Offer a flexible platform for increasingly complex systems
 - Example: FPGA (Field-Programmable Gate Array)

Reconfigurable hardware vs ICs

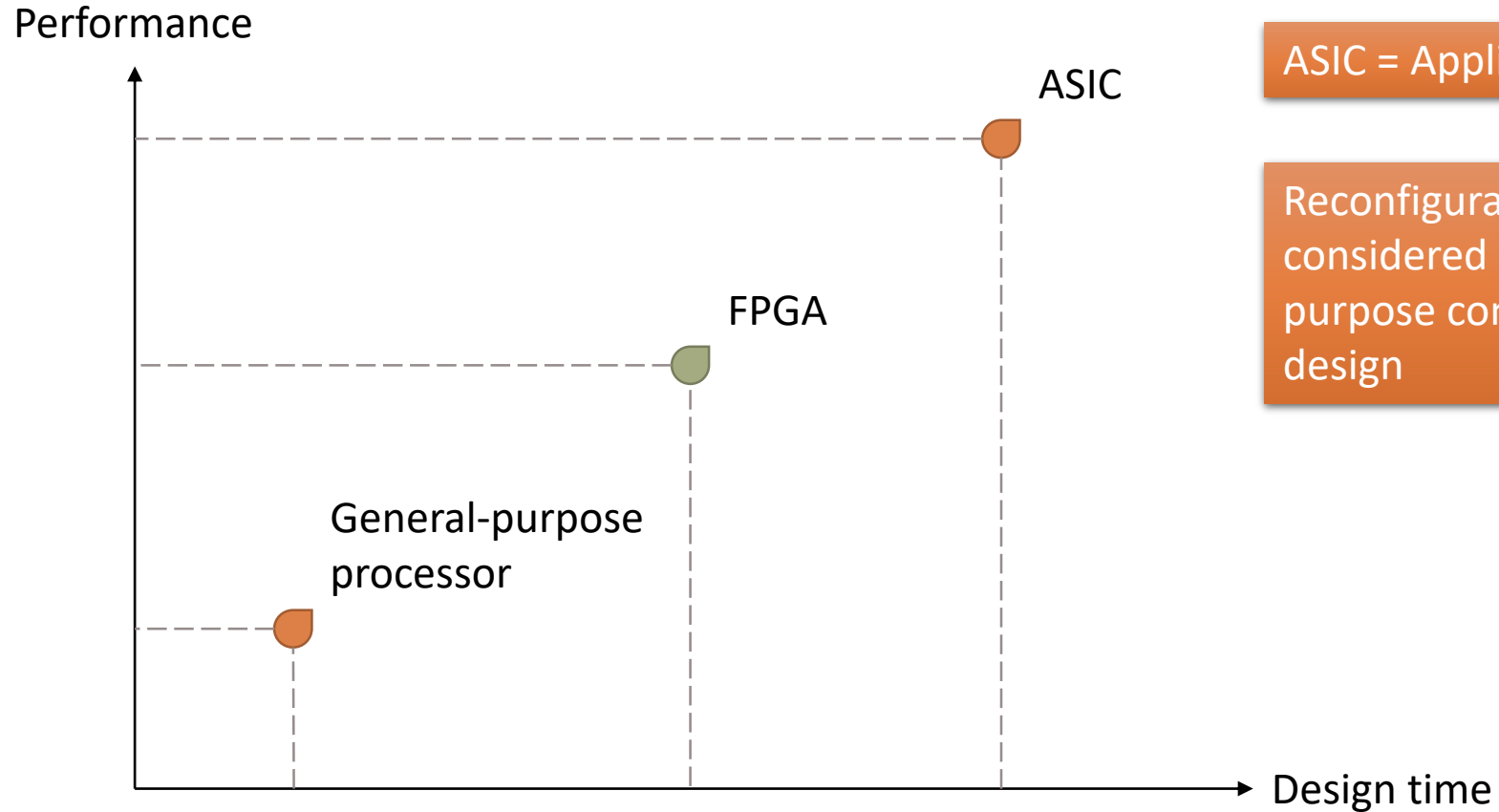


ASIC = Application Specific Integrated Circuit

Reconfigurable computing can be considered as a trade-off between general-purpose computing and application-specific design

Reconfigurable hardware vs ICs

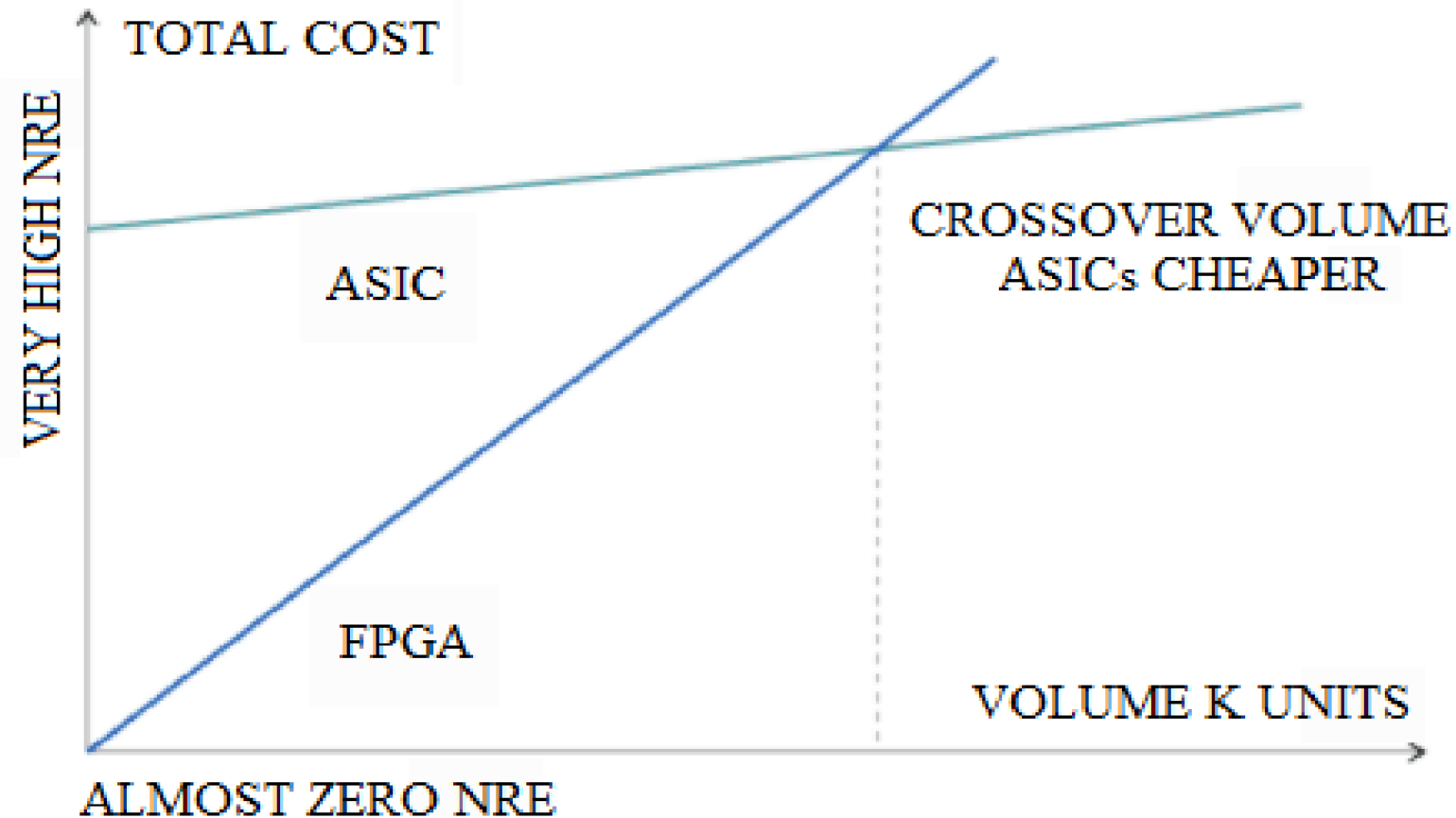- FPGAs are less costly with smaller volumes due to lower Non-Recurring Engineering (NRE) costs:



FPGA applications



Aerospace
(satellites, planes)



Military equipment



Medical devices



Automotive
industry



High-end
broadcast systems



Wired and wireless
communication



Production line
robots



Video processing
and surveillance



Data centers



AI/ML applications


Examples of FPGA applications

- NASA
 - Mars Science Lab mission (Curiosity)
 - Mars Exploration Rover mission (Spirit, Opportunity)
 - Mars 2020 Perseverance rover
- Microsoft
 - Bing indexing acceleration
 - Deep learning acceleration in Azure cloud
- Amazon
 - Amazon Elastic Compute Cloud (EC2) F1 instances




<https://www.xilinx.com/about/blogs/xilinx-xclusive-blog/2021/rover-lands-on-mars-with-xilinx-fpgas-on-board.html>

FPGA structure

 


- Basic blocks:
 - Configurable Logic Block (CLB)
 - Implement logic functions
 - Connection Box (CB)
 - Connect inputs and outputs of CLBs to the connection wires
 - Switch Box (SB)
 - Connect vertical and horizontal wires
 - Input/Output Block (IOB)
 - Connect IO pins with the internal resources

Configurable Logic Block

 


- Look-up Table (LUT) implements a combinational logic function
 - Stores a truth table of the function
 - Inputs act as an address or index of the table cell
- Register (flip-flop FF) optionally stores the output of LUT
- MUX selects the output of the CLB

Switch Box

 


- Each switch point consists of six programmable switches
- Switches are controlled by configuration memory cells

Connection Box

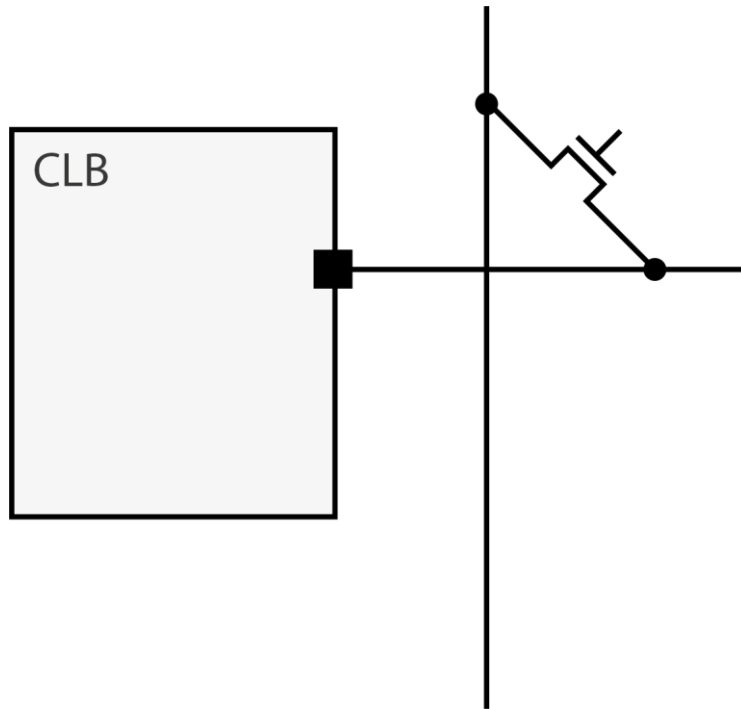


Connecting to output of a CLB

 

Connecting to input of a CLB



Input/Output Block

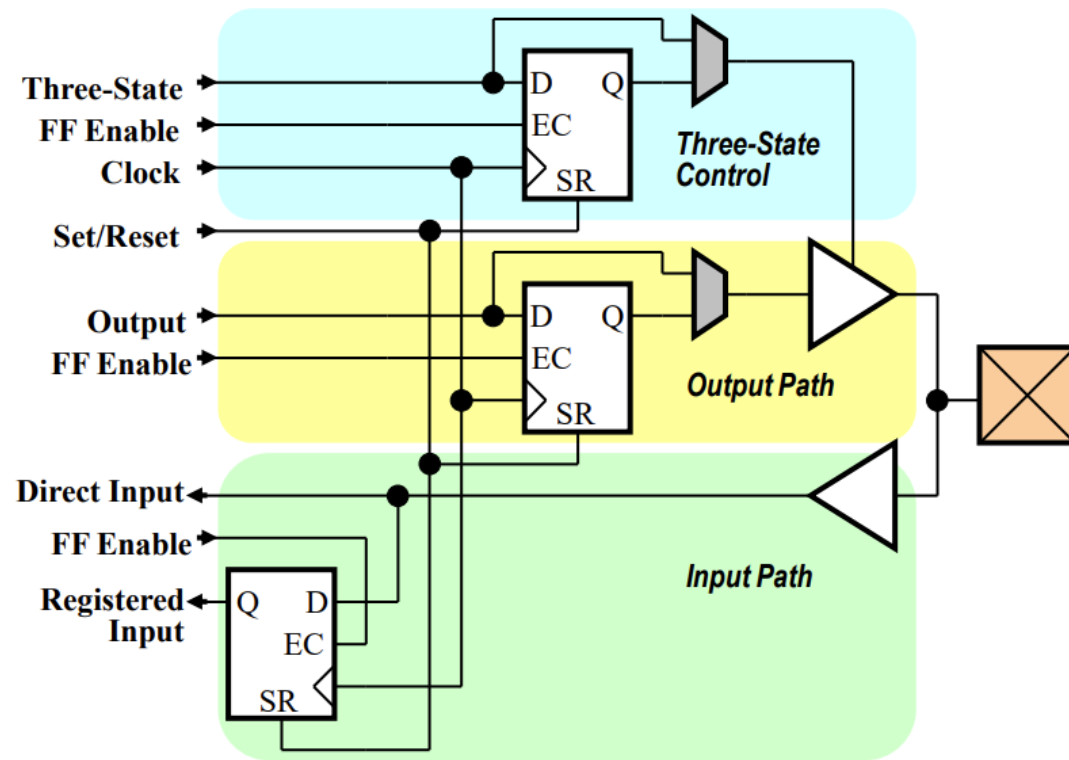

- Each IOB can work as a uni- or bi-directional IO
- Outputs can be forced into high-impedance
- Inputs and outputs can be latched to registers

Cristinel Ababei, *EECE-4740 Advanced VHDL and FPGA Design* [lecture slides]

Example

  


FPGA technology

- Antifuse
 - One-time programmable
- Flash
 - Non-volatile memory → configuration is not lost when the power is down
 - Limited re-programmability
- SRAM
 - Volatile memory
 - Easily re-programmable

FPGA vendors

- AMD-Xilinx Inc.
 - Intel (Altera)
- } ~90% of the market
- Microchip
 - Lattice Semiconductor
 - QuickLogic Corporation
 - Achronix
 - Efinix Inc.

Design flow for FPGA

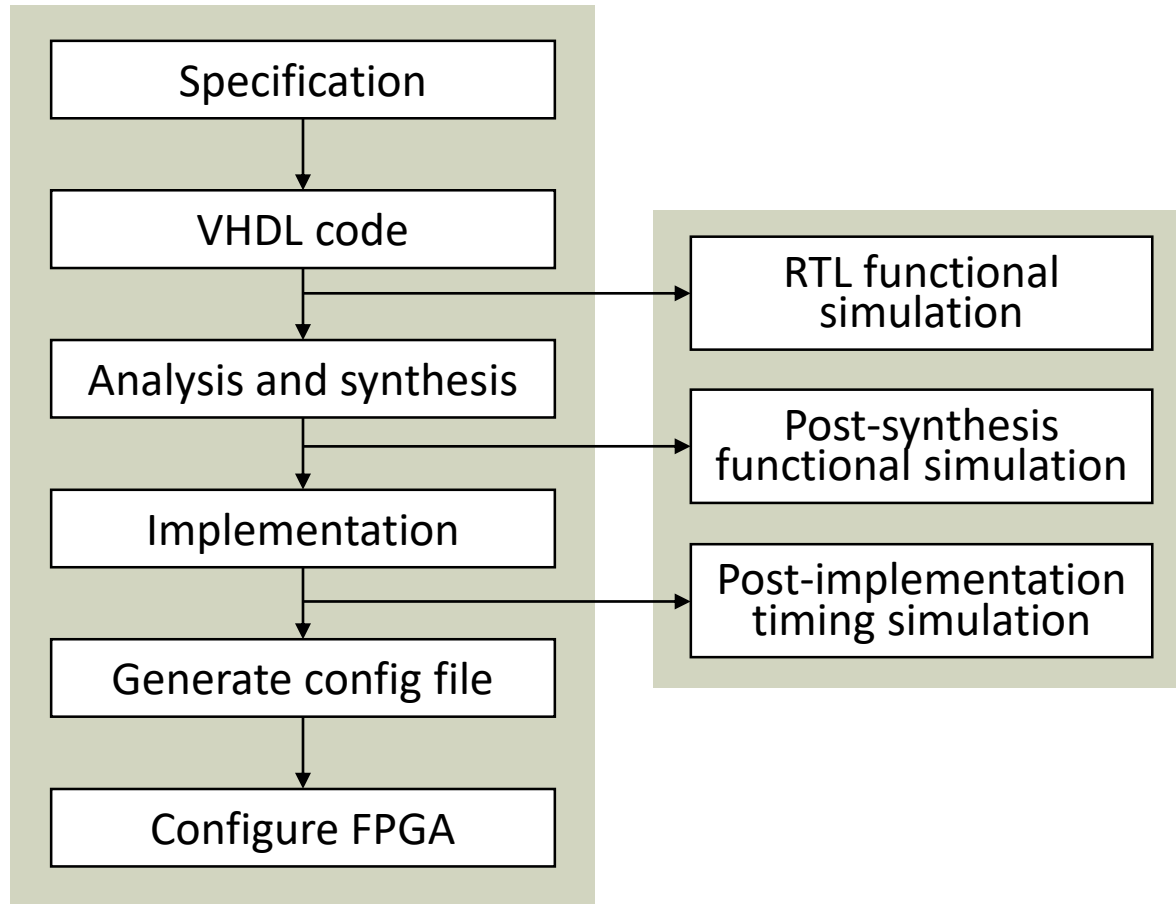

- Synthesis is the transformation of the HDL description into HW components
- Implementation combines placement and routing
- Configuration file (bitstream) is loaded into configuration memory

Synthesis



HDL description → HW components

Technology mapping

```
architecture MLU_DATAFLOW of MLU is
  signal A1:STD_LOGIC;
  signal B1:STD_LOGIC;
  signal Y1:STD_LOGIC;
  signal MUX_0,MUX_1,MUX_2,MUX_3:STD_LOGIC;
begin
  A1<=A when (NEG_A='0') else
    not A;
  B1<=B when (NEG_B='0') else
    not B;
  Y<=Y1 when (NEG_Y='0') else
    not Y1;


  MUX_0<=A1 and B1;
  MUX_1<=A1 or B1;
  MUX_2<=A1 xor B1;
  MUX_3<=A1 xnor B1;

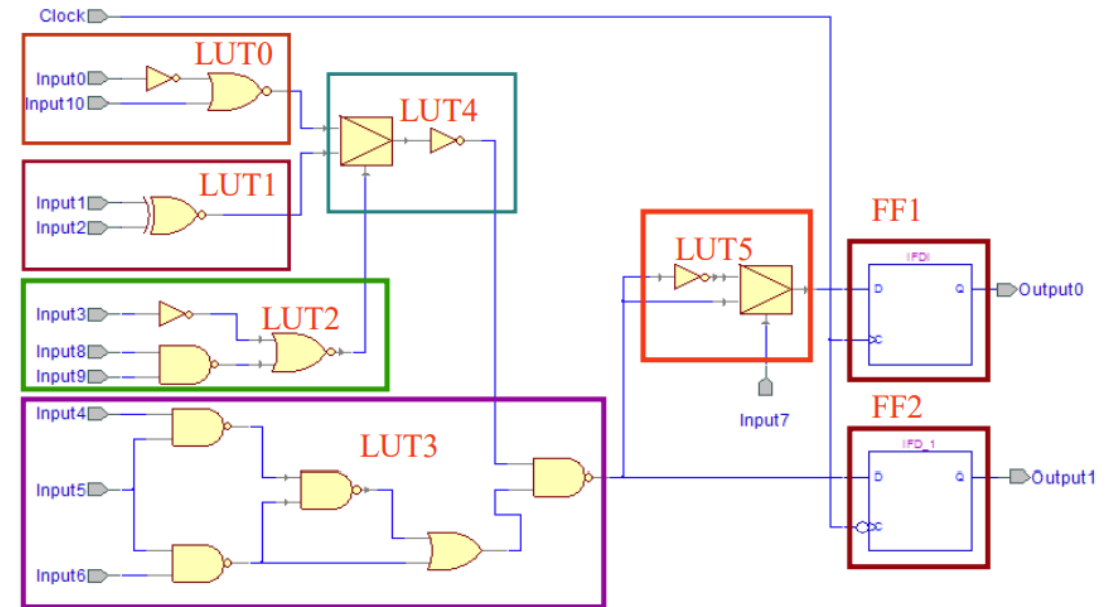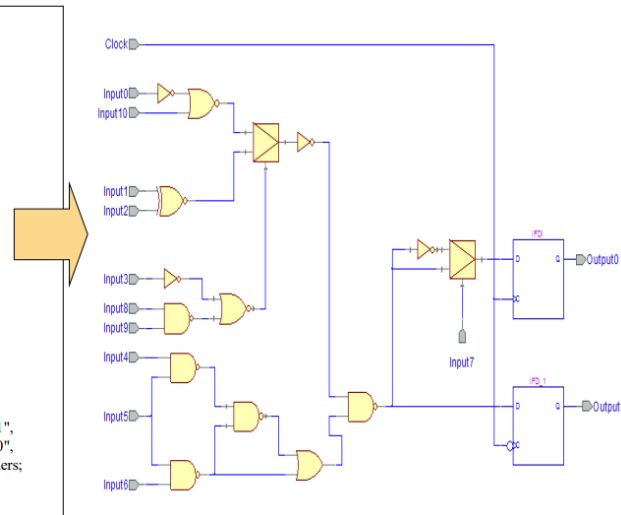  with (L1 & L0) select
    Y1<=MUX_0 when "00",
        MUX_1 when "01",
        MUX_2 when "10",
        MUX_3 when others;
end MLU_DATAFLOW;
```




Implementation

Placement

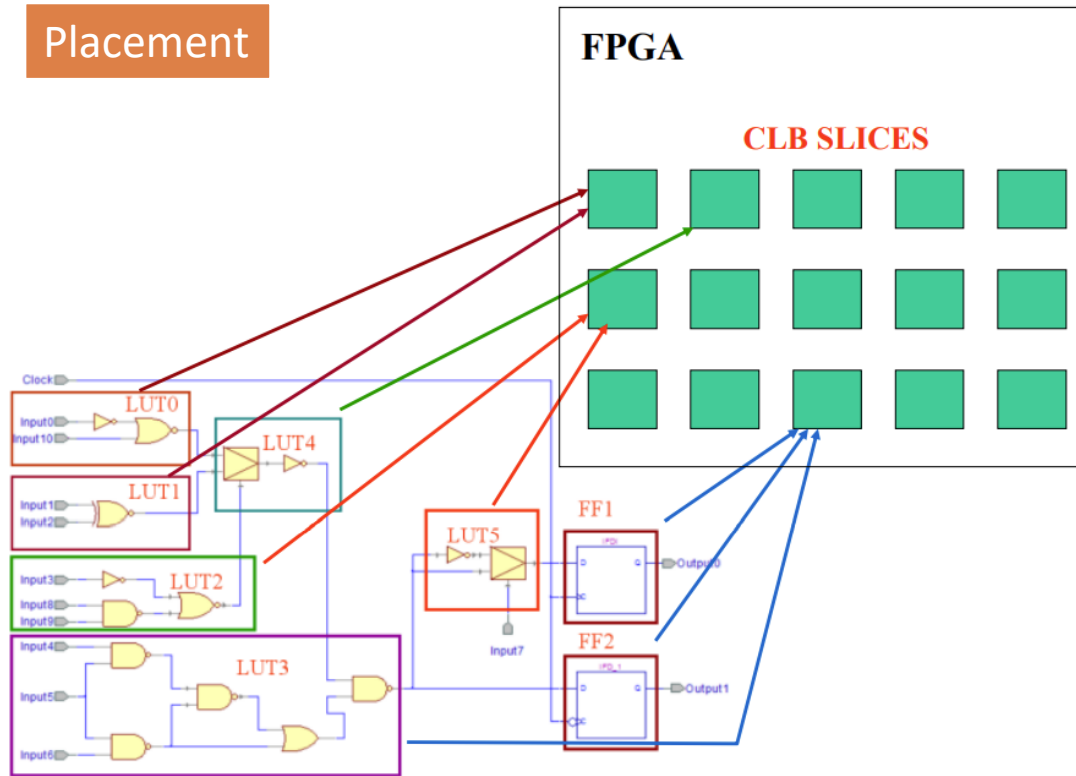

Routing

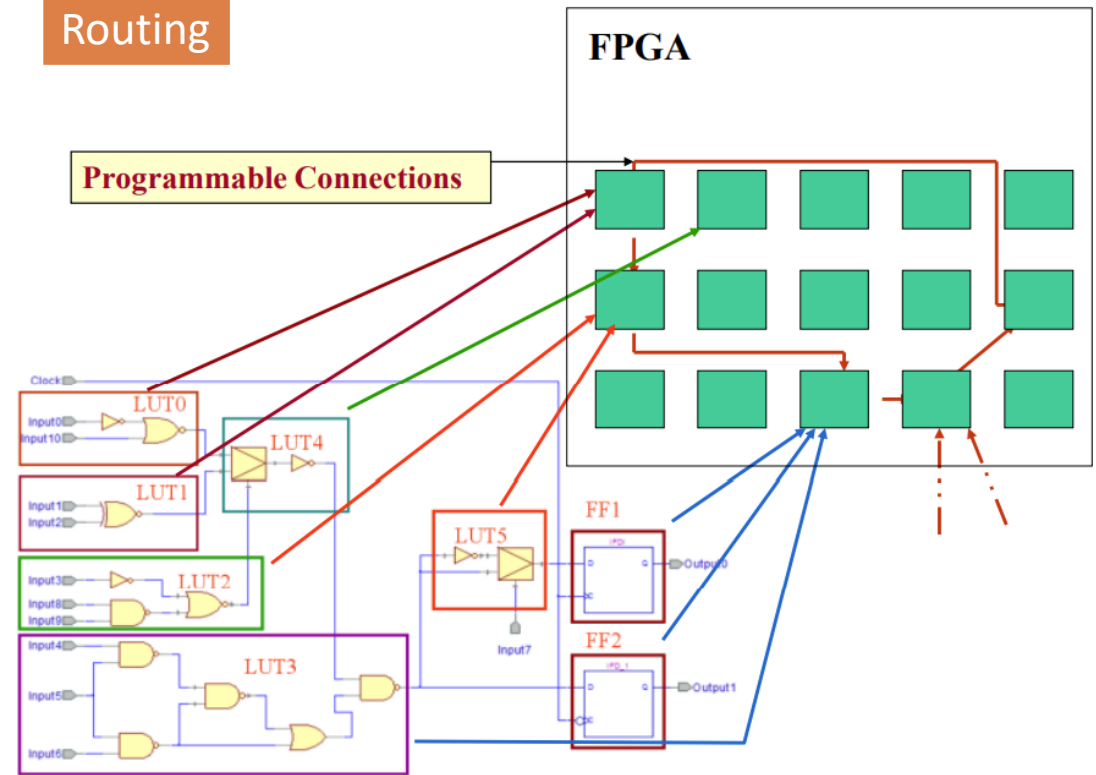

Configuration

- Once a design is implemented, you must create a file that the FPGA can understand
- This file is called a bitstream: a BIT file
- Bitstream holds values that will be loaded into configuration memory
 - LUT values
 - Routing configuration
 - Control signals for CLBs and IOBs