


Dataflow modeling style

IAS0600 Digital Systems Design with VHDL


Natalia Cherezova, Peeter Ellervee

Modeling styles

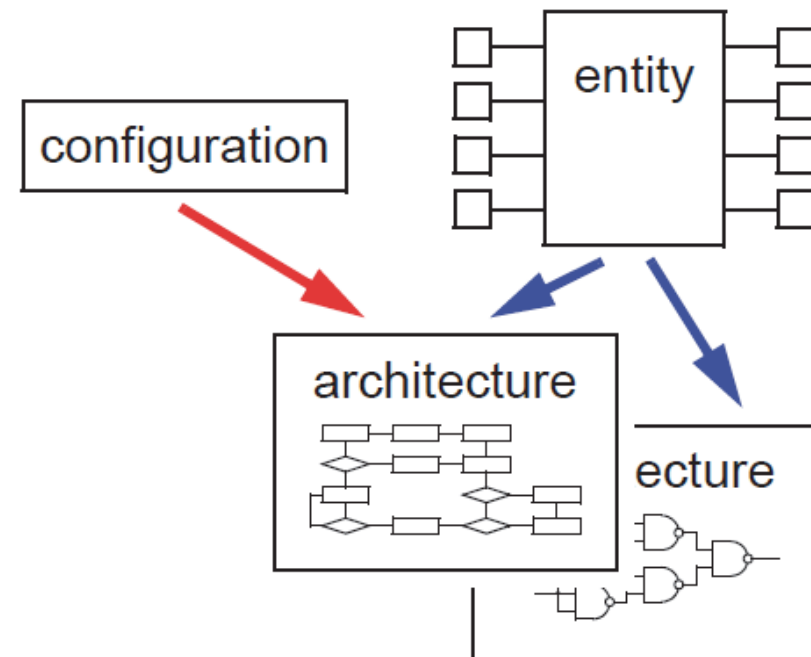- Dataflow
 - Concurrent signal assignments
- Structural
 - Interconnected components
- Behavioral
 - Sequential statements (in a process)
- Architectures may combine different styles to describe the needed behavior and/or structure of the system



Boolean equation

 

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity example is
  Port ( a, b, c : in STD_LOGIC;
        q : out STD_LOGIC);
end example;

architecture bool of example is
  signal d : STD_LOGIC;
begin
  d <= b AND c;
  q <= (NOT a) OR d;
end bool;
```

- Supported operators
 - AND, OR, XOR, NOT, NAND, NOR, XNOR
- The only operator with precedence over the others is NOT

```
q <= (NOT a) OR d; -- optional brackets
q <= a OR (b AND c); -- brackets are required
```

```
q <= (NOT a) OR d;
d <= b AND c;
```


```
q <= (NOT a) OR (b AND c);
```

Conditional signal assignment

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity example is
  Port ( a, b, c : in STD_LOGIC;
         q : out STD_LOGIC);
end example;

 architecture cond of example is
begin
  q <= '1' when a = '0' else
       '1' when b = '1' and c = '1' else
       '0';
end cond;
```



a	b	c	q
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

- The WHEN ... ELSE statement

```
<signal> <= <value> when <condition> else
           <value> when <condition> else
           ...;
```


- The order of conditions is important
- Output should get the value in all the possible cases

Selected signal assignment

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity example is  
  Port ( a, b, c : in STD_LOGIC;  
         q : out STD_LOGIC);  
end example;
```

```
architecture select of example is  
begin  
  with (a & b & c) select  
    q <= '1' when "000" | "001",  
         '1' when "010" | "011",  
         '1' when "111",  
         '0' when others;  
end select;
```

 

a	b	c	q
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1


- The WITH...SELECT statement

```
with <identifier> select  
  <signal> <= <value> when <identifier values>,  
           <value> when <identifier values>,  
           ...;
```

- Multiple identifier values can be grouped together using either | (means or) or TO (defines range)
- All identifier values should be covered, for which the keyword OTHERS is very useful

Data type STD_LOGIC

 
- 'U' uninitialized model behavior
- 'X' forcing unknown model behavior
- '0' forcing 0 logic level ("transistor")
- '1' forcing 1 logic level ("transistor")
- 'Z' high impedance disconnect
- 'W' weak unknown model behavior
- 'L' weak 0 logic level ("resistor")
- 'H' weak 1 logic level ("resistor")
- '-' don't care match all



- IEEE.std_logic_1164 – std_ulogic, std_logic ja std_logic_vector
 - std_ulogic – base type; std_logic – multiple signal sources and resolution function
 - IEEE.std_logic_arith & other packages define also arithmetic operations

Testbench automation

 - During the simulation and testing, design inputs are driven by test vectors, and outputs are monitored and checked
- How to automate?
 - Output verification through assertion statements
 - Automated test vector generation for inputs



Assertions

- The ASSERT statement

```
assert <condition that should be TRUE>  
  report <message issued when the condition is FALSE>  
  severity <assertion type>;
```

- 4 types of assertions (severity levels):
 - note
 - warning
 - error
 - failure (simulation halts)

Input generation

- Loop through all possible input values

```
for <iterator> in <start> to <end> loop
  <loop_body>
end loop;
```

- No need to declare an iterator beforehand
- Define the range of the loop using integer values
- Convert integer values into corresponding std_logic_vector values
 - Uncomment `ieee.numeric_std.all` library
 - Integer → unsigned → std_logic_vector

```
x <= std_logic_vector(to_unsigned(<integer>, <number_of_bits>));
```

3 can be represented as 11
or as 0011 etc.

Testbench template

```
stimuli : process
begin
  for i in ... to ... loop
    for j in ... to ... loop
      in1_tb <= ...      -- convert integer i to std_logic_vector
      in2_tb <= ...      -- convert integer j to std_logic_vector
      wait for 10 ns;    -- required for the simulation!
      assert ...        -- compare UUT output with the result of i and j comparison
    end loop;
  end loop;
  wait;                -- halt the simulation
end process;
```



Problem: result of a comparison is of type BOOLEAN, design entity output is of type STD_LOGIC, there is no library function for BOOLEAN to STD_LOGIC conversion.



Solution: write conversion function ourselves.

Functions

- Function is a block of sequential VHDL code implementing a solution for a commonly encountered problem

```
function <name> (<input_list>) return <return_value_type> is  
  [declarative_part]  
begin  
  <statement_part>  
  return <expression>;  
end function;
```

- A function call is always a part of the expression
- Only one value can be returned
- No timing control allowed!

Boolean to std_logic function

```
architecture arch of testbench is
-----
---- put your function definition in the -----
---- declarative part of the architecture -----
-----

    function bool_to_std_logic (input: boolean) return std_logic is
begin
    if input then
        return '1';
    else
        return '0';
    end if;
end function;

begin
    ...
    assert (eq_o_tb = bool_to_std_logic(i = j))
    ...
end arch;
```