





# Arithmetic circuits, parametric design and finite state machines

IAS0600 Digital Systems Design with VHDL



Natalia Cherezova, Peeter Ellervee
    
# Arithmetic circuits


- Digital system == data-path + control-path
  - Data-path ~ arithmetic units & registers
  - Control-path ~ finite state machine (FSM)
    - Often multiple FSM-s
- Central building blocks of digital systems
- Various implementations exist
- Trade off between complexity and speed



# Digital multiplier

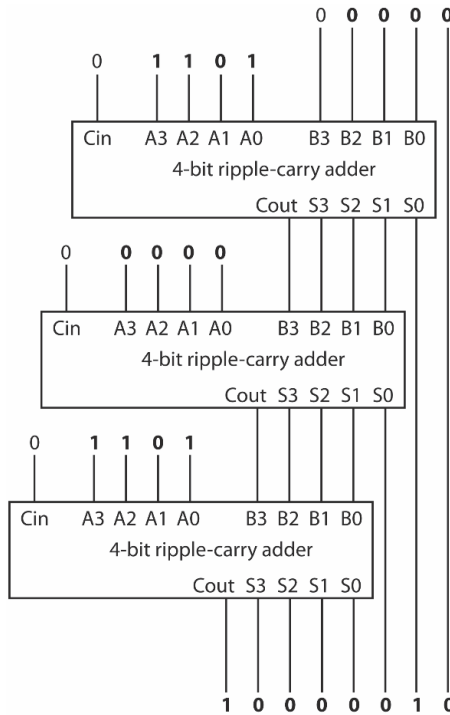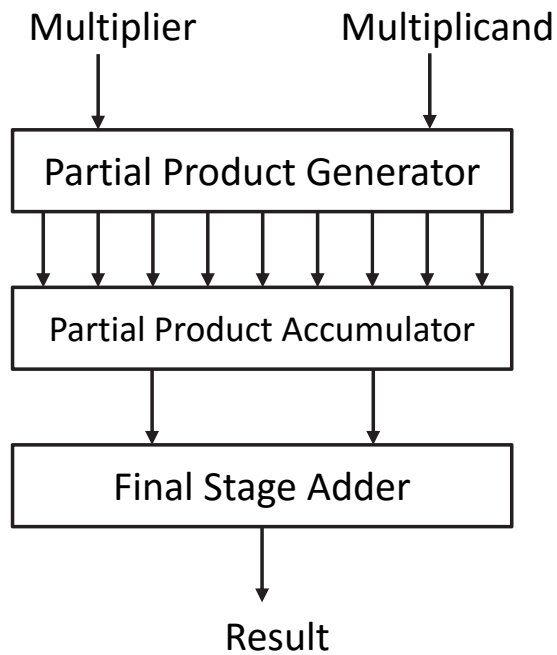


Partial products accumulator

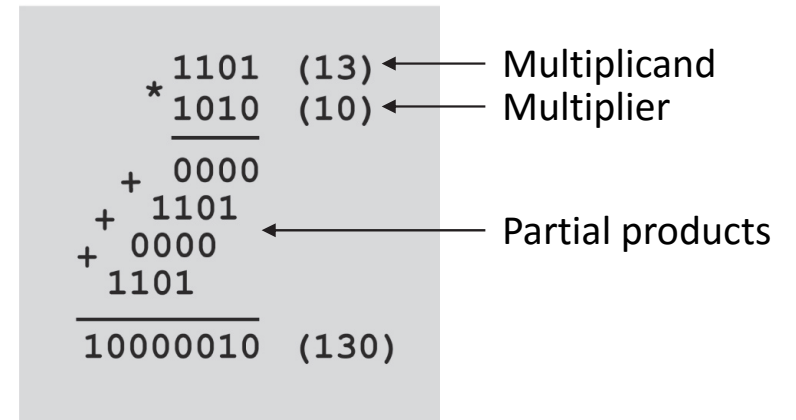


# Ripple carry adder

- Full adders connected in series

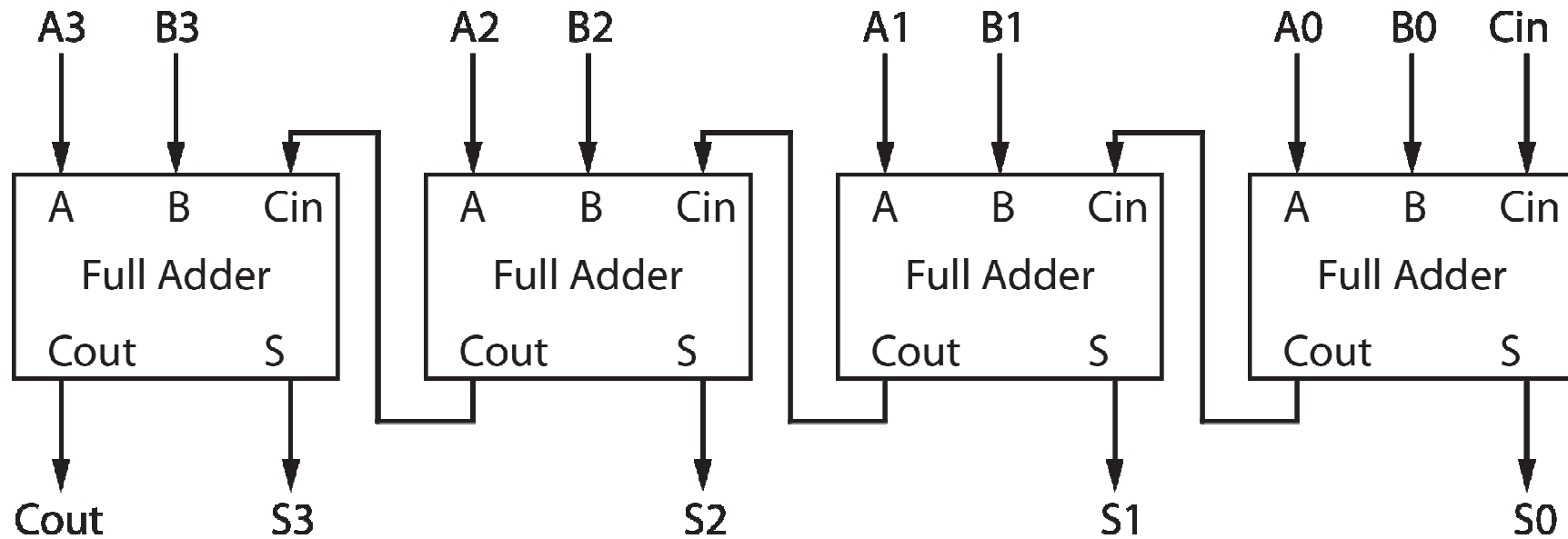

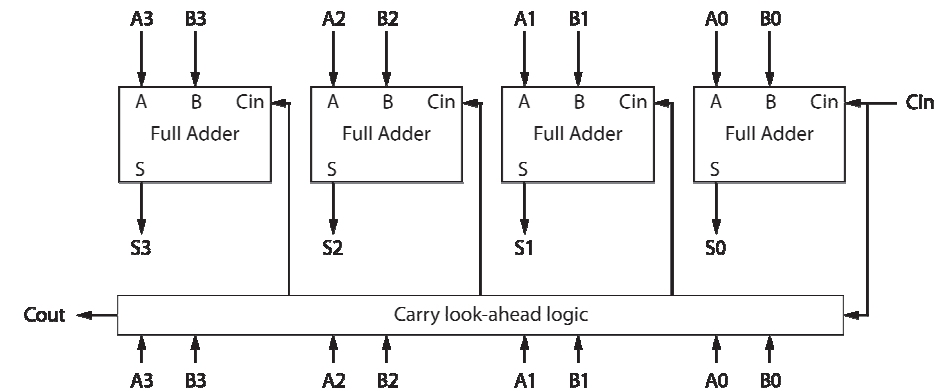
# Fast carry propagation

- Carry look-ahead adder
  - Full adders work in parallel, carry values are calculated separately
  - Generated carry  $G_i = A_i$  and  $B_i$
  - Propagated carry  $P_i = A_i$  or  $B_i$  (or  $P_i = A_i \text{ xor } B_i$ )
  - $C_{i+1} = G_i$  or ( $P_i$  and  $C_i$ )
  - $C_0 = C_{input}$



 - Carry select adder
  - Result is calculated for both carry-in values
  - Result is selected when the carry-in arrives



# Arithmetic operations simulator

- <http://www.ecs.umass.edu/ece/koren/arith/simulator/>

### Ripple Carry Adder


A: 00101110  
B: 01100010

bin • dec •

Number of Bits: 8

Signal Delays			
A <sub>i</sub> to C <sub>i+1</sub>	2.2	C <sub>i</sub> to C <sub>i+1</sub>	1.9
C <sub>i</sub> to S <sub>i</sub>	2.5	A <sub>i</sub> to S <sub>i</sub>	2.6

Compute  
Reset

 

A 00101110 :46  
B +01100010 :98  
Sum 10010000 :144

Time taken to generate all Sum bits - (16.1)units  
Time taken to generate all Carryout - (15.5)units

Delays to calculate Sum in each bit position

BitNumber	7	6	5
SumDelay	(16.1)units	(14.2)units	(12.3)units

### Carry Look Ahead Adder


A: 00101110  
B: 01100010

bin • dec •

Total Bits: 8 Group Size: 4

Signal Delays	
AND/OR Gate Delay	1.0
XOR Gate Delay	1.6
Maximum Fan-in	4

Compute  
Reset  
Help

 

A 00101110 :46  
B +01100010 :98  
Sum 10010000 :144

Time taken to generate all Sum bits - (10.2)units

Delays to calculate Sum in each bit position


BitNumber	7	6	5	4	3	2	1	0
SumDelay	(10.2)units	(10.2)units	(10.2)units	(10.2)units	(7.2)units	(7.2)units	(7.2)units	(7.2)units

### 2's Complement Array Multiplier

A: 00101  
X: 11001  
bin • dec •  
Number of Bits (>2): 5

Signal Delays			
A <sub>i</sub> to C <sub>i+1</sub>	1.5	C <sub>i</sub> to C <sub>i+1</sub>	1.0
C <sub>i</sub> to S <sub>i</sub>	1.5	A <sub>i</sub> to S <sub>i</sub>	2.0

Compute  
Reset  
Help

 

# Parametric design

- Generic value
- Generate statement
- Attributes

# Generic

- Generic parameters allow parameterizing the design
- Increase flexibility and reusability of the code
- Default value can be overwritten during component instantiation

```
entity <entity_name>  
  generic (<name> : <type> := <default_value>;  
          <name> : <type> := <default_value>;  
          ... );  
  port ( ... );  
end <entity_name>;
```



# Generate statement

- Concurrent statement
- Unconditional generate

Both range limits should be static



```
<label> : for <identifier> in <range> generate  
    <concurrent statements>  
end generate;
```

- Conditional generate

```
<label> : if <condition> generate  
    <concurrent statements>  
end generate;
```

# Attributes

- Four categories of predefined attributes
  - Predefined attributes of scalar types
    - E.g., integer'image(x)
  - Predefined attributes of array types
  - Predefined attributes of signals
    - E.g., clock'event
  - Predefined attributes of named entities

# Attributes of array types

Name	Result
<code>x'left</code>	The left bound of the index range of x
<code>x'right</code>	The right bound of the index range of x
<code>x'low</code>	Lower bound of the index range of x
<code>x'high</code>	Higher bound of the index range of x
<code>x'range</code>	Range of the index range of x
<code>x'reverse_range</code>	Reverse range of the index range of x
<code>x'length</code>	Number of values in x
<code>x'ascending</code>	TRUE if the index range of x is ascending, FALSE otherwise
<code>x'element</code>	Type of elements of x

# Arrays

- Considered as a type in VHDL
- **Constrained**
  - Range is defined in the type definition

```
type constr_array is array (0 to n-1) of std_logic_vector(n-1 downto 0);  
signal constr_array_signal : constr_array;
```

- **Unconstrained**
  - Range is defined in the signal declaration

```
type unconstr_arr is array (natural range <>) of std_logic_vector(n-1 downto 0);  
signal unconstr_array_signal : unconstr_arr(0 to n-1);
```

NATURAL is the subtype of the INTEGER restricted to the values greater than or equal to 0

# Using attributes – flexible loops

- Inflexible code

```
signal s: bit_vector (7 downto 0);  
...  
for i in 0 to 7 loop ...
```

- Flexible code

```
constant sz: integer := 16;  
signal s: bit_vector (sz-1 downto 0);  
...  
for i in 0 to sz-1 loop ...
```

- More flexible code


- Attributes & generic parameter

```
entity ... is  
generic (sz: positive);  
port ...  
...  
signal s: bit_vector (sz-1 downto 0);  
...  
for i in s'low to s'high loop ...  
for i in s'reverse_range loop ...
```
 
# Using attributes – set-up & hold times

- Set-up – the input data must be fixed for certain time before the active clock flank
- Hold – the input data must be stable for certain time after the active clock flank

```
process (clock,data_in) begin
  if clock'event and clock='1' then
    assert data_in'last_event >= 3 ns
    report "setup time violation" severity warning;
    data_out <= data_in after 3 ns;
  end if;
  if data_in'event and clock='1' then
    assert clock'last_event >= 5 ns
    report "hold time violation" severity warning;
  end if;
end process;
```




# Finite State Machine

- FSM is a modelling technique that provides systematic approach for designing sequential circuits
- A process is divided into finite number of states
- Each state performs its task
- Process can be in one of those states at a time
- Workflow of the process is represented by the transition between states
- Transition between states is based on control signals (inputs)

# Representation

Transition graph

 

Transition table

Current state	Next state			Output
	rst = '1'	in = '0'	in = '1'	
state0	state0	state0	state1	out = '0'
state1	state0	state0	state1	out = '1'



# FSM types


- **Moore FSM**
  - Named after Edward F. Moore (1925–2003)
  - The output of the state does not depend on the input
- **Mealy FSM**
  - Named after George H. Mealy (1927–2010)
  - The output of the state depends on the input
  - Usually require less states than the Moore machine

# FSM in VHDL


- Create a state type for your FSM (enumerated type)


```
type State is (State_0, State_1, State_2, State_3, State_4);  
signal current_state, next_state : State;
```

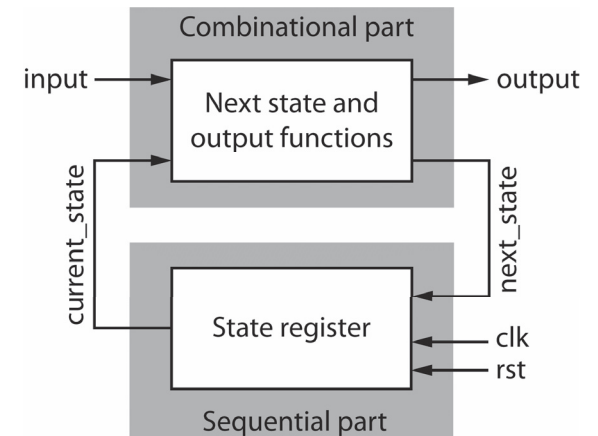- Divide the FSM description into 2 parts (processes)
  - Combinational for output and next state computations
  - Sequential for current state storage
- Keep in mind
  - Registers change on the next clock edge
  - Outputs of the combinational logic are computed immediately



# Unintended latch


- To avoid unintended latch inference from a combinational process
  - Add all read signals to the sensitivity list
  - Assign values to the output signals in every case
- During functional simulation everything will be correct
- But the design will not work as intended on the board
- Keep an eye for warning messages from the synthesis tool
  -  [Synth 8-327] inferring latch for variable 'eq\_o\_reg' [comparator.vhd:115]
- Try post-implementation timing simulation




Tip: assign default value at the beginning of the process
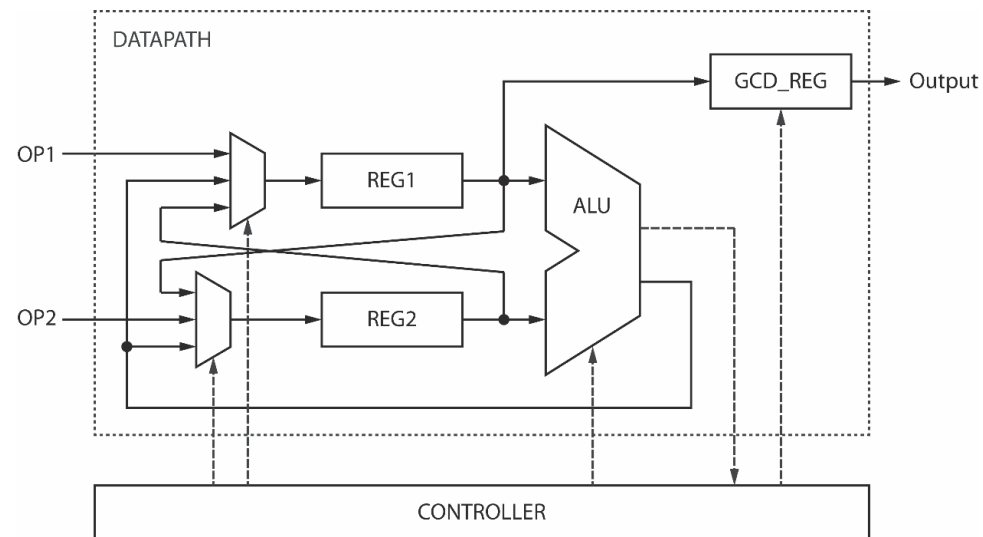
# Datapath

- Datapath is a collection of units that hold the data and operate on the data
- Functional units that form the path between the inputs and the outputs
- Datapath is controlled by the FSM



# Algorithm to FSM

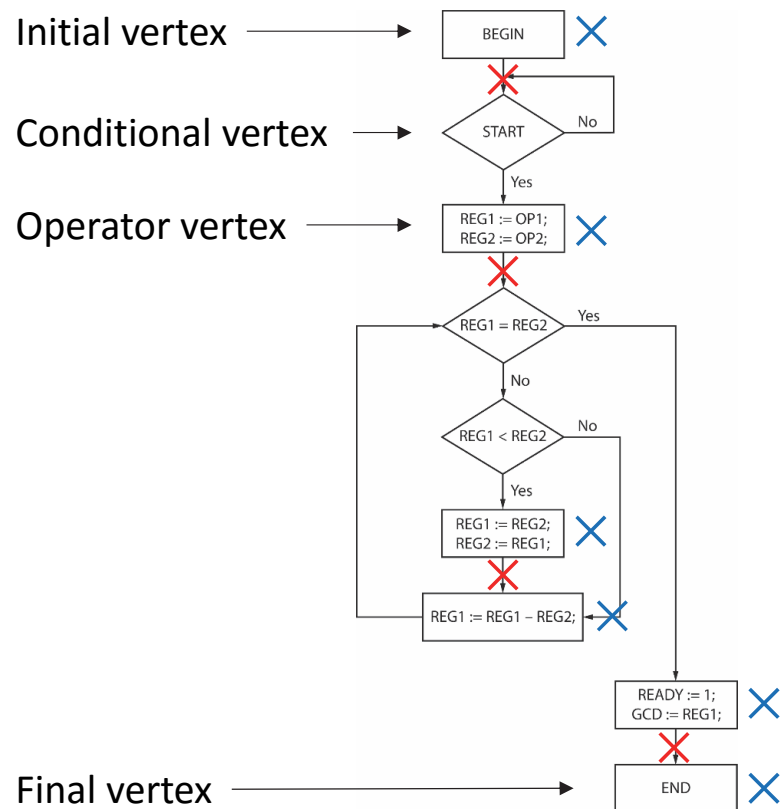

- Draw an algorithmic graph
- Identify inputs of the FSM
  - $x_0 = \text{start}$
  - $x_1 = (\text{reg1} = \text{reg2})$
  - $x_2 = (\text{reg1} < \text{reg2})$
- Identify outputs of the FSM
  - $\text{reg1}, \text{reg2}, \text{gcd\_reg}$  inputs
  - $\text{ready value}, \text{ALU opcode}$
- Identify states

Inputs are defined by the conditional vertices



Outputs will control the operations

**Mealy machine:** by marking the inputs of vertices following operator vertices

**Moore machine:** by marking operator vertices
  
# Controlling register values

```
-- regA_next value is defined by FSM  
process (clk, rst) begin  
  if rst = '0' then  
    regA <= (others => '0');  
  elsif rising_edge(clk) then  
    regA <= regA_next;  
  end if;  
end process;
```




```
-- regA_en and regA_sel values  
-- are defined by FSM  
process (clk, rst) begin  
  if rst = '0' then  
    regA <= (others => '0');  
  elsif rising_edge(clk) then  
    if regA_en = '1' then  
      regA <= regA_next;  
    end if;  
  end if;  
end process;  
  
with regA_sel select  
  regA_next <= <...>
```

# Register Transfer Level

- Register Transfer Level (RTL) is a level of abstraction for digital systems modeling
- Design is formed from a collection of registers linked by combinational logic
- System function is performed as a sequence of register transfers
- Register transfer is the movement and transformation of data between registers


Controlled by FSM

A datapath

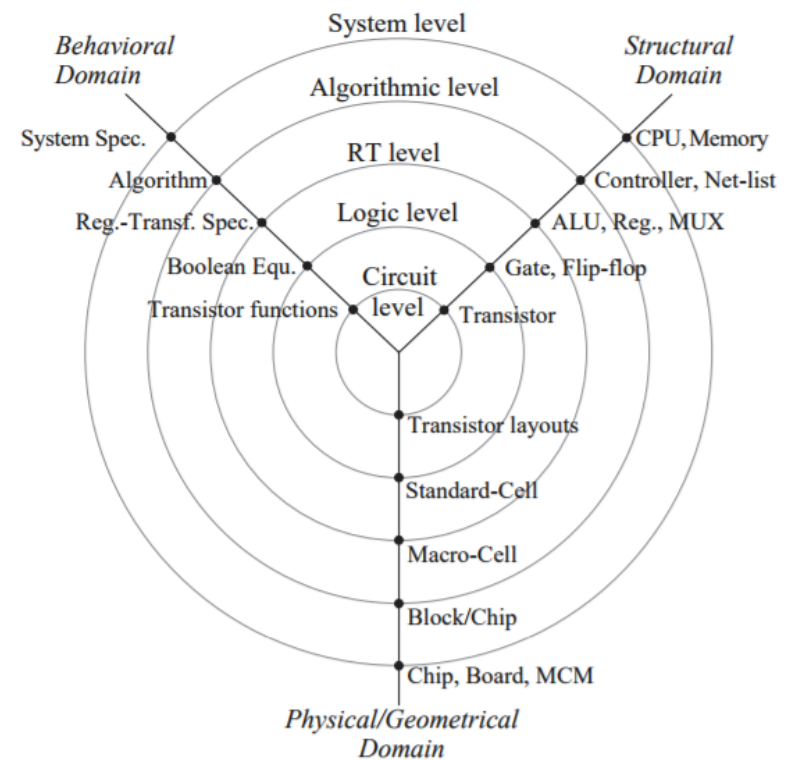


Gajski-Kuhn diagram

# RTL examples – GCD architectures

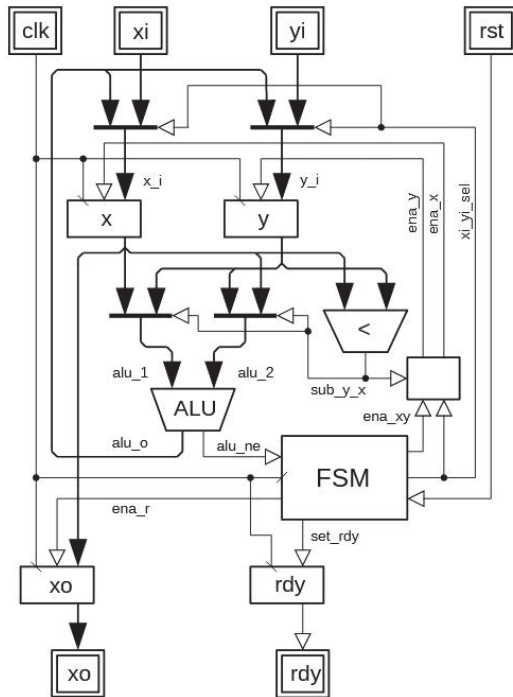

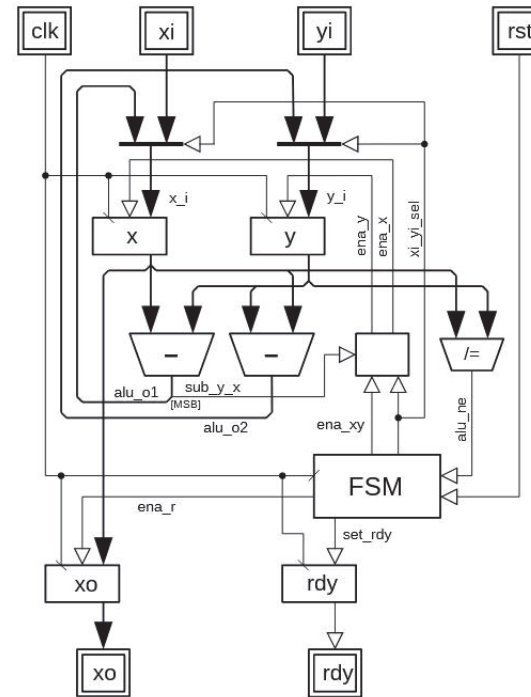Register-transfer level description with comparator controlling subtractions.




Register-transfer level description with out-of-order subtractions. Only data-path differs from RTL #3 & #4.

Code: gcd-rtl3.vhdl

1 ALU ("-", "/="), 1 comparator  
[1 clock step per iteration]

 ASIC: 1134 e.g. / 20.0 ns  
FPGA: 58 SLC / 17.0 ns



Code: gcd-rtl5.vhdl

2 subtractors, 1 comparator  
[1 clock step per iteration]

ASIC: 915 e.g. / 20.0 ns  
FPGA: 58 SLC / 8.0 ns

