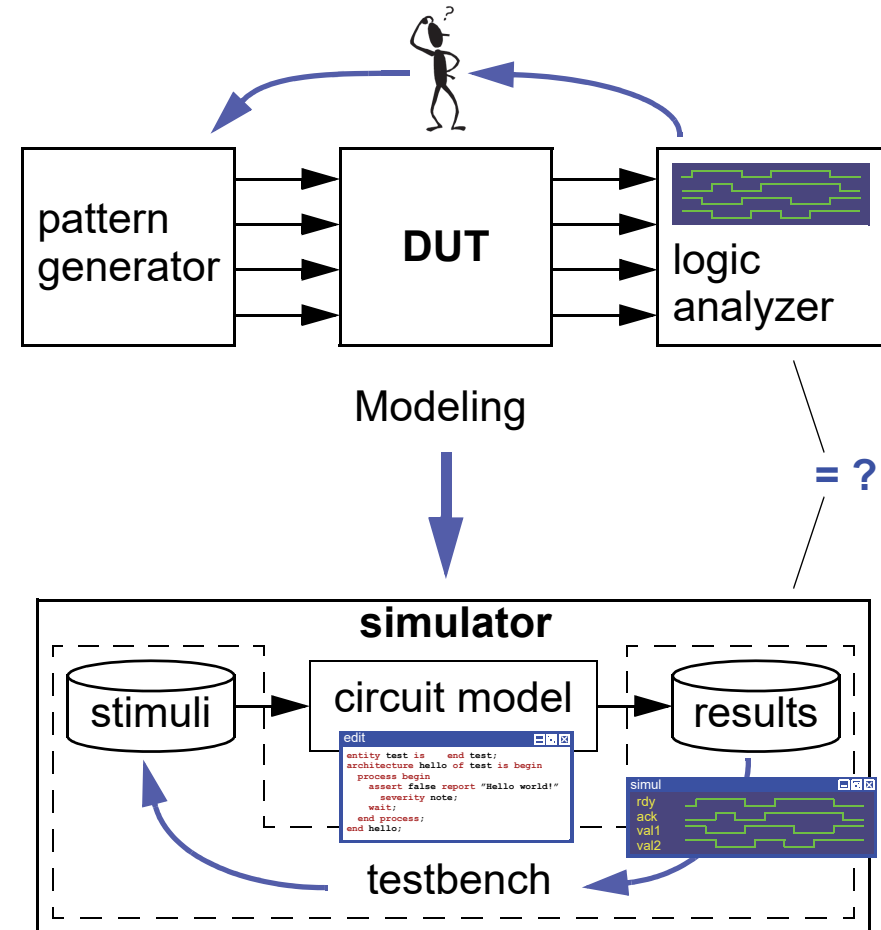


Simulation environment

- **Simulation = modeling + analysis**
- **Environment**
 - **design under test (DUT)**
 - different abstraction levels
 - **stimuli generator**
 - different input-data sequences
 - **results analyzer**
 - is DUT responding correctly?
- **Different combinations exist...**



Use of HDL → Simulation

- **Simulation = modeling + analysis**
 - **Logic / register-transfer / functional (behavioral) / system level simulation**

concurrent / parallel modules


connected via signal / channels

sequential vs. concurrent execution?

execution order?!

current / new values to avoid non-determinism

event queue history+future

 

module / unit / process

continuous execution is slow

only when needed?

time / event triggered

different simulation engines




Simulators & timing/delay models

- **Time & events**
 - *Time-driven*:
all components of the digital logic system are evaluated at every time step
 - *Event-driven*:
system input events are kept in an time-ordered event queue
- **Delay models**
 - unit-delay (RTL simulator)
 - zero-delay (Verilog)
 - *delta*-delay (VHDL) – δ -delay, Δ -delay
- **Simulation engines**
 - all make use of the three following steps but details differ...
 - (1) calculate (and remember) new values for signals
 - (2) update signal values
 - (3) update time





Unit-delay simulation model

 

Unit-delay simulation model (example)

```

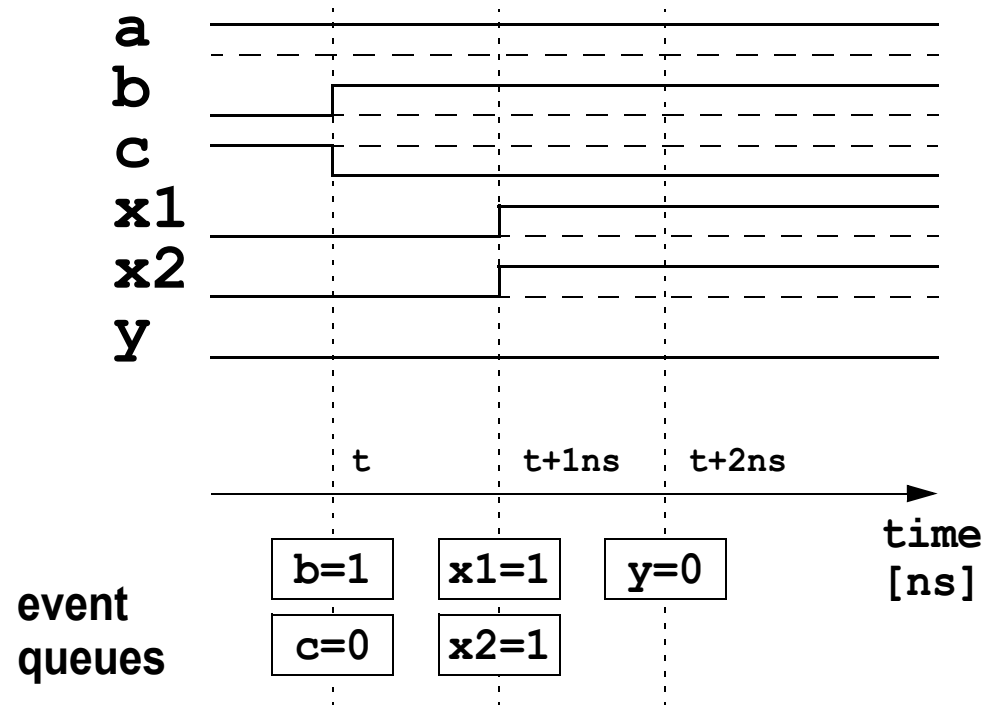 
x1 <= a and b;
x2 <= not c;
y <= x1 xor x2;
  
```



- **Very fast but does not allow immediate signal changes**



Zero-delay simulation model (Verilog)

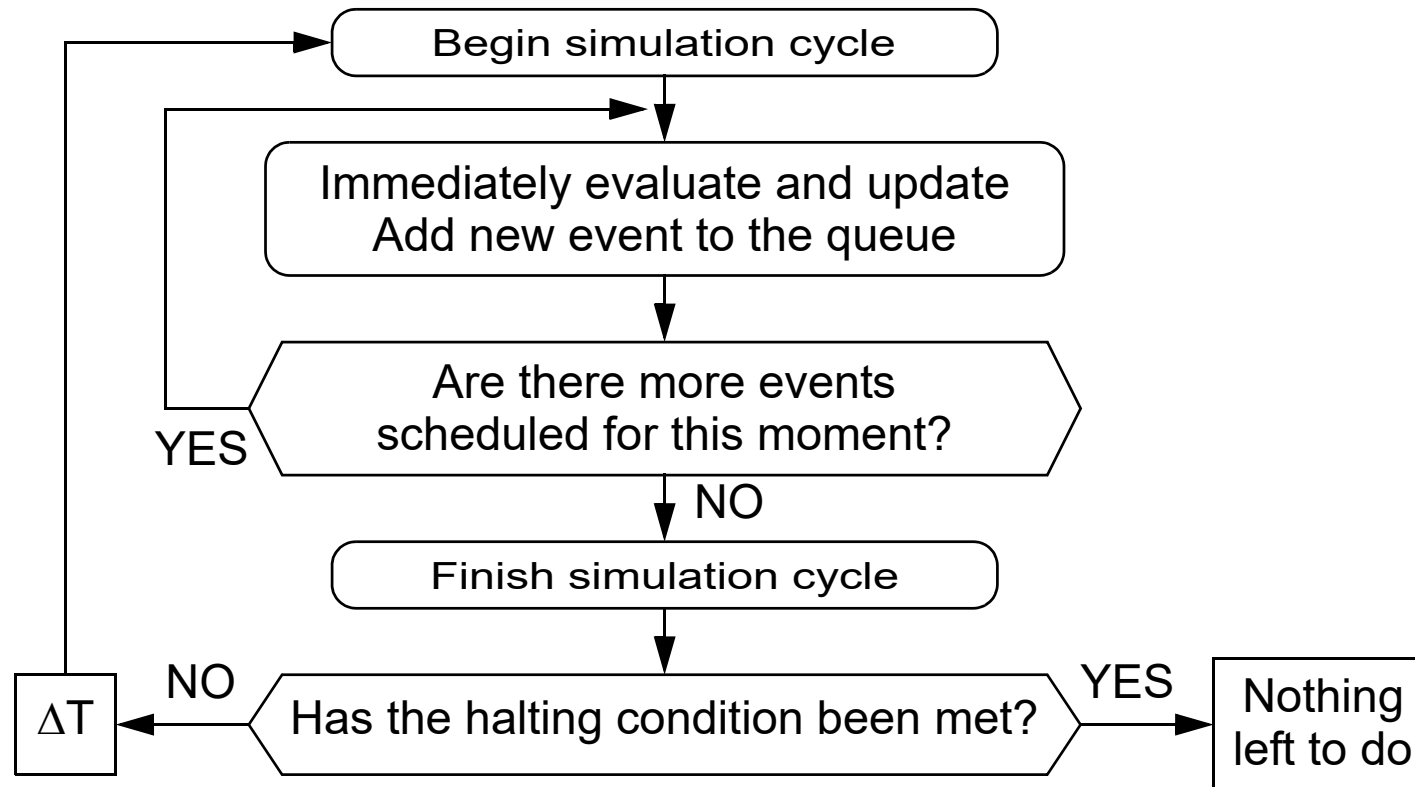





Zero-delay simulation model (example #1)

```

x1 <= a and b;
x2 <= not c;
y <= x1 xor x2;



```

  

Zero-delay simulation model (example #2)

```

 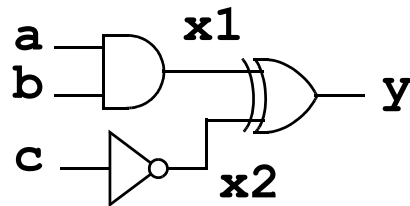x1 <= a and b;
x2 <= not c;
y <= x1 xor x2;
    
```



- Fast and allows immediate signal changes, may suffer from non-determinism



Non-deterministic behavior


```
module anotherVerilogTrick;  
  reg [3:0] w;  
  reg x;  
  initial begin  
    x = 0; w = 0;  
    #100 x = 1; #100;  
  end  
  always @(posedge x) w = 3;  
  always @(posedge x) w = 5;  
endmodule
```

Time	Signal	Value
0	:anotherVerilogTrick.w	0000
100	:anotherVerilogTrick.w	0101
100	:anotherVerilogTrick.x	1

```
module anotherVerilogTrick;  
  reg [3:0] w;  
  reg x;  
  initial begin  
    x = 0; w = 0;  
    #100 x = 1; #100;  
  end  
  always @(posedge x) w = 5;  
  always @(posedge x) w = 3;  
endmodule
```

Time	Signal	Value
0	:anotherVerilogTrick.w	0000
100	:anotherVerilogTrick.w	0011
100	:anotherVerilogTrick.x	1



Delta-delay simulation model (VHDL)

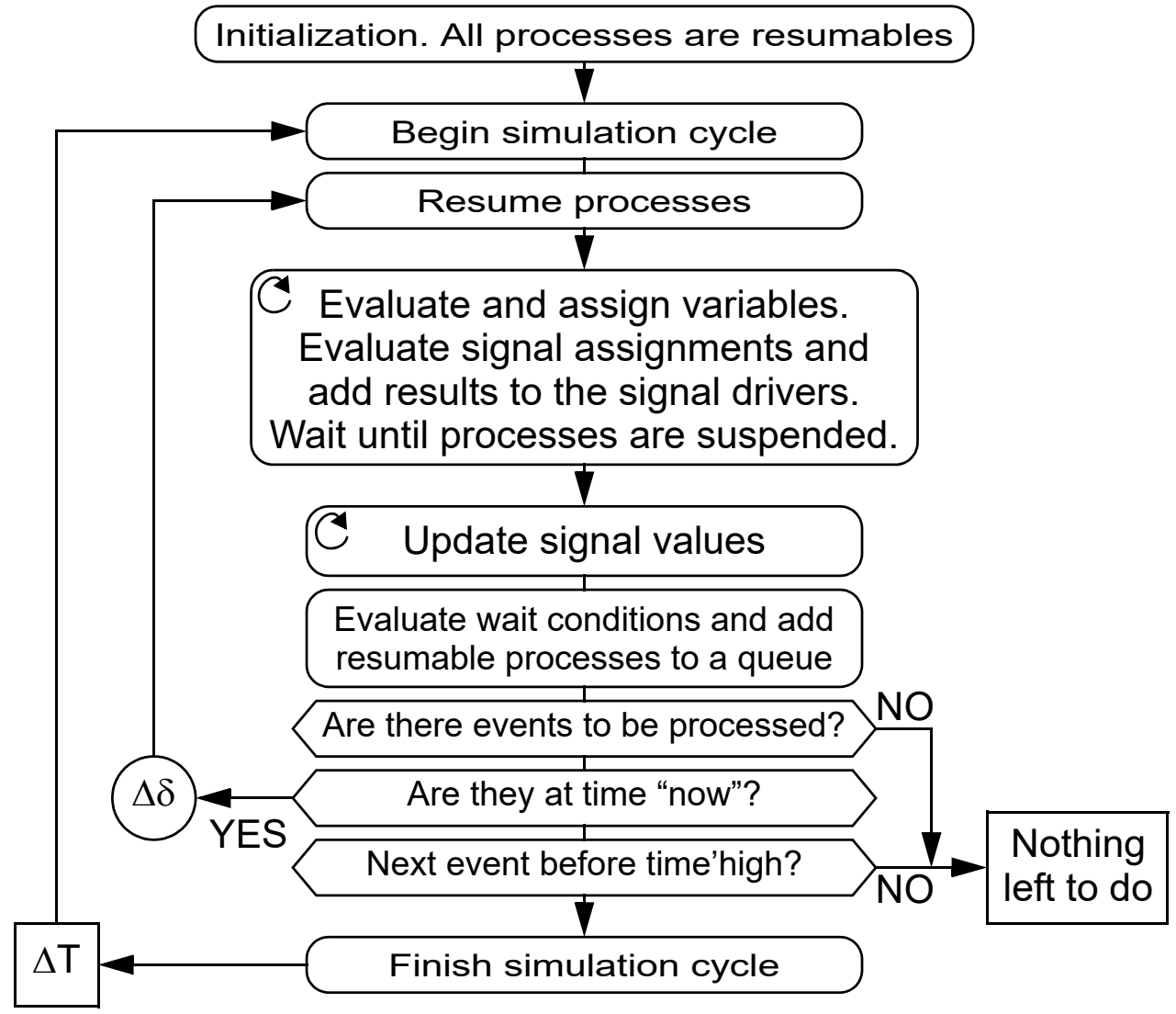

Delta-delay (VHDL) simulation model (example)

```

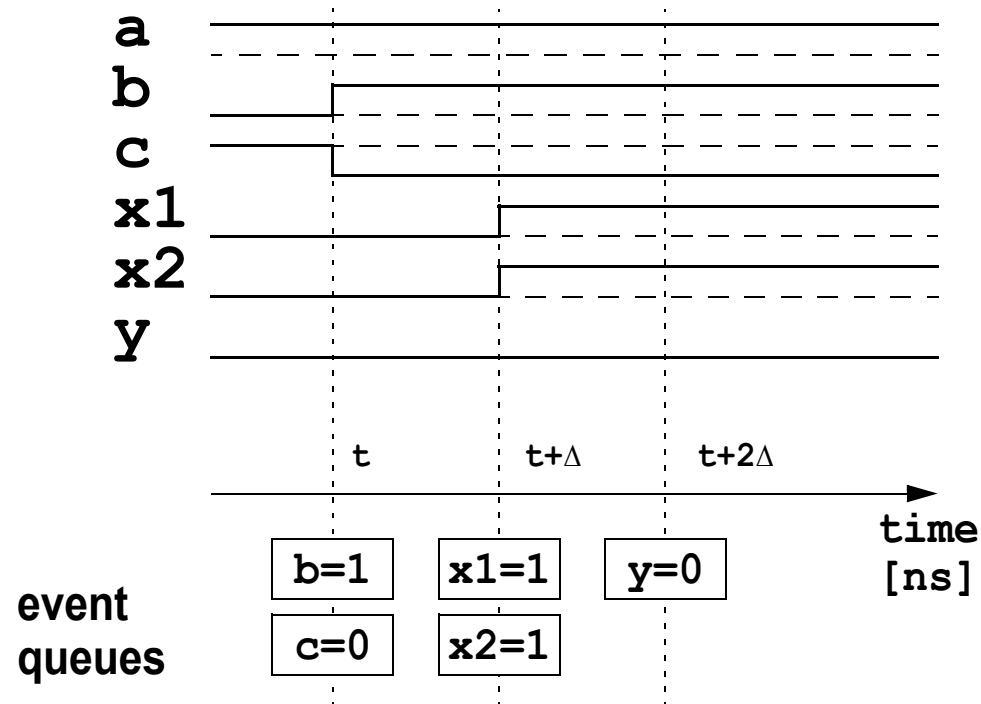 
x1 <= a and b;
x2 <= not c;
y <= x1 xor x2;
  
```



- **Deterministic but slower and may suffer from delta-cycle oscillation**




VHDL simulation scheme

 



VHDL simulation scheme

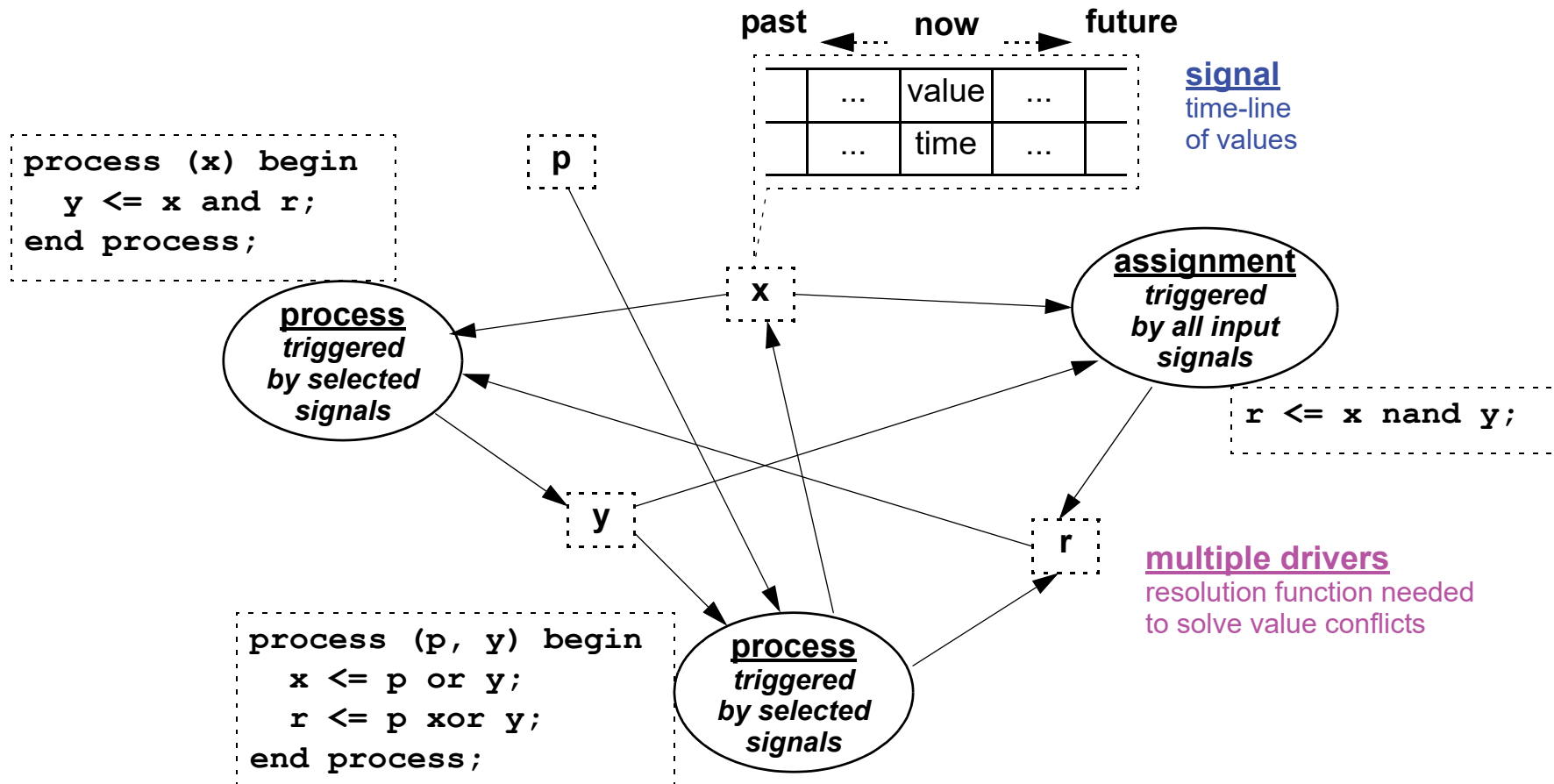



Delta delay example #1

```
-- SR flip-flop  
x <= not (y and lset); -- (1)  
y <= not (x and reset); -- (2)
```

- **Note the different initial values!**

time	lset	x	y	reset	stm.
20 ns	_	0	1	1	(1)
20 ns + 1 Δ	0	_/	1	1	(2)
20 ns + 2 Δ	0	1	_	1	(1)
20 ns + 3 Δ	0	1	0	1	-
30 ns	_/	1	0	1	(1)
30 ns + 1 Δ	1	1	0	1	-
40 ns	1	1	0	_	(2)
40 ns + 1 Δ	1	1	_/	0	(1)
40 ns + 2 Δ	1	_	1	0	(2)
40 ns + 3 Δ	1	0	1	0	-



Delta delay example #2

```
-- SR flip-flop + delays
x <= not (y and lset)
    after 2 ns;           -- (1)
y <= not (x and reset)
    after 2 ns;         -- (2)
```

- **Note the different initial values!**

time	lset	x	y	reset	stm.
20 ns	_	0	1	1	(1)
22 ns	0	_/	1	1	(2)
24 ns	0	1	_	1	(1)
24 ns + 1 Δ	0	1	0	1	-
30 ns	_/	1	0	1	(1)
30 ns + 1 Δ	1	1	0	1	-
40 ns	1	1	0	_	(2)
42 ns	1	1	_/	0	(1)
44 ns	1	_	1	0	(2)
44 ns + 1 Δ	1	0	1	0	-



Delta delay example #3

- Dangers of default initialization**

```
-- SR flip-flop & oscillation
x <= not (y and lset); -- (1)
y <= not (x and reset); -- (2)
```

- Equal initial values will result in oscillation even with after clause!**

time	lset	x	y	reset	stm.
0 ns	_/	_	_	_/	(1),(2)
0 ns + 1 Δ	1	_/	_/	1	(1),(2)
0 ns + 2 Δ	1	_	_	1	(1),(2)
0 ns + 3 Δ	1	_/	_/	1	(1),(2)
etc.	1	1	(1),(2)
0 ns	_/	_/	_/	_/	(1),(2)
0 ns + 1 Δ	1	_	_	1	(1),(2)
0 ns + 2 Δ	1	_/	_/	1	(1),(2)
0 ns + 3 Δ	1	_	_	1	(1),(2)
etc.	1	1	(1),(2)