

Digitaalsüsteemide modelleerimine – motivatsioon

- Erinevad abstraktsiooni-tasemed


- Sama keel kõikidel projekteerimisetappidel
 - ... või vähemalt enamikel projekteerimisetappidel
- Sama mooduli erinevate kirjelduste võrreldavus
- Simuleerimine erinevatel kirjeldustasemetel

- Dokumenteerimine

- Modelleeritav spetsifikatsioon
 - “isedokumenteeriv mudel”

- Süntees

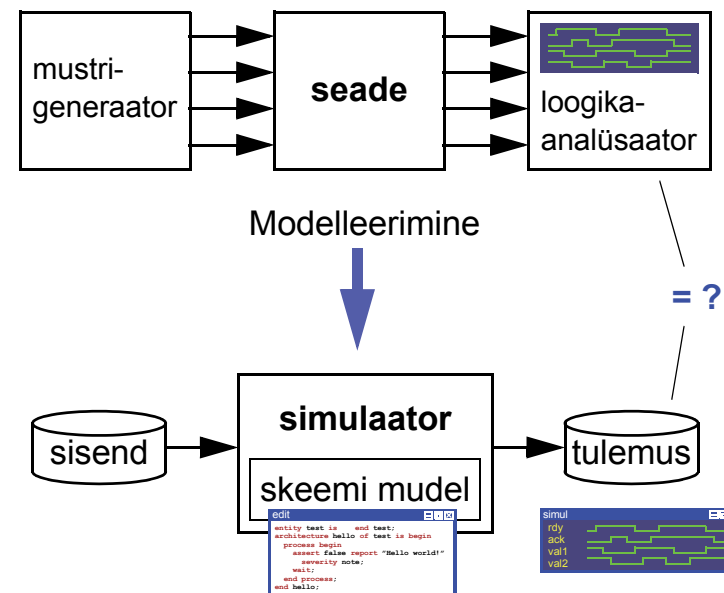- Lähtekirjedus kõrgel abstraktsioonitasemel
- Formaliseeritav teisendus kõrgemalt abstraktsioonitasemelt madalamale
- Automatiseeritavus
- Verifitseeritavus, st. formaalne erinevate kirjeldustasemete võrdlus
- Valideeritavus, st. käitumuslik erinevate kirjeldustasemete võrdlus





HDL – Hardware Description Language

- **Riistvara kirjelduskeel**
 - **Tükeldamine**
 - **struktuurne hierarhia**
 - **Funktsionaalsuse kapseldatavus**
 - **funktsionaalne hierahia**
 - **Andmete kapseldatavus**
 - **abstaktsed andmetüübid**
 - **Paralleelsus / Sama-aegsus**
- **VHDL – VHSIC Hardware Description Language**
 - **VHSIC – Very High Speed Integrated Circuit**
 - **1981 juuni – ajurünnak Massachusettsis (riik, DoD, akadeemia)**
 - **1986 – IEEE alustas standardiseerimist. IEEE-1076 (VHDL'87)**
 - **1994 – versioon VHDL'93 (IEEE 1076-1993), täiendused**
 - **1999 – VHDL-AMS (IEEE 1076.1-1999), analoog- ja segasignaalid**
 - **2002 – VHDL'2000 (IEEE 1076-2002), vigade parandused ja täpsustused**
 - **2009 – VHDL 4.0 (IEEE 1076-2008), parendatud sünteesitavus, arendus jätkub...**



VHDL kirjandus


- **Peter J. Ashenden, “The Student's Guide to VHDL” & “The Designer's Guide to VHDL.”**
- **Michael John Sebastian Smith, “Application-Specific Integrated Circuits.”**
 - <http://www10.edacafe.com/book/ASIC/ASICs.php> vt. peatükk 10
- **Dirk Jansen et al. (editors), “The electronic design automation handbook.”**
- **Kalle Tammemäe, “Riistvara kirjeldamiskeel VHDL.”**
- **IAY0340 “Digitaalsüsteemide modelleerimine ja süntees”**
 - <http://mini.pld.ttu.ee/~lrv/IAY0340/>
 - **lisakirjandus & simulaatorid**
 - http://www.mentor.com/company/higher_ed/modelsim-student-edition
 - <http://www.xilinx.com/products/design-tools/ise-design-suite/ise-webpack.htm>
 - <http://zamiacad.sourceforge.net/web/>
 - <http://ghdl.free.fr/> & <http://sourceforge.net/projects/gtkwave/>

Riistvara disain tänapäeval

- **Mudel VHDL-s**


```
--
-- Highway is green, sidestreet is red.
--
if sidestreet_car = NoCar then
  wait until sidestreet_car = Car;
end if;
-- Waiting for no more than 25 seconds ...
if highway_car = Car then
  wait until highway_car = NoCar for 25 sec;
end if;
-- ... and changing lights
highway_light <= GreenBlink;
wait for 3 sec;
highway_light <= Yellow;
sidestreet_light <= Yellow;
wait for 2 sec;
highway_light <= Red;
sidestreet_light <= Green;
```

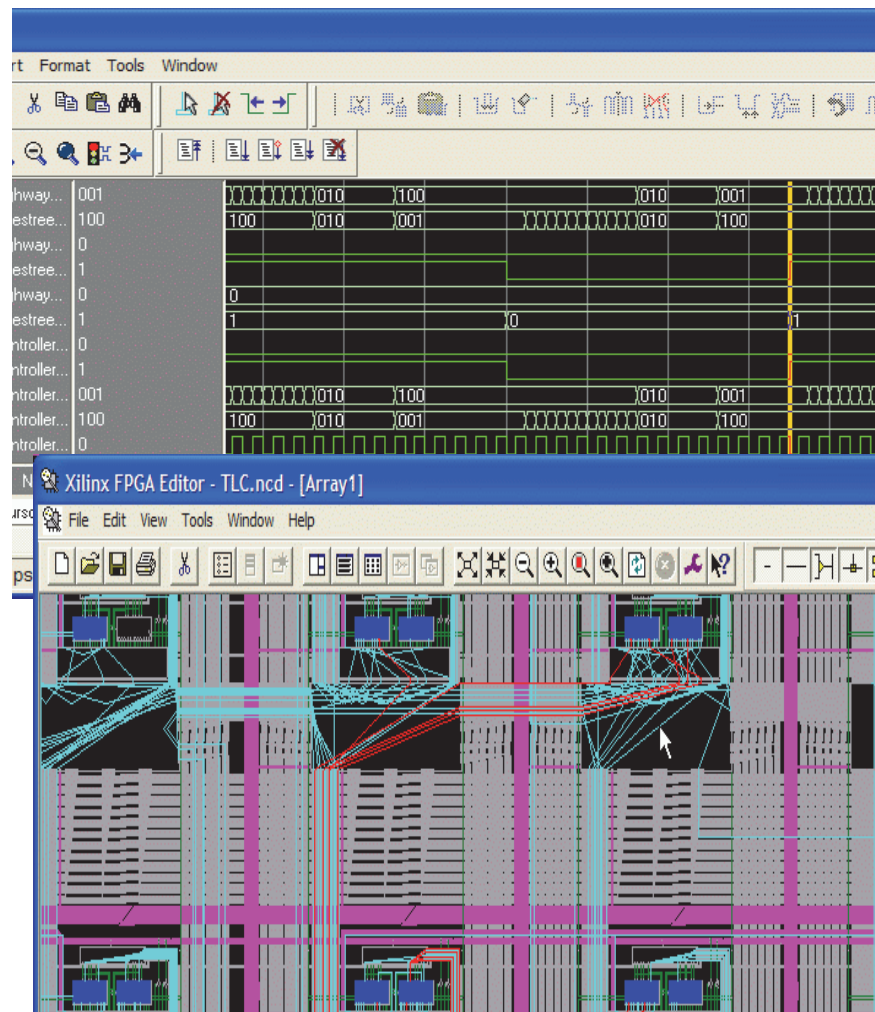- **Samm-sammuline täiendamine**
- **Süntees FPGA-le**




Prototüüpimine

 - Võimalus kontrollida süsteemi tööd realsusele lähedastes tingimustes ilma vajaduseta luua ülikallist spetsialiseeritud mikroskeemi



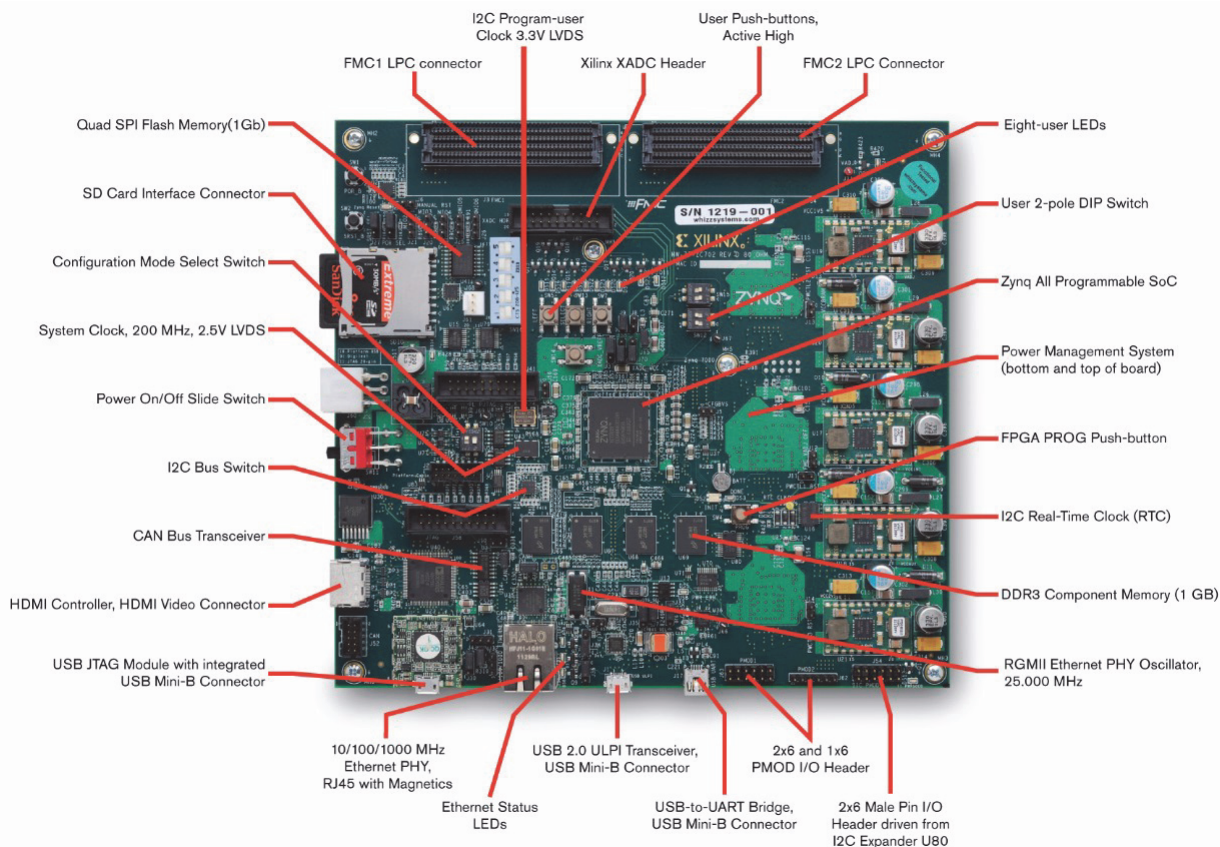
XESS Corp., XuLA-200
 www.xess.com, \$55
 [Xilinx Inc., FPGA XC3S200A]



Xilinx Inc., Zynq-7000 SoC Eval.Kit, XC7Z020, \$895

VHDL-i põhielemendid

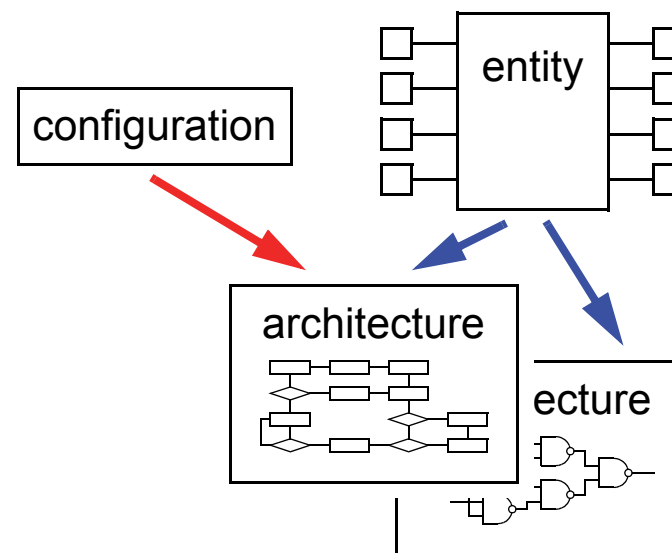- **entity (olem)**
 - liidese kirjeldus
- **architecture (arhitektuur)**
 - käitumise/struktuuri kirjeldus
- **configuration (konfiguratsioon)**
 - kirjelduse (abstr.taseme) määramine
- **package (paketid)**
 - andmetüübid jne.




```

entity test is      end test;
architecture hello of test is begin
  process begin
    assert false report "Hello world!" severity note;
    wait;
  end process;
end hello;
  
```

Funktsiooni esitamine – näide ja stiilid

- $f1 = \overline{(b \oplus c)} + a b \bar{c}$
`f1 <= (not (b xor c)) or (a and b and (not c));`
- $f2 = b(a + c) + \bar{b}\bar{c}$
`f2 <= (b and (a or c)) or ((not b) and (not c));`
- $f3 = (b + \bar{c})(a + \bar{b} + c)$
`f3 <= (b or (not c)) and (a or (not b) or c);`
- f4 – skeem**
`f4 <= t1 or t2; t1 <= ci and a and b;`
`t2 <= not t3; t3 <= b xor c; ci <= not c;`
- f0 – tõeväärtustabeli kirjeldus**
 
```
process (a, b, c) begin
  f0 <= '0';
  if a='0' then
    if b=c then f0 <= '1'; end if;
  else
    if b='1' or c='0' then f0 <= '1'; end if;
  end if;
end process;
```




abc	f0
000	1
001	0
010	0
011	1
100	1
101	0
110	1
111	1





Kontroll ehk simuleerimine

```
entity example is
end entity example;
architecture allinone of example is
    signal a, b, c, f0, f1, f2, f3: bit;
    signal f4, t1, t2, t3, ci: bit;
begin
    a <= '0', '1' after 40 ns;
    b <= '0', '1' after 20 ns, '0' after 40 ns, '1' after 60 ns;
    c <= '0', '1' after 10 ns, '0' after 20 ns, '1' after 30 ns,
        '0' after 40 ns, '1' after 50 ns, '0' after 60 ns, '1' after 70 ns;
    f1 <= (not (b xor c)) or (a and b and (not c));
    f2 <= (b and (a or c)) or ((not b) and (not c));
    f3 <= (b or (not c)) and (a or (not b) or c);
    f4 <= t1 or t2; t1 <= ci and a and b; t2 <= not t3;
    t3 <= b xor c; ci <= not c;
    process (a, b, c) begin
        f0 <= '0';
        if a='0' then
            if b=c then f0 <= '1'; end if;
        else
            if b='1' or c='0' then f0 <= '1'; end if;
        end if;
    end process;
end architecture allinone;
```

 

Multiplexer

  - $o = \bar{a} i_0 + a i_1$
- De Morgan'i seadus
 - $\bar{a} \& \bar{b} = \overline{a + b}$ $\bar{a} + \bar{b} = \overline{a \& b}$
 - $a' \& b' = (a + b)'$ $a' + b' = (a \& b)'$
- $o = ((a' \& i_0)' \& (a \& i_1)')'$






Multiplekser

olem
 
```
entity MUX is
  port ( a, i0, i1 : in bit;
         o : out bit );
end MUX;
```



käitumuslik

```
architecture behave of MUX is
begin
  process ( a, i0, i1 ) begin
    if a = '1' then
      o <= i1;
    else
      o <= i0;
    end if;
  end process;
end behave;
```


- $$o = \bar{a} i_0 + a i_1$$

Multiplexser

andmevoog

```
architecture dataflow of MUX is
begin
  o <= ( (not a) and i0 ) or
        ( a and i1 );
end dataflow;
```

- $o = \bar{a} i_0 + a i_1$

 

structuur

```
architecture struct of MUX is
  component NANDg
    port ( i0, i1 : in bit;
           c : out bit );
  end component;
  signal na, s1, s0 : bit;
begin
  U1: NANDg port map (a, a, na);
  U2: NANDg port map (i1, a, s1);
  U3: NANDg port map (i0, na, s0);
  U4: NANDg port map (s1, s0, o);
end struct;
```



Andmete esitamine

- **Neli objektide klassi:**
 - konstant (constant) – fikseeritud väärtus
 - signaal (signal) – väärtustel on ajalugu (sündmused)
 - muutuja (variable) – ainult jooksev väärtus
 - fail (file) – simuleeriva arvuti failisüsteemi objekt
- **Tüüp (type)**
 - esitab objekti struktuuri, ülesehitust ja mäluvajadust
- **Klass kirjeldab objekti käitumist ja kuidas objekti mudelis kasutatakse**
 - jooksva väärtuse lugemine
 - uue väärtuse omistamine
- **Indentifikaatorid**
 - “INTGR9”, “intgl_5” – legaalne
 - “Intgrl-5”, “Acquire_”, “8to3”, “Abc@adr” – illegaalne
- **Literaaliid**
 - arvud – 12 1.34E-12 8#1470_0220#
 - sümbolid/stringid – 'A' "string"
 - bitid/vektorid – '0' "1101" X"FFF"



Eraldajad

	Name	Example
&	jätkaja (konkatenaator)	FourB_v := TwoB_v & "10"
	"või"	when 'Y' 'y' =>
#	baasiga literaalid	Total_v := 16#2AF#
:	andmeobj. eraldaja	variable Sw_v : OnOff_Typ;
.	kirje element	OnOff_v := Message_v.Switch_v;
=>	"siis"	when On1 => Sun_v := 6;
=>	"saab"	Arr_v := (E11 => 5, others => 100);
:=	muutujale omistamine	Sum_v := Numb_s +7;
<=	signaalile omistamine	Count_s <= 5 after 5 ns;
<>	"määramata"	type S_Typ is array (integer range <>) ...
--	kommentaar	-- this is definitely a comment;



Operaatorid

- **loogika:** *and, or, nand, nor, xor* (VHDL'87) *xnor* (VHDL'93)
 - **võrdlus:** =, /=, <, >, <=, >=
 - **nihutamine:** sll, srl, sla, sra, rol, ror (VHDL'93)
 - **liitmine:** +, -, &
 - **märk:** +, -
 - **korrutamine:** *, /, mod, rem
 - **varia:** **, abs, not
-
- **Näited**
 - **&** : jätkamine, '1' & "10" = "110"
 - ****** : astendamine, 2**3 = 8
 - **mod** : moodul, 7 mod (-2) = -1 – $A=B*N+(A \text{ mod } B)$
 - **rem** : jääk, 7 rem (-2) = 1 – $A=(A/B)*B+(A \text{ rem } B)$



Avaldised & käsud

- **Omistamine**
 - **signaalile** – `s <= [transport | inertial] expression [after time] ;`
 - **muutujale** – `v := expression;`
 - **avaldis** – `expression operation expression`
variable | signal
function-call
- **Kontrollvoo käsud (järjestikulised)**
 - **signaalile/muutujale omistamine**
 - **tingimuslikud** – if-then-else, case
 - **tsüklid** – for-loop, while-loop
 - **protseduuri välja kutsumine**
 - **ajakontroll (wait); muud käsud (nt. assert)**
- **Andmevoo käsud (sama-aegsed)**
 - **signaalile omistamine**
 - **tingimuslikud** – when-else
 - **sama-aegse protseduuri välja kutsumine**
 - **komponentide sidumine; muud käsud (nt. assert, generate)**



Tüübid

- Skalaartüüp – diskreetne (integer, enumeration, physical) või reaaltüüp
- Komposiit-tüüp – massiivid ja kirjed
- Pöördustüüp (access) & failitüüp – (ainult simuleerimine)
- **Alamtüübi (*subtype*) korral seatakse andmetüübile täiendavaid piiranguid**
 - piirangutest kinni pidamist kontrollitakse simuleerimise käigus
 - Näited:
 - `type Bit_position is range 7 downto 0;` -- uus tüüp
 - `subtype Int0_5_Typ is integer range 0 to 5;` -- alamtüüp
 - `type Color is (Green, Yellow, Red);` -- loendustüüp (enumeration)



Pakett STANDARD

```
package STANDARD is
  type BOOLEAN is (FALSE, TRUE);
  type BIT is ('0', '1');
  type CHARACTER is (NUL, SOH, ..., 'a', 'b', 'c', ..., DEL);
  type SEVERITY_LEVEL is (NOTE, WARNING, ERROR, FAILURE);
  type INTEGER is range -(2**31-1) to (2**31-1);
  type REAL is range ...;
  type TIME is range ...
    units fs; ps=1000 fs; ... hr=60 min; end units;
  function NOW return TIME;
  subtype NATURAL is INTEGER range 0 to INTEGER'HIGH;
  subtype POSITIVE is INTEGER range 1 to INTEGER'HIGH;
  type STRING is array (POSITIVE range <>) of CHARACTER;
  type BIT_VECTOR is array (NATURAL range <>) of BIT;
end STANDARD;
```



Tüübiteisendus

- VHDL on range tüüpimisega
 - teisendused on vajalikud eri tüüpide vahel

```

use IEEE.std_logic_1164.all;      -- for std_logic_vector
use IEEE.std_logic_arith.all;    -- for signed and unsigned
...
signal k: std_logic_vector(7 downto 0) := "11110000";
signal a, b: signed(7 downto 0);
signal c: unsigned(15 downto 0);
...
a <= conv_signed(100,8);          -- conversion function
c <= conv_unsigned(65535,16);    -- conversion function
b <= signed' ("00001111");      -- type casting
a <= a + signed'(k);            -- type casting

```



Arhitektuur

- **Arhitektuur (architecture) – deklaratsioonid ja tegevused**
 - **Protsessid (process) ja andmevoo käsud (concurrent signal assignment)**
 - **Alamkomponentide paigaldus (component instantiation)**
 - **Muud sama-aegselt täidetavad käsud**
 - concurrent procedure, generate, concurrent assertion, block
- **Protsess (process) – deklaratsioonid ja mudeli käitumine**
 - peab sisaldama aja kontrolli – tundlikkuse nimistu või ootekäsud
- **Ekvivalentsed käitumised**
 - andmevoo käsk
`x <= a and b after 5 ns;`
 - protsess & tundlikkuse nimistu
`process (a, b) begin`
`x <= a and b after 5 ns;`
`end process;`
 - protsess & ootekäsk
`process begin`
`wait on a, b;`
`x <= a and b after 5 ns;`
`end process;`



Ajakontroll

- Signaalile omistamise edasi lükkamine – “... after T;”
- Tundlikkuse nimistu
- Ootekäsud (wait)
 - oota signaali sündmust – `wait on x;`
 - oota tingimuse täitumist – `wait until x='1';`
 - oota kindel ajavahemik – `wait for 20 us;`
 - oota (igavesti) – `wait;`
 - kombineeritud kasutamine – `wait on clk until clk='1' and ready='1' for 1 us;`
- ootekäskude tundlikkus
 - `wait on a until a='1' and b='0';` – tundlik muutustele ainult signaalil *a*
 - `wait until a='1' and b='0';` – tundlik muutustele signaalidel *a* ja *b*



Tingimuslikud käsud

- **if-then-else**

```
[label:] if conditional-expression then statements...
elsif conditional-expression then statements...
else statements...
end if [label];
```

- *conditional-expression* – avaldis, mis tagastab loogikaväärtuse (boolean)

- **case**

```
[label:] case expression is
when constant-value [| constant-value] => statements...
when others => null
end case [label];
```



Tsüklid

```
[label:] [iteration-method] loop
  statements...
end loop [label];
```

```
iteration-method ::=
  while conditional-expression | for counter in range
```

```
exit [label] [when conditional-expression];
next [label] [when conditional-expression];
```

```
range ::= expression to expression |
           expression downto expression |
           type'range | ...
```



Tsükliid – näide

- **for-loop**

```
for I in my_array'range loop
  next when I<lower_limit;
  exit when I>upper_limit;
  sum := sum + my_array(I);
end loop;
```
- **while-loop**

```
while a<10 loop
  a := a + 1;
end loop;
```



Käitumuslik hierarhia

- **Funktsioonid ja protseduurid**
 - **function**
 - kasutatakse ainult avaldisena
 - ei tohi sisaldada ajakontrolli käske
 - ainult sisendparameetrid (sisuliselt konstandid)
 - operaatorite defineerimine
 - **procedure**
 - kasutatakse käsuna
 - võib sisaldada ajakontrolli käske
 - sisend- (konstandid) ja väljundparameetrid (muutujad/signaalid)

```
function "and" (l,r: signed) return signed is begin
    return signed(std_logic_vector(l) and std_logic_vector(r));
end;
-- ...
x <= a and b;
-- ...
```




Käitumuslik hierarhia – protseduurid

```
PACKAGE adder elements IS
-- full_adder: 1-bit full adder (declaration)
PROCEDURE full_adder (
  CONSTANT a0, b0, c0: IN bit;
  VARIABLE o0, c1: OUT bit);
END adder_elements;
```

```
PACKAGE BODY adder elements IS
PROCEDURE half_adder (
  CONSTANT a0, b0: IN bit;
  VARIABLE o0, c1: OUT bit)
IS
BEGIN
  o0 := a0 XOR b0;
  c1 := a0 AND b0;
END half_adder;

-- full_adder: 1-bit full adder
-- (body, i.e. implementation)
PROCEDURE full_adder (
  CONSTANT a0, b0, c0: IN bit;
  VARIABLE o0, c1: OUT bit)
IS
  VARIABLE c_1, c_2, o_1: bit;
BEGIN
  half_adder ( a0, b0, o_1, c_1 );
  half_adder ( o_1, c0, o0, c_2 );
  c1 := c_1 or c_2;
END full_adder;
END adder_elements;
```

```
PACKAGE BODY adder elements IS
-- full_adder: 1-bit full adder
-- (body, i.e. implementation)
PROCEDURE full_adder (
  CONSTANT a0, b0, c0: IN bit;
  VARIABLE o0, c1: OUT bit)
IS
  -- Defining a 3-D array (hyper-cube)
  TYPE look_up_1 IS ARRAY (bit) OF bit;
  TYPE look_up_2 IS ARRAY (bit) OF look_up_1;
  TYPE look_up_3 IS ARRAY (bit) OF look_up_2;
  CONSTANT output: look_up_3 :=
  -- -----
  -- | 0 1 0 1 | a0 / |
  -- | 0 0 1 1 | b0 / c0 |
  -- -----
  ( ( ( '0', '1' ), ( '1', '0' ) ), -- | 0 |
    ( ( '1', '0' ), ( '0', '1' ) ) ); -- | 1 |
  CONSTANT carry: look_up_3 :=
  -- -----
  -- | 0 1 0 1 | a0 / |
  -- | 0 0 1 1 | b0 / c0 |
  -- -----
  ( ( ( '0', '0' ), ( '0', '1' ) ), -- | 0 |
    ( ( '0', '1' ), ( '1', '1' ) ) ); -- | 1 |
BEGIN
  o0 := output (a0) (b0) (c0);
  c1 := carry (a0) (b0) (c0);
END full_adder;
END adder_elements;
```



Atribuudid

```

-- type myArray is array (9 downto 0) of any_type;
-- variable an_array: myArray;
-- type fourval is ('0', '1', 'Z', 'X');
-- signal sig: sigtype;
-- constant T: time := 10 ns;

```

Atribuut	Tüüp	Tulemus
myArray'high left low right	integer	9 9 0 0
myArray'ascending	boolean	false
an_array'length range reverse_range	integer	10 9 downto 0 0 to 9
fourval'leftof('0') rightof('1')	fourval	error 'Z'
fourval'pos('Z')	integer	2
fourval'pred('1') succ('Z') val(3)	fourval	'0' 'X' 'X'
sig'delayed(T)	sigtype	sig-i 10 ns hilistatud väärtus
sig'event	boolean	tõene kui sig-l on sündmus
sig'last_event	time	aeg eelmisest sündmusest
sig'last_value	sigtype	väärtus enne viimast sündmust
sig'stable(T)	boolean	sündmus (now-T)-st kuni now-ni
...



Atribuutide kasutamine

- **Fikseeritud kood**

```
signal s: bit_vector (7 downto 0);  
...  
for i in 0 to 7 loop ...
```

- **Paindlikum kood**

```
constant sz: integer := 16;  
signal s: bit_vector (sz-1 downto 0);  
...  
for i in 0 to sz-1 loop ...
```

- **Kõige paindlikum kood (atribuudid ja üldistatud parameeter)**


```
entity ... is  
  generic (sz: positive);  
  port ...  
  ...  
  signal s: bit_vector (sz-1 downto 0);  
  ...  
  for i in s'low to s'high loop ...  
  for i in s'reverse_range loop ...
```

Atribuutide kasutamine – #2

- **Seade- & hoide-ajad mäluelementides (trigerites)**
 - seadeaeg (setup time) – sisend peab olema stabiilne mingi aeg enne taktsignaali aktiivset fronti
 - hoideaeg (hold time) – sisend peab olema stabiilne mingi aeg pärast taktsignaali aktiivset fronti
- Põhjuseks signaalide levimine eri teid pidi mäluelemendi sees
- Tagajärjeks võib olla metastabiilsus – väljundi '0' ja '1' vahel

```

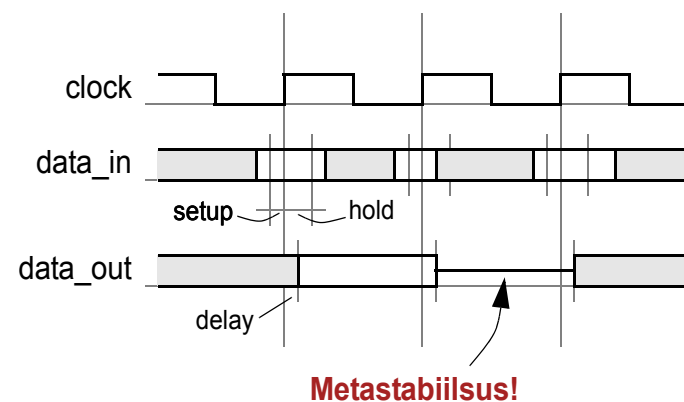process (clock,data_in) begin
  if clock'event and clock='1' then
    assert data_in'last_event >= 3 ns
      report "setup time violation" severity warning;
    data_out <= data_in after 3 ns;
  end if;
  if data_in'event and clock='1' then
    assert clock'last_event >= 5 ns
      report "hold time violation" severity warning;
  end if;
end process;
  
```





Struktuurne hierarhia

- Paketid, teegid
- Komponentid, konfiguratsioonid

Mäluelemendid

- Protsess, mis peab meeles (osade) signaalide/muutujate väärtuseid
- Protsessi peatamine kindlaks ajaks


```
process begin
    wait on CLK until CLK='1';
    Q1 <= D1;
end process;

process (CLK) begin
    if CLK='1' and CLK'event then
        Q2 <= D2;
    end if;
end process;
```


```
process (CLK) begin
    if CLK='1' and CLK'event then
        if RES='1' then
            Q3 <= '0';
        elsif ENA='1' then
            Q3 <= D3;
        end if;
    end if;
end process;
```

Näide #2 – LFSR
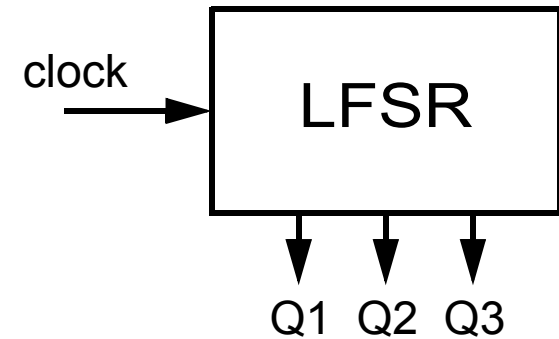
```
entity LFSR is
  port ( clock : in bit;
        Q1,Q2,Q3 : out bit );
end LFSR;
```



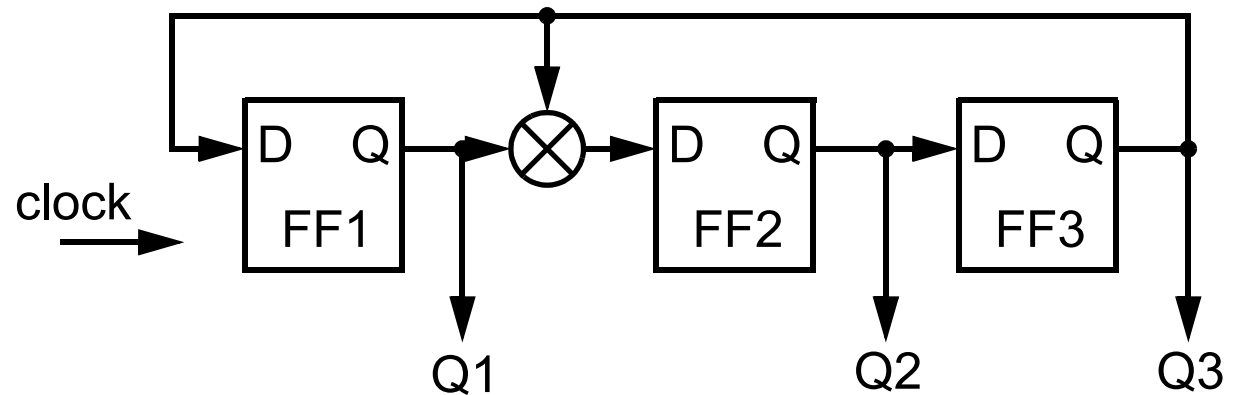- $Q3 := Q2 \parallel$
 $Q2 := Q1 + Q3 \parallel$
 $Q1 := Q3$





LFSR – käitumuslik kirjeldus

architecture behavior of LFSR is

```

begin
  process
    variable Olek: bit_vector(3 downto 0) := "0111";
  begin
    Q3 <= Olek(2) after 5 ns;
    Q2 <= Olek(1) after 5 ns;
    Q1 <= Olek(0) after 5 ns;
    wait on clock until clock = '1';
    Olek := Olek(2 downto 0) & '0';
    if Olek(3) = '1'
      then Olek := Olek xor "1011";
    end if;
  end process;
end behavior;

```



LFSR – andmevoo kirjeldus

architecture dataflow of LFSR is

```
    signal FF1, FF2, FF3 : bit := '1';  
begin  
b1: block (clock = '1' and not clock'stable)  
    begin  
        FF3 <= guarded FF2 after 5 ns;  
        FF2 <= guarded FF1 xor FF3 after 5 ns;  
        FF1 <= guarded FF3 after 5 ns;  
    end block;  
    Q3 <= FF3;  
    Q2 <= FF2;  
    Q1 <= FF1;  
end dataflow;
```




LFSR – struktuurne kirjeldus

architecture structure of LFSR is


```
signal xor_out : bit;
signal SR1, SR2, SR3 : bit := '1';
component FF
    port ( clock, data : in bit; Q out bit );
end component;
component XORgate
    port ( a, b : in bit; x : out bit );
end component;
begin
    FF1: FF port map ( clock, SR3, SR1 );
    FF2: FF port map ( clock, xor_out, SR2 );
    FF3: FF port map ( clock, SR2, SR3 );
    xor1: XORgate port map ( SR1, SR3, xor_out );
    Q3 <= SR3;    Q2 <= SR2;    Q1<= SR1;
end structure;
```



LFSR – testpink

- **stiimul-signaali generaator → testitav moodul → tulemuste analüüs**

```
entity LFSRstim is
end LFSRstim;
```

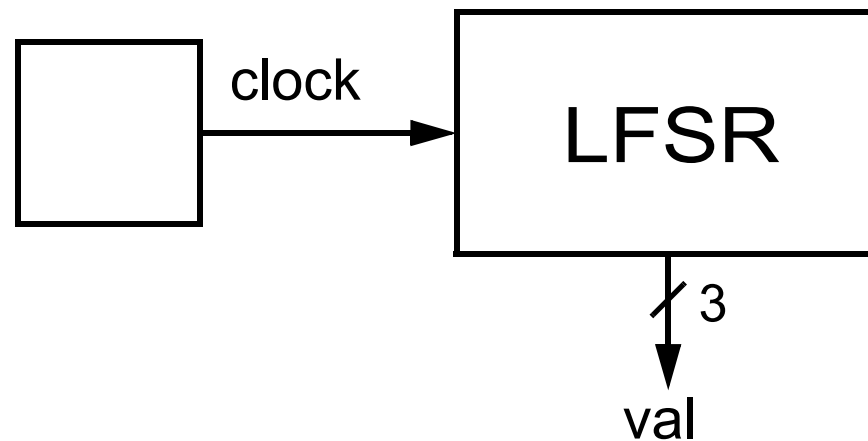




LFSR – testpink

architecture test of LFSRstim is

```
    component LFSR
        port ( clock : in bit;  Q1, Q2, Q3 : out bit );
    end component;
    signal clock : bit := '0';
    signal val : bit_vector (3 downto 1);
begin
    L1: LFSR port map ( clock, val(1), val(2), val(3) );
    process begin
        for I in 1 to 20 loop
            wait for 1 us;    clock <= not clock;
        end loop;
        wait;
    end process;
end test;
```

LFSR – simulatsiooni tulemused

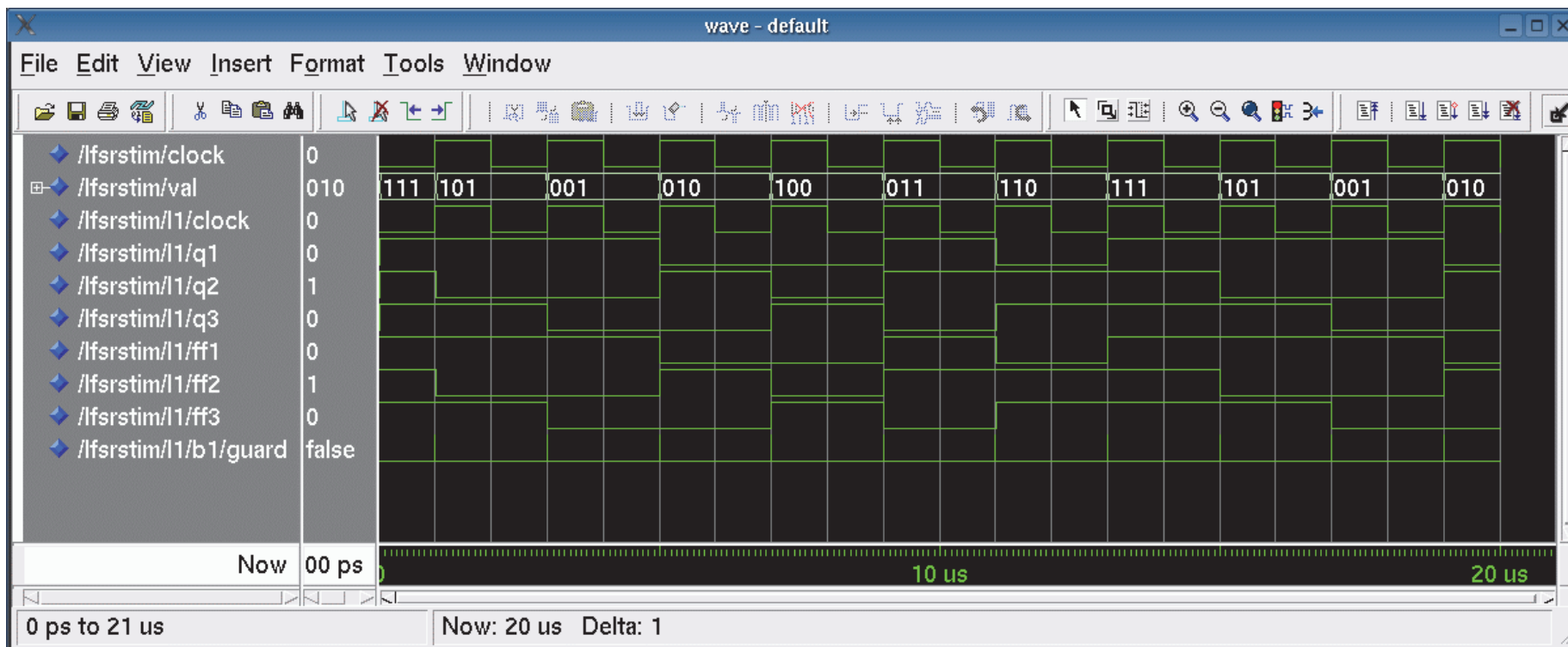



Konfiguratsioon [\(http://www10.edacafe.com/book/ASIC/ASICs.php\)](http://www10.edacafe.com/book/ASIC/ASICs.php)

- **komponendid**

```
entity AD2 is port (A1, A2: in BIT; Y: out BIT); end;  
architecture B of AD2 is begin Y <= A1 and A2; end;  
entity XR2 is port (X1, X2: in BIT; Y: out BIT); end;  
architecture B of XR2 is begin Y <= X1 xor X2; end;
```

- **komponentide deklaratsioonid & konfiguratsiooni spetsifikatsioon**


```
entity Half_Adder is port (X, Y: BIT; Sum, Cout: out BIT); end;  
architecture Netlist of Half_Adder is use work.all;  
    component MX port (A, B: BIT; Z:out BIT); end component;  
    component MA port (A, B: BIT; Z:out BIT); end component;  
    for G1:MX use entity XR2(B) port map(X1 => A,X2 => B,Y => Z);  
begin  
    G1:MX port map (X, Y, Sum); G2:MA port map (X, Y, Cout);  
end;
```

- **konfiguratsiooni deklaratsioon, plokk-konfiguratsioon, komponendi konfiguratsioon**

```
configuration C1 of Half_Adder is  
    use work.all;  
    for Netlist  
        for G2:MA  
            use entity AD2(B) port map(A1 => A,A2 => B,Y => Z);  
        end for;  
    end for;  
end;
```

IEEE 9-valentne loogika

Väärtus	Nimetus	Interpretatsioon
'U'	uninitialized	mudeli käitumine
'X'	forcing unknown	mudeli käitumine
'0'	forcing 0	loogikaväärtus ("transistor")
'1'	forcing 1	loogikaväärtus ("transistor")
'Z'	high impedance	ühendamata
'W'	weak unknown	mudeli käitumine
'L'	weak 0	loogikaväärtusl ("takisti")
'H'	weak 1	lloogikaväärtus ("takisti")
'-'	don't care	määramatusl

 

- **IEEE.std_logic_1164 – std_ulogic, std_logic ja std_logic_vector**
 - **std_ulogic** – baastüüp; **std_logic** – mitu signaali-allikat ja lahendus-funktsioon
- **IEEE.std_logic_arith – signed, unsigned**
 - **std_logic_vector**'i laiendamine märgiga või märgita täisarvuks




Lahendusfunktsioon (resolution function) – I²C näitel

```

package I2C_defs is
  type I2C_bit is ( '0', 'Z', 'H' );
  type I2C_bit_vector is array (integer range <>) of I2C_bit;
  function resolved ( v: I2C_bit_vector ) return I2C_bit;
  -- ...
end I2C_defs;
package body I2C_defs is
  function resolved ( v: I2C_bit_vector ) return I2C_bit is
    variable r: I2C_bit := 'Z';
    type I2C_1d is array ( I2C_bit ) of I2C_bit;
    type I2C_2d is array ( I2C_bit ) of I2C_1d;
    constant resolution_table: I2C_2d := (
      -----
      -- '0'  'Z'  'H'
      -----
      ( '0', '0', '0' ),   -- '0'
      ( '0', 'Z', 'H' ),  -- 'Z'
      ( '0', 'H', 'H' ) ); -- 'H'
  begin
    for i in v'range loop      r := resolution_table ( r ) ( v(i) );    end loop;
    return r;
  end resolved;
  -- ...
end I2C_defs;

```

 


VHDL & süntees – “what you write is what you get...”

- Mitte kõik konstruktsioonid pole sünteesitavad
- Kombinatorne loogika ja mäluelemendid tuleks eraldi kirjeldada (mõtle riistvaras!)
- Ettevaatust signaalide ja muutujate segiläbi kasutamisel!

```

signal A1, A2: BIT;
-- . . .
process (CLOCK)
  variable A3: BIT;
begin
  if CLOCK='1' and CLOCK'event then
    A3 := A1 and A2;
    Z <= A3;
  end if;
end process;


```

 

```

signal A1, A2, A3: BIT;
-- . . .
process (CLOCK)
begin
  if CLOCK='1' and CLOCK'event then
    A3 <= A1 and A2;
    Z <= A3;
  end if;
end process;

```

 


Lukk-register või frondist töötav (flip-flop)?

```
P1_L: process (CLK, D) begin
    if CLK='1' then    Q <= D;
    end if;
end process P1_L;
```


```
P2_FL: process (CLK) begin
    if CLK='1' then    Q<=D;
    end if;
end process P2_FL;
```
 
```
P1_FF: process (CLK) begin
    if CLK='1' and
        CLK'event then Q<=D;
    end if;
end process P1_FF;
```




- **Simulation OK kuid mitte süntees!**
 - Warning: Variable 'd' is being read
 - in routine .. line .. in file '..',
 - but is not in the process sensitivity
 - list of the block which begins
 - there. (HDL-179)

- **Tulemus – lukk-register**

 


VHDL & süntees – mõtle riistvaras!

 

```

library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_arith.all;
entity test is
  port ( a, b, c: in unsigned(7 downto 0);
        x: in unsigned(2 downto 0);
        o: out unsigned(7 downto 0) );
end test;
architecture bhv2 of test is begin
process (a, b, c, x) begin
  case x is
    when "010" => o <= a+b;
    when "011" => o <= a+c;
    when "110" => o <= b+c;
    when others =>
      o <= (others=>'0');
  end case;
end process;
end architecture bhv2;
  
```



220 l.e. / 11.57 ns

 

VHDL & süntees – mõtle riistvaras!

```

architecture rtl of test is
  signal a1, a2: unsigned(7 downto 0);
  signal dc: unsigned(1 downto 0);
begin
  dec: process (x) begin
    case x is
      when "010" => dc <= "01";
      when "011" => dc <= "10";
      when "110" => dc <= "11";
      when others => dc <= "00";
    end case;
  end process dec;
  m1: process (a, b, dc) begin
    case dc is
      when "01" => a1 <= a;
      when "10" => a1 <= a;
      when "11" => a1 <= b;
      when others => a1 <= (others=>'0');
    end case;
  end process m1;
  m2: process (b, c, dc) begin
    -- ...
  end process m2;
  o <= a1 + a2;
end architecture rtl;
  
```

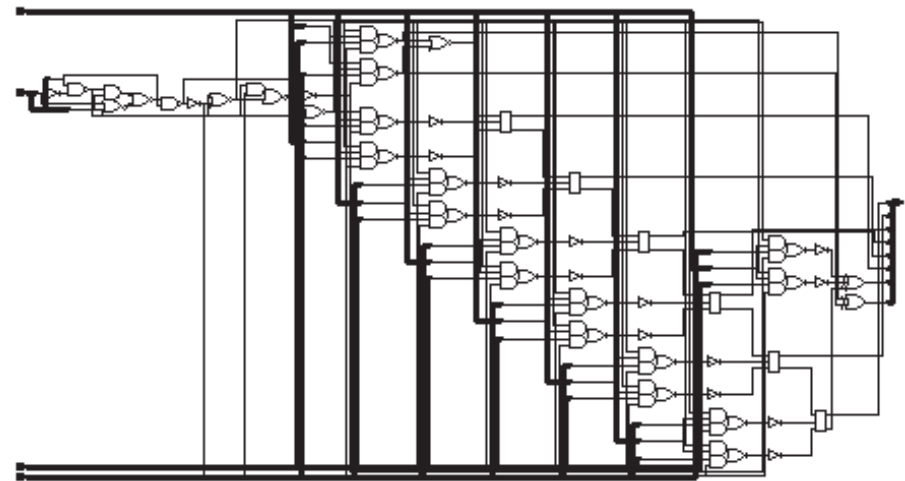 

117 l.e. / 19.2 ns




Universaalne liitja-lahutaja

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_arith.all;
entity add_sub is
  port ( a, b: in unsigned(7 downto 0);
        x: in std_logic;
        o: out unsigned(7 downto 0) );
end add_sub;
architecture bhv of add_sub is begin
process (a, b, x) begin
  if x='0' then o <= a+b;
  else          o <= a-b; end if;
end process;
end architecture bhv;
```

145 l.e. / 11.64 ns

```
architecture dfl of test5 is
  signal a1, b1, o1: unsigned(8 downto 0);
begin
  a1 <= a & '1';
  b1 <= b & '0' when x='0' else
    unsigned(not std_logic_vector(b)) &
    '1';
  o1 <= a1+b1;
  o <= o1(8 downto 1);
end architecture dfl;
```

87 l.e. / 12.45 ns

 


Liitjad & lahutajad

```

signal a, b, o: unsigned (7 downto 0);
signal a1,b1,o1: unsigned (9 downto 0);
-- ...
a1 <= '0' & a & '1';
b1 <= '0' & b & ci;
o1 <= a1 + b1;
o <= o1(8 downto 1);
co <= o1(9);
  
```

 
64 l.e. / 10.66 ns [60 l.e. / 10.08 ns ilma ci/co]



```

signal a, b, o: unsigned (7 downto 0);
signal a1,b1,o1: unsigned (9 downto 0);
-- ...
a1 <= '0' & a & '1';
b1 <= '0' &
    unsigned(not std_logic_vector(b)) & ci;
o1 <= a1 + b1;
o <= o1(8 downto 1);
co <= o1(9);
  
```

 72 l.e. / 10.62 ns [66 l.e. / 10.35 ns ilma ci/co]







Automaat – kirjeldus-stiilid & süntees

Kaks protsessi (modulo-4 counter)

```

library IEEE; use IEEE.std_logic_1164.all;
entity counter03 is
  port ( clk: in bit;
         resetn: in std_logic;
         three: out std_logic );
end entity counter03;
architecture fsm2 of counter03 is
  subtype state_type is integer range 0 to 3;
  signal pres_state, next_state: state_type := 0;
begin
  process (clk) begin -- State memory
    if clk'event and clk = '1' then
      pres_state <= next_state;
    end if;
  end process;
  -- Next state & output functions
  process (resetn, pres_state) begin
    three <= '0';
    if resetn='0' then      next_state <= 0;
    else
      case pres_state is
        when 0 to 2 => next_state <= pres_state + 1;
        when 3 => next_state <= 0;  three <= '1';
      end case;
    end if;
  end process;
end architecture fsm2;

```

  

22 gates / 3.70 ns

Automaat – kirjeldus-stiilid & süntees



Kolm protsessi (modulo-4 counter)

```

library IEEE; use IEEE.std_logic_1164.all;
architecture fsm3 of counter03 is
  subtype state_type is integer range 0 to 3;
  signal pres_state, next_state: state_type := 0;
begin
  process (clk) begin -- State memory
    if clk'event and clk = '1' then
      pres_state <= next_state;
    end if;
  end process;

  -- Next state function
  process (resetn, pres_state) begin
    if resetn='0' then next_state <= 0;
    else
      if pres_state=3 then next_state <= 0;
      else next_state <= pres_state + 1;
      end if;
    end if;
  end process;

    -- Output function
  process (resetn, pres_state) begin
    if pres_state=3 then three <= '1';
    else three <= '0';
    end if;
  end process;
end architecture fsm3;
  
```



23 gates / 4.36 ns





Automaat – kirjeldus-stiilid & süntees

Üks protsess (modulo-4 counter)

```
library IEEE; use IEEE.std_logic_1164.all;
architecture fsm1 of counter03 is
    subtype state_type is integer range 0 to 3;
    signal state: state_type := 0;
begin
    process (clk) begin
        if clk'event and clk = '1' then
            three <= '0';
            if resetn='0' then    state <= 0;
            else
                case state is
                    when 0 | 1 => state <= state + 1;
                    when 2 => state <= state + 1; three <= '1';
                    when 3 => state <= 0;
                end case;
            end if;
        end if;
    end process;
end architecture fsm1;

  // Another version to build the process
process begin
    wait on clk until clk='1';
    three <= '0';
    if resetn='0' then    state <= 0;
    else
        -- and so on...
```




38 gates / 5.68 ns



VHDL & kodutöö #1

- Teisenduste korrektsuse kontroll

```
entity test is end test;
architecture bench of test is
    signal a, b, c, d, k_err, ...: bit;
    ...
begin
    -- Sisendsignaaliid (sammuga 10 ns)
    a <= '0' after 0 ns, '1' after 80 ns, ...;
    ...
    -- Minimeerimise tulemus
    k0 <= ((not a) and (not d)) or (a and c and d)
        or ((not a) and b and (not c)) or
        (b and (not c) and (not d));
    ...
    -- Optimeerimise tulemus
    ai <= not (a and a);      bi <= not (b and b);
    ...
    t51 <= not (a and d);      t52 <= b xor d;
    t5t6i <= not (t51 and b and ci);
    k2 <= not (t0i and t4i and t5t6i);
    ...
    -- Kontrollimine...
    k_err <= k0 xor k2;      l_err <= l0 xor l2;
    ...
end bench;
```

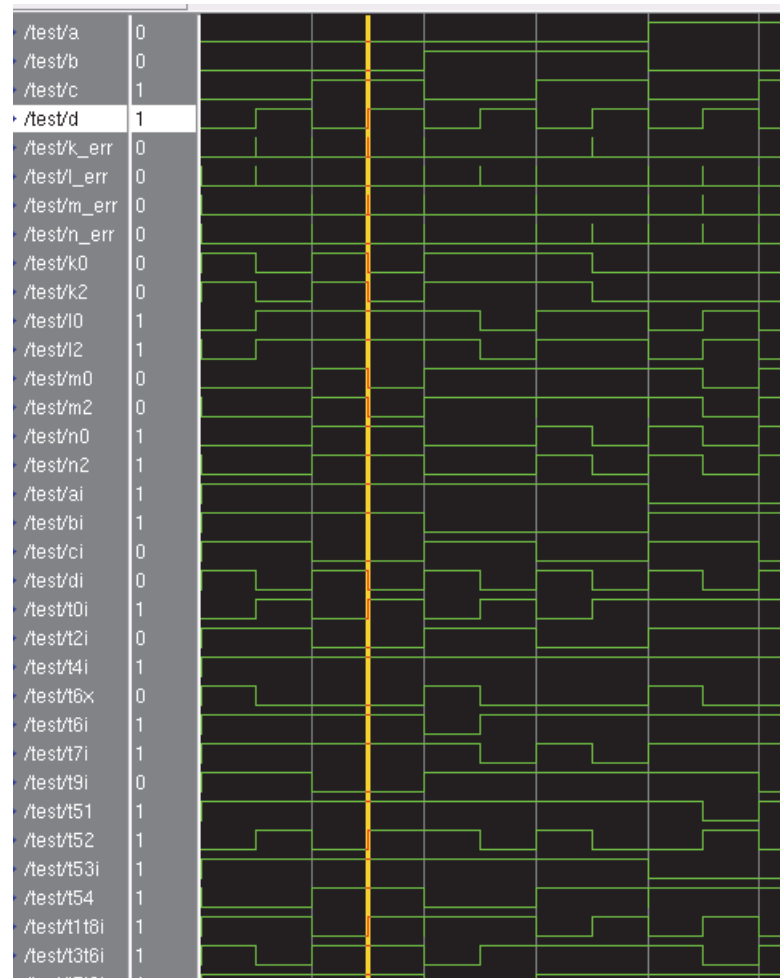



VHDL & kodutöö #1

- Loogikaelementide viitega mudelid

```
-- NOT - 1.5/1.5
entity inv is
  port (a: in bit; o: out bit);
end inv;
architecture str of inv is begin
  o <= not a after 1500 ps;
end str;
```

```
-- 2-NAND - 1.0/1.0
entity nand2 is
  port (a, b: in bit; o: out bit);
end nand2;
architecture str of nand2 is begin
  o <= not (a and b) after 1000 ps;
end str;
```

- Struktuur

- testpink, skeem, komponendid

```
entity test_str is  end test_str;

architecture bench of test_str is
  signal a, b, c, d, k_err, ...: bit;
  ...
  component skeem is
    port ( a, b, c, d: in bit;
          k, l, m, n: out bit );
  end component;
begin
```


```
-- Sisendsignaaliid (sammuga 10 ns)
a <= '0' after 0 ns, '1' after 80 ns,
    '0' after 160 ns;
...
-- Lõplik skeem
u1: skeem port map
    ( a, b, c, d, k2, l2, m2, n2 );
-- Võrdlemine...
k_err <= k0 xor k2;  ...
end bench;
```



VHDL & kodutöö #1

- Teisenduste korrektsuse kontroll

```
entity skeem is
  port ( a, b, c, d: in bit;  k, l, m, n: out bit );
end skeem;
architecture struktuur of skeem is
  signal ai, bi, ci, di: bit;
  ...
  component nand2 is
    port (a, b: in bit; o: out bit); end component;
  ...
  component xor2 is
    port (a, b: in bit; o: out bit); end component;
begin
  u01: nand2 port map (a,a,ai);
  ...
  u11: or2 port map (a,d,t0i);
  ...
  u21: nand2 port map (a,d,t51);
  ...
  u33: nand3 port map (t51,b,ci,t5t6i);
  u41: nand3 port map (t0i,t4i,t5t6i,k);
  u42: nand2 port map (t2i,t3t6i,l);
  u43: nand3 port map (t1t8i,t6i,t7i,m);
  u44: nand3 port map (t1t8i,t4i,t9i,n);
end struktuur;
```

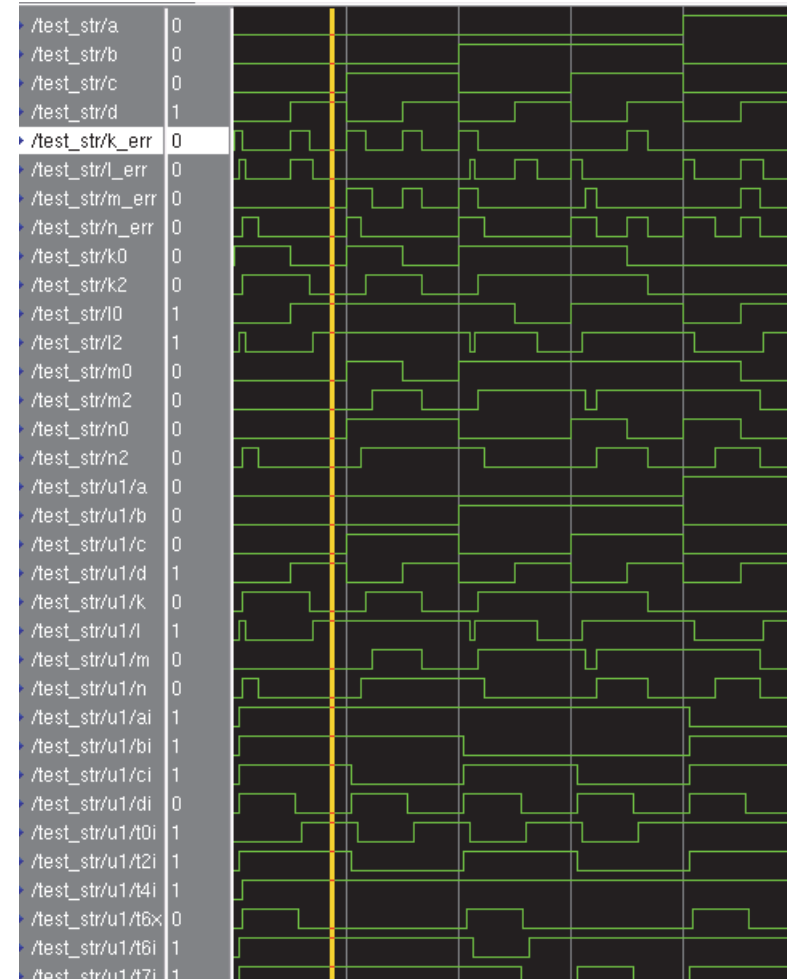



VHDL & kodutöö #1

- Mitme versiooni korraga simuleerimine

```
library IEEE; use IEEE.std_logic_1164.all;
entity test2 is      end entity test2;
library IEEE; use IEEE.std_logic_1164.all;
architecture bench of test2 is
    signal a, b, c, d, k, l, m, n: std_logic;
    signal k2, k3, l2, l3, m2, m3, n2, n3: std_logic;
    component f_system
        port ( a, b, c, d: in std_logic;
              k, l, m, n: out std_logic );
    end component;
    for U1: f_system use entity work.f_system(tabel);
    for U2: f_system use entity work.f_system(espresso);
    for U3: f_system use entity work.f_system(opti);
begin
    -- Input signals (after every 10 ns)
    a <= '0' after 0 ns, '1' after 80 ns, '0' after 160 ns;
    b <= '0' after 0 ns, '1' after 40 ns, ...
    c <= '0' after 0 ns, '1' after 20 ns, ...
    d <= '0' after 0 ns, '1' after 10 ns, ...
    -- System of Boolean functions
    U1: f_system port map (a, b, c, d, k, l, m, n);
    U2: f_system port map (a, b, c, d, k2, l2, m2, n2);
    U3: f_system port map (a, b, c, d, k3, l3, m3, n3);
end architecture bench;
```

