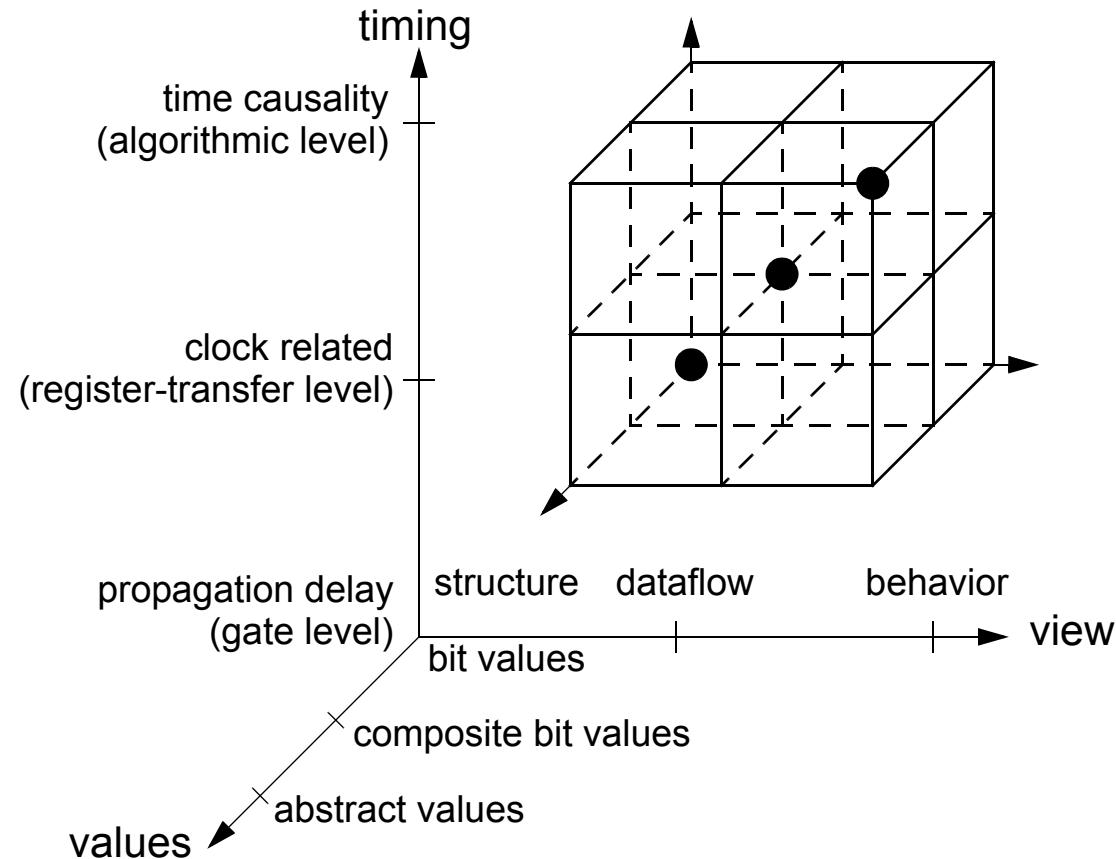




TTÜ1918




HDL Design Cube





Synthesis and VHDL

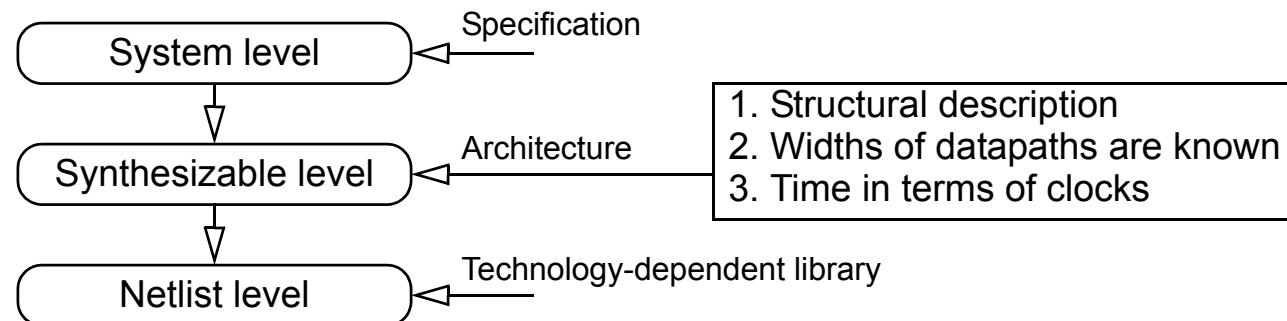- **VHDL LRM defines only simulation semantics of the language.**
- **LRM – Language Reference Manual**



- **Synthesis restrictions:**
 - the lack of maturity of synthesis tools
 - the state-of-art in synthesis targets RTL synthesis only
 - certain VHDL features are simply not synthesizable
- **The same applies to Verilog/SystemVerilog...**



TTÜ1918



Synthesis style

- **Delay expressions (after clauses, wait for statements are ignored)**
- **Certain restrictions on the writing of process statement occur**
- **Only a few types are allowed**
 - integer, enumerated, e.g., bit, bit_vector, signed
- **Type conversion and resolution functions are not interpreted**
- **Description is oriented towards synchronous styles with explicit clocks**
- **Types: enumeration, integer, one-dimensional array, record**

```
type WORD is array (31 downto 0) of BIT;
type RAM is array (1023 downto 0) of WORD;
```
- **In record, an item address becomes hardware coded**
- **!!! Time type is not supported !!!**
- **No explicit or default initialization**
- **Parenthesis in expressions have effect on HW generation**
- **Some arithmetic operations are supported partially only**



TTÜ1918



Sensitivity list

- **Equivalent processes:**

```
process (A, B, C)
...
begin
...
end process;
```



```
process
...
begin
wait on A, B, C;
...
end process;
```



```
process
...
begin
...
wait on A, B, C;
end process;
```

- Some synthesizers support only sensitivity list for combinational logic
- In case of single synchronization process there is no need to “remember” at which synchronization point it was stopped -> such behavior does not imply memorization
- Process with multiple synchronization points, i.e. several wait states, infer memorization – FSM



TTÜ1918




Assignment statement synthesis

```
signal A,B: BIT_VECTOR(0 to 3);
signal I: INTEGER range 0 to 3;
signal Y,Z: BIT;

-- . . .

process ( I, Y, Z ) begin
  A<="0000";
  B<="0000";
  A(I)<=Y; -- Computable index
  B(3)<=Z; -- Constant index
end process;
```


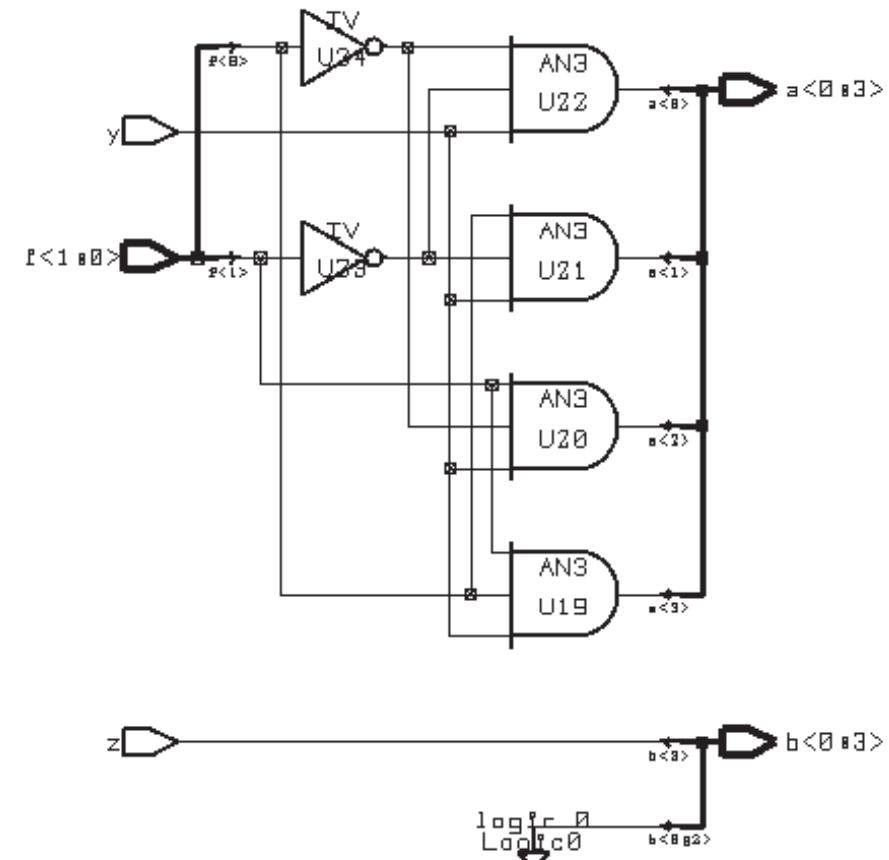




TTÜ1918



```
signal A,B,C,P1,P2,Z: BIT;  
-- . . .  
process (P1,P2,A,B,C) begin  
  if (P1 = '1') then  
    Z <= A;  
  elsif (P2 = '0') then  
    Z <= B;  
  else  
    Z <= C;  
  end if;  
end process;
```

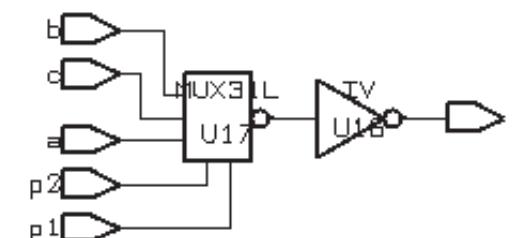
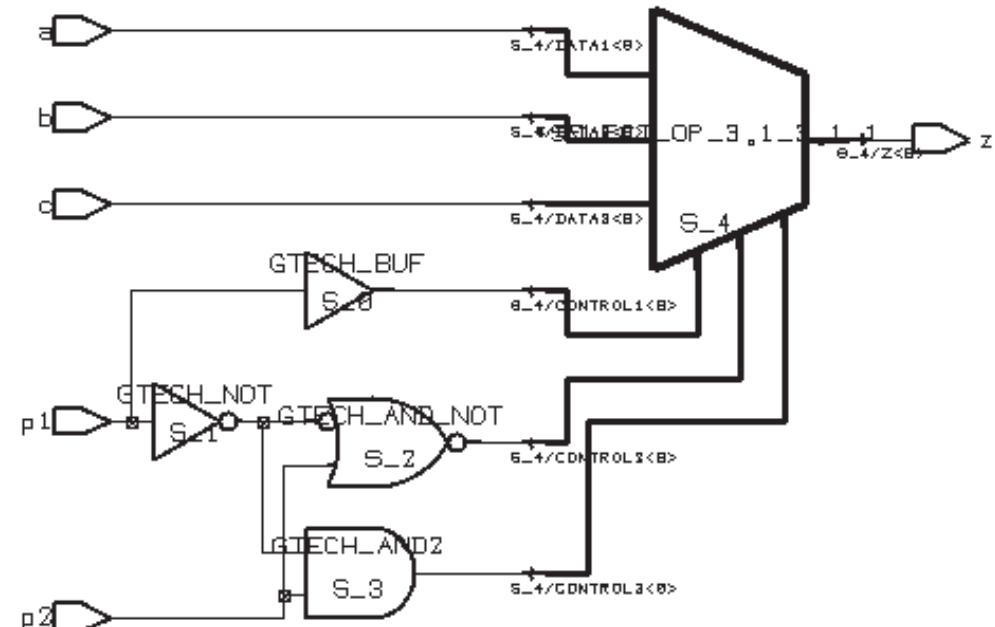




TTÜ1918



SR latch

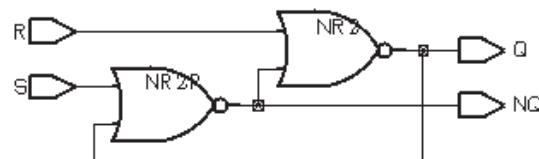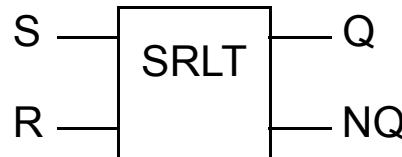

```
use WORK.CHECK_PKG.all;
entity SRLT is
    port ( S, R:  in bit;
           Q, NQ: out bit );
begin
    NOT_AT_THE_SAME_TIME(S,R);
end SRLT;

-----
architecture A1 of SRLT is
    signal LQ:  bit := '1';
    signal LNQ: bit := '0';
begin
    LNQ <= S nor LQ;
    LQ  <= R nor LNQ;
    Q   <= LQ;
    NQ  <= LNQ;
end A1;
```

- **NB! Asynchronous feed-back is temporarily cut by synthesizers...**



TTÜ1918



Combinational circuit

- A process is combinational, i.e. does not infer memorization, if:
 - the process has an explicit sensitivity list or contains a single synchronization point (waiting for changes on all input values); ¹⁾
 - no local variable declarations, or variables are assigned before being read;
 - all signals, which values are read, are part of the sensitivity list; ²⁾ and
 - all output signals are targets of signal assignments independent on the branch of the process, i.e. all signal assignments are covered by all conditional combinations.

¹⁾ waiting on a clock signal, e.g., “wait on clk until clk='1'; ”, implies buffered outputs (FF-s)

²⁾ interpretation may differ from tool to tool



TTÜ1918





Complex assignments

- No memory

```
S <= A when X='1' else B when Y='1' else C;
```

```
process (A, B, C, X, Y) begin
    if      X='1' then S <= A;
    elsif  Y='1' then S <= B;
    else
        S <= C;
    end if;
end process;
```

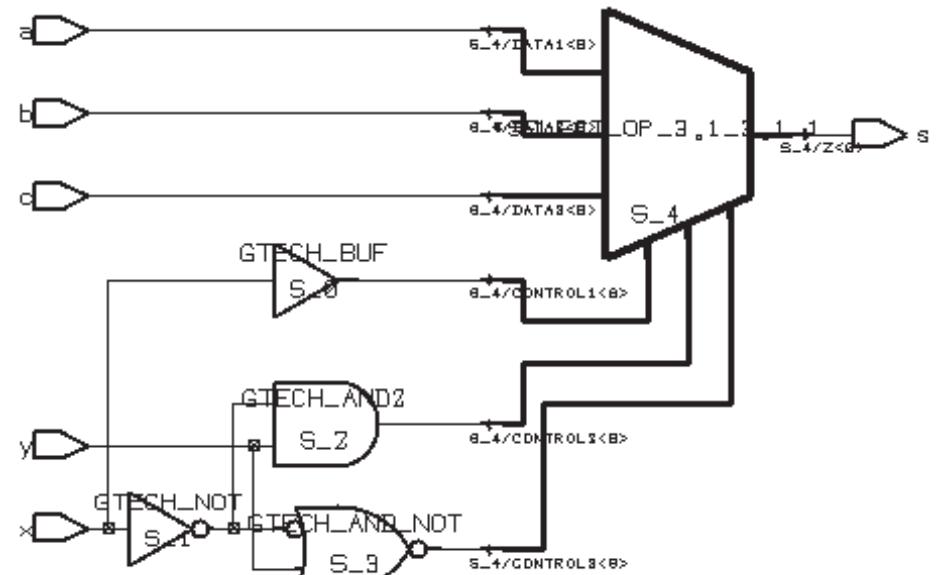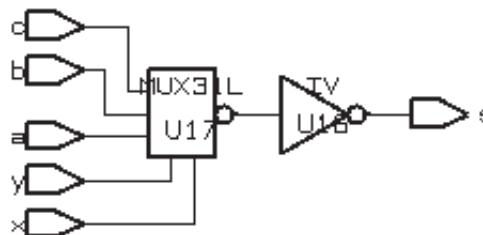





TTÜ1918



Complex assignments (#2)

- **Memory element generated!**

```
process (A, B, X, Y) begin
  if  X='1' then  S <= A;
  elsif Y='1' then  S <= B;
  end if;
end process;
```

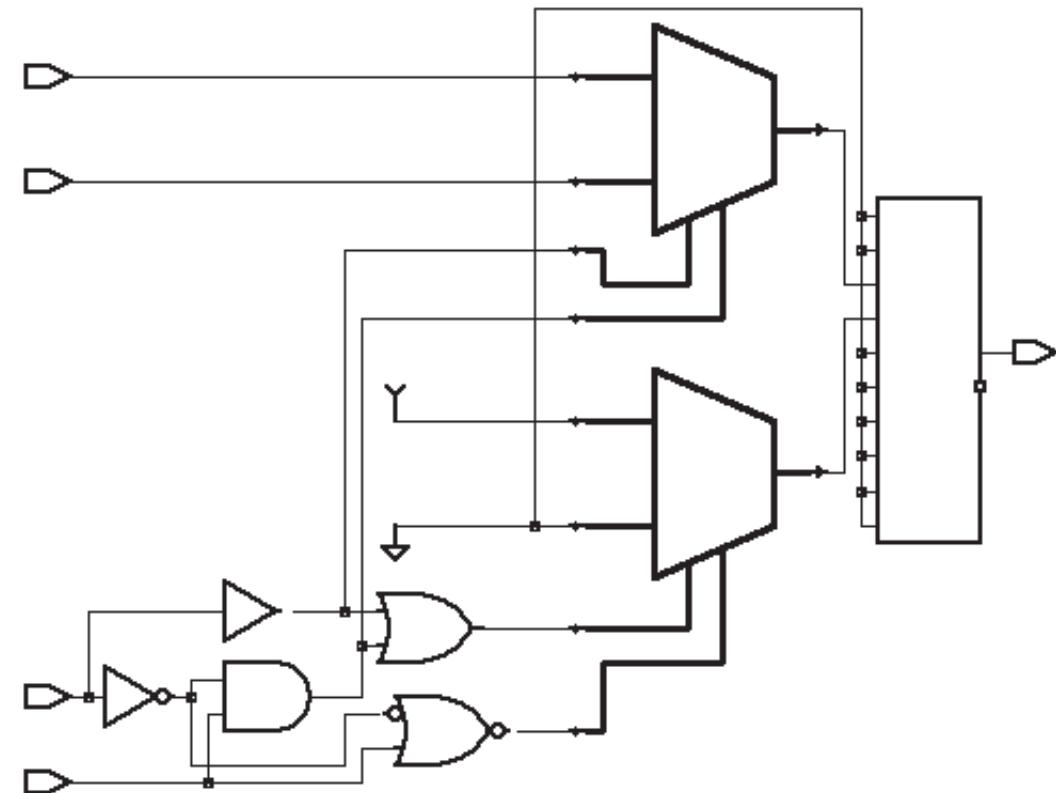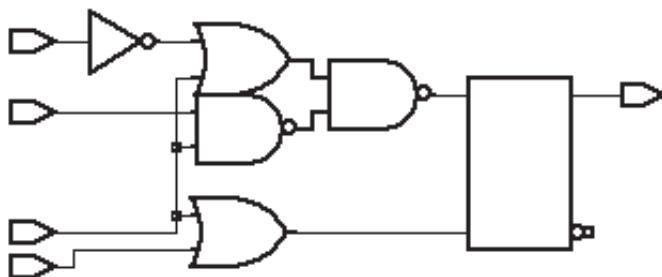



TTÜ1918





Complex assignments (#3)

- **Memory element generated!**

```
S <= A when X='1' else B when Y='1' else S;
```

```
process (A, B, X, Y) begin
    if      X='1' then    S <= A;
    elsif  Y='1' then    S <= B;
    else
        end if;
end process;
```

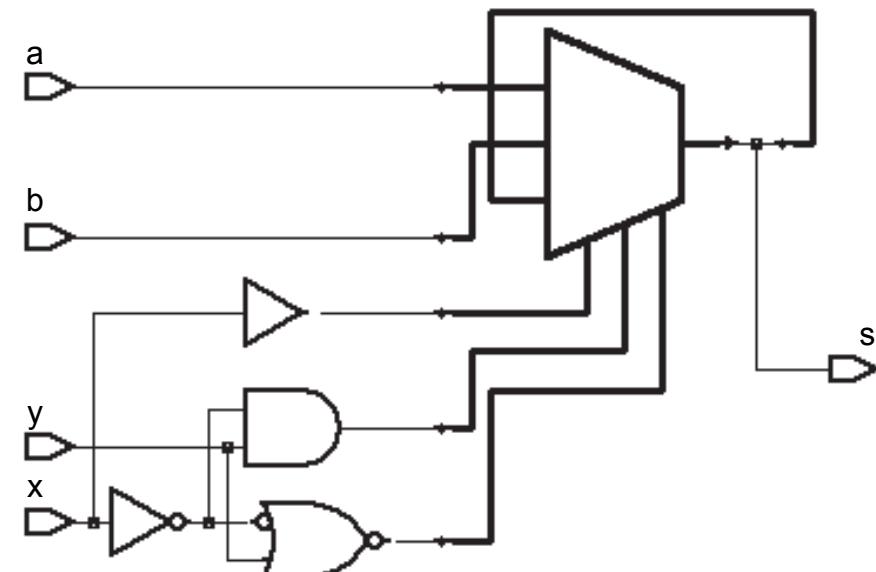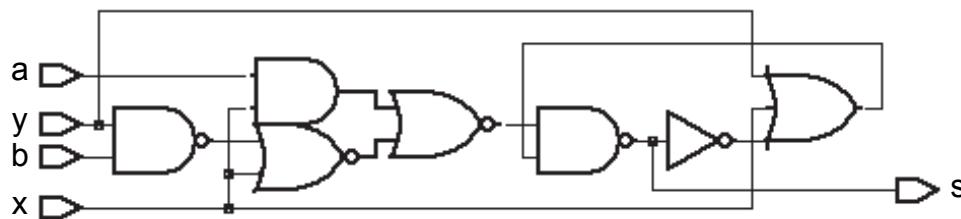



TTÜ1918





Default values

- The default values inherited from type or subtype definitions
- The explicit initialization that is given when the object is declared
- A value assigned using a statement at the beginning of a process
- Only the last case is supported by synthesis tools!
- Usually, a part of the synthesizable code is devoted to set/reset constructions
- Default values can be used to guarantee that the signal always gets a new value

```
process (A, B, X, Y) begin
    S <= '0';
    if      X='1' then    S <= A;
    elsif   Y='1' then    S <= B;
    end if;
end process;
```
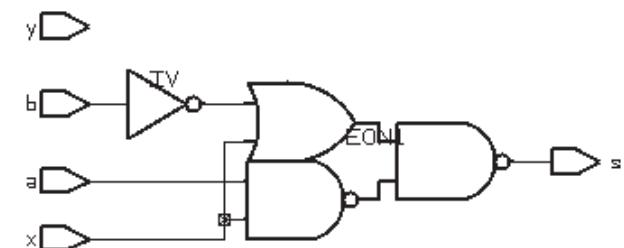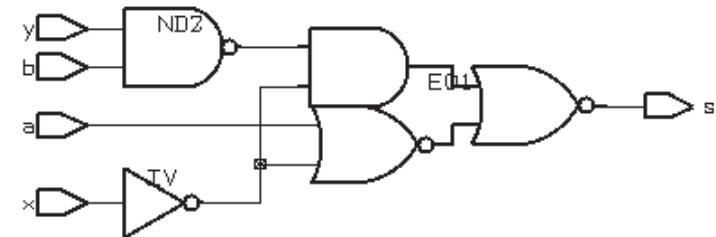
```
process (A, B, X, Y) begin
    S <= '-';
    if      X='1' then    S <= A;
    elsif   Y='1' then    S <= B;
    end if;
end process;
```






Flip-flops

- **Process with the clock signal in the sensitivity list and explicit clock flank definition**
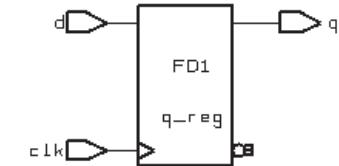
```
process (CLK) begin
    if CLK='1' and CLK'event then      Q <= D;      end if;
end process;
```



- **Process with the clock signal and clock flank definition in the wait statement**


```
process begin
    wait on CLK until CLK='1';      Q <= D;
end process;
```

- **Concurrent assignment with the clock signal and clock flank definition**

```
Q <= D when CLK='1' and CLK'event;
```

- **Asynchronous reset & synchronous enable**

```
process (RES,CLK) begin
    if      RES='1' then      Q <= '0';      -- asynchronous reset
    elsif CLK='1' and CLK'EVENT then
        if  ENA='1' then      Q <= D;      end if;
    end if;
end process P4_FF;
```

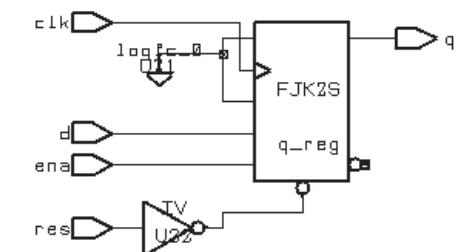



TTÜ1918



Latch vs. Flip-flop?



```
P1_L: process (CLK, D) begin
    if CLK='1' then      Q <= D;
    end if;
end process P1_L;
```

```
P2_FL: process (CLK) begin
    if CLK='1' then      Q<=D;
    end if;
end process P2_FL;
```

```
P1_FF: process (CLK) begin
    if CLK='1' and
        CLK'event then  Q<=D;
    end if;
end process P1_FF;
```

- Simulation OK but not synthesis!
-- Warning: Variable 'd' is being read
-- in routine .. line .. in file '...',
-- but is not in the process sensitivity
-- list of the block which begins
-- there. (HDL-179)

- Result - latch

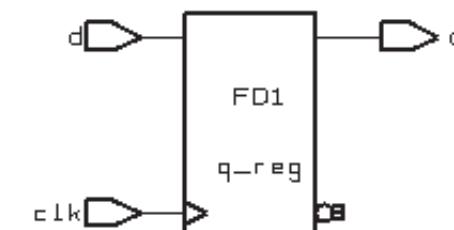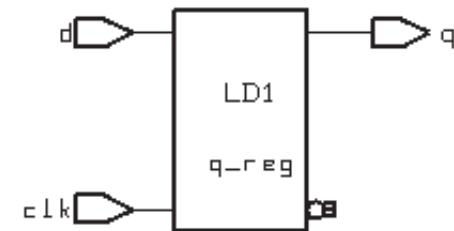




TTÜ1918



Synthesis rules

- Guidelines in priority order:
 - the target signal(s) will be synthesized as flip-flops when there is a signal edge expression, e.g. CLK'event and CLK='1', in the process
 - usually, only one edge expression is allowed per process
 - different processes can have different clocks (tool depending)
 - the target signal will infer three-state buffer(s) when it can be assigned a value 'Z'
 - example: $Q \leq D$ when $SEL='1'$ else 'Z';
 - the target signal will infer a latch (latches) when the target signal is not assigned with a value in every conditional branch, and the edge expression is missing
 - a combinational circuit will be synthesized otherwise
- It is a good practice to isolate flip-flops, latches and three-state buffers inferences to ensure design correctness

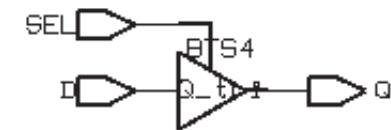





Signal versus variable

- The hardware resulting from synthesis of variables or signals differs:
either nothing, wires, or memory elements

```
signal A1, A2: BIT;  
-- . . .  
process (CLOCK)  
  variable A3: BIT;  
begin  
  if CLOCK='1' and CLOCK'event then  
    A3 := A1 and A2;  
    Z <= A3;  
  end if;  
end process;
```
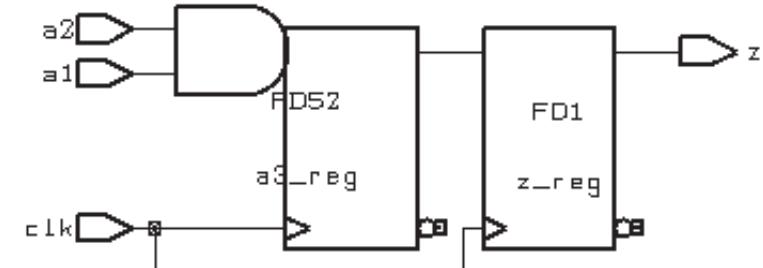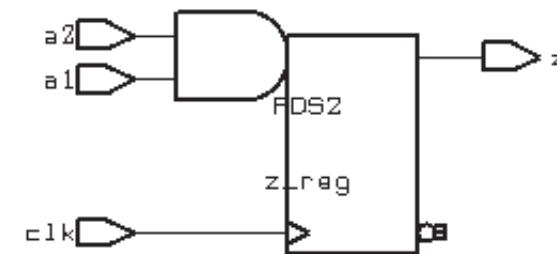
```
signal A1, A2, A3: BIT;  
-- . . .  
process (CLOCK)  
begin  
  if CLOCK='1' and CLOCK'event then  
    A3 <= A1 and A2;      -- Next delta-cycle!!  
    Z <= A3;  
  end if;  
end process;
```






Arithmetics

- Overloaded arithmetic operations:

```
library IEEE;  
use IEEE.std_logic_1164.all;  
use IEEE.std_logic_arith.all;
```

- Sources of the named packages are in the directory: \$SYNOPSYS/packages/IEEE/src
 - \$SYNOPSYS/packages is the root directory for all Synopsys packages
 - Be careful with "*", '/', '**' - extremely chip area consuming
 - Safe in some special cases - multiplication by power of two
 - Use parenthesis to group a set of gates
- Don't care values and synthesis

```
process (A, B, SEL) begin  
  case SEL is  
    when "001" => X <= A;  
    when "010" => X <= B;  
    when others => X <= '-';  
  end case;  
end process;
```

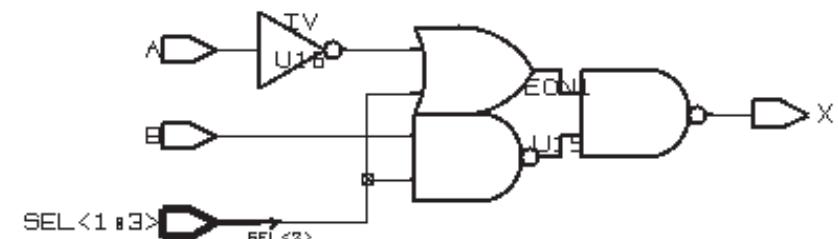




TTÜ1918



Data-part & control-part

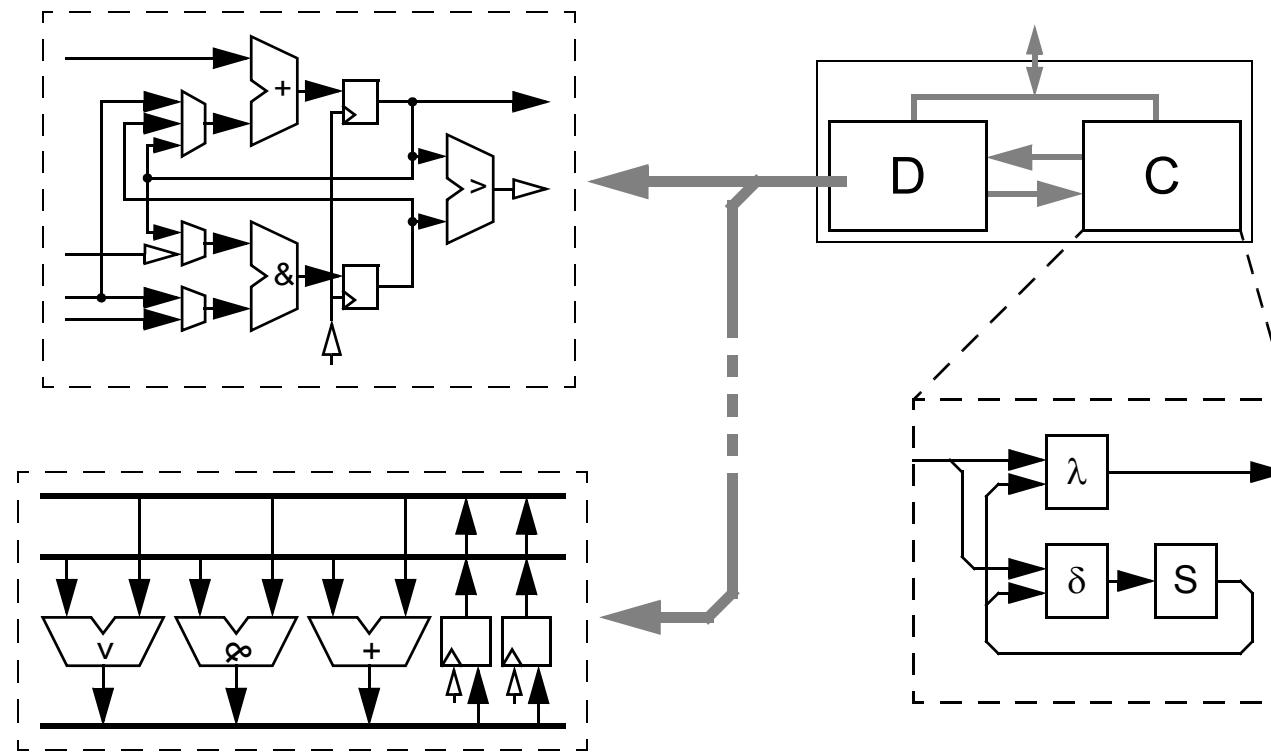

- **one unit – one process**
 - functional units – combinational processes
 - storage units – clocked processes
- [all inputs in the sensitivity list]
[activation at clock edge]




TTÜ 1918



FSM in VHDL

- **FSM:** $M = (S, I, O, \delta, \lambda)$
 - **S:** set of states
 - **I:** set of inputs
 - **O:** set of outputs
 - **δ :** transition function - $\delta: S \times I \rightarrow S$
 - **λ :** output function - $\lambda: S \times I \rightarrow O$
- **How many processes?**
 - Process per block
- **Three processes**
 - (1) transition function, (2) output function, (3) state register
- **Two processes**
 - (1) merged transition and output functions, (2) state register [Mealy]
- **One process**
 - buffered outputs! [Moore]

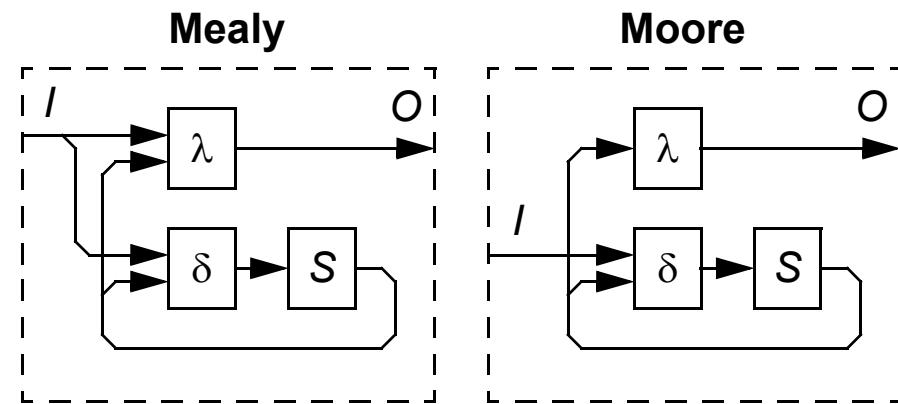



FSM as a single process

- Note that all signals assigned in the process will have flip-flops!

```
-- RESET is the asynchronous reset, CLK is the clock
-- STATE is a variable (or signal) memorizing the current state
process (RESET,CLK)
begin
    if RESET='1' then          -- asynchronous reset
        STATE <= S_INIT;
    elsif CLK='1' and CLK'EVENT then
        case STATE is
            when S_INIT => if I0='1' then STATE <= S5; end if;
            when ... => ...
        end case;
    end if;
end process;
```



Three process FSM

- **storage elements, transition function & output function**

```
architecture B of FSM is
    type TYPE_STATE is (S_INIT,S1,...Sn);
    signal CURRENT_STATE, NEXT_STATE : TYPE_STATE;
begin
    P_STATE: process begin -- sequential process / storage elements
        wait until CLK'EVENT and CLK='1';
        if RESET ='1' then CURRENT_STATE <= S_INIT;
        else                  CURRENT_STATE <= NEXT_STATE; end if;
    end process P_STATE;
    P_NEXT_STATE: process (I0, ..., CURRENT_STATE) begin -- next state function
        NEXT_STATE <= CURRENT_STATE;
        case CURRENT_STATE is
            when S_INIT => if I0='1' then NEXT_STATE <= S5; end if;
            when ... => ...
        end case;
    end process P_NEXT_STATE;
    P_OUTPUTS: process (CURRENT_STATE) begin -- output function
        case CURRENT_STATE is
            when S_INIT => O <= '0';
            when ... => ...
        end case;
    end process P_OUTPUTS;
end B;
```





TTÜ1918



FSM #2 – description styles & synthesis

Two processes (modulo-4 counter)

```
library IEEE; use IEEE.std_logic_1164.all;
entity counter03 is
    port ( clk: in bit;
           resetn: in std_logic;
           three: out std_logic );
end entity counter03;
architecture fsm2 of counter03 is
    subtype state_type is integer range 0 to 3;
    signal pres_state, next_state: state_type := 0;
begin
    process (clk) begin -- State memory
        if clk'event and clk = '1' then
            pres_state <= next_state;
        end if;
    end process;
    -- Next state & output functions
    process (resetn, pres_state) begin
        three <= '0';
        if resetn='0' then      next_state <= 0;
        else
            case pres_state is
                when 0 to 2 => next_state <= pres_state + 1;
                when 3 => next_state <= 0;  three <= '1';
            end case;
        end if;
    end process;
end architecture fsm2;
```

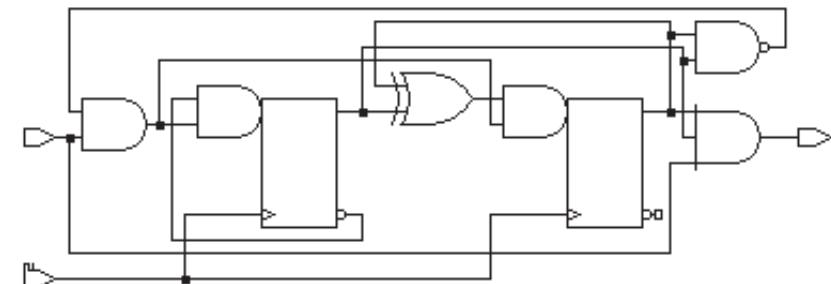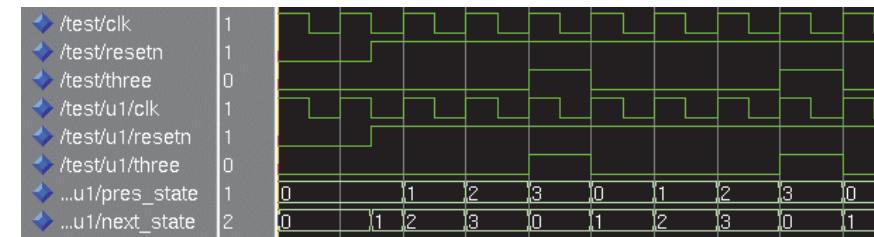

22 gates / 3.70 ns



TTÜ1918





FSM #2 – description styles & synthesis

Three processes (modulo-4 counter)

```
library IEEE; use IEEE.std_logic_1164.all;
architecture fsm3 of counter03 is
    subtype state_type is integer range 0 to 3;
    signal pres_state, next_state: state_type := 0;
begin
    process (clk) begin -- State memory
        if clk'event and clk = '1' then
            pres_state <= next_state;
        end if;
    end process;

    -- Next state function
    process (resetn, pres_state) begin
        if resetn='0' then      next_state <= 0;
        else
            if pres_state=3 then      next_state <= 0;
            else      next_state <= pres_state + 1;
            end if;
        end if;
    end process;
    -- Output function
    process (resetn, pres_state) begin
        if pres_state=3 then      three <= '1';
        else                      three <= '0';
        end if;
    end process;
end architecture fsm3;
```

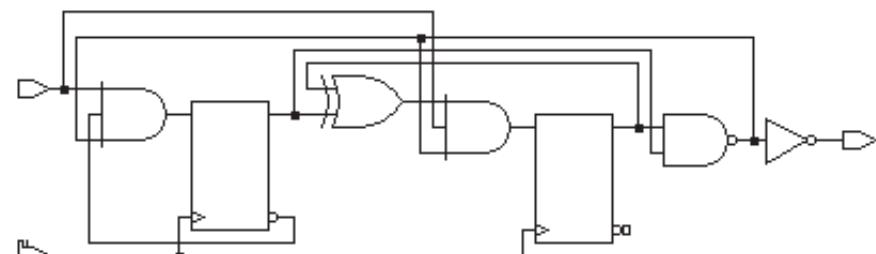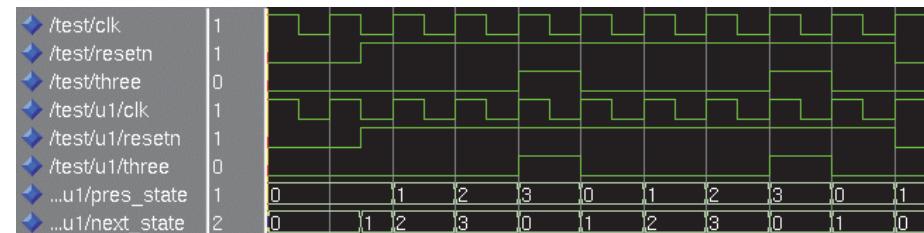

23 gates / 4.36 ns



TTÜ1918





FSM #2 – description styles & synthesis

One process (modulo-4 counter)

```
library IEEE; use IEEE.std_logic_1164.all;
architecture fsm1 of counter03 is
  subtype state_type is integer range 0 to 3;
  signal state: state_type := 0;
begin
  process (clk) begin
    if clk'event and clk = '1' then
      three <= '0';
      if resetn='0' then      state <= 0;
      else
        case state is
          when 0 | 1 => state <= state + 1;
          when 2 => state <= state + 1;  three <= '1';
          when 3 => state <= 0;
        end case;
      end if;
    end if;
  end process;
end architecture fsm1;

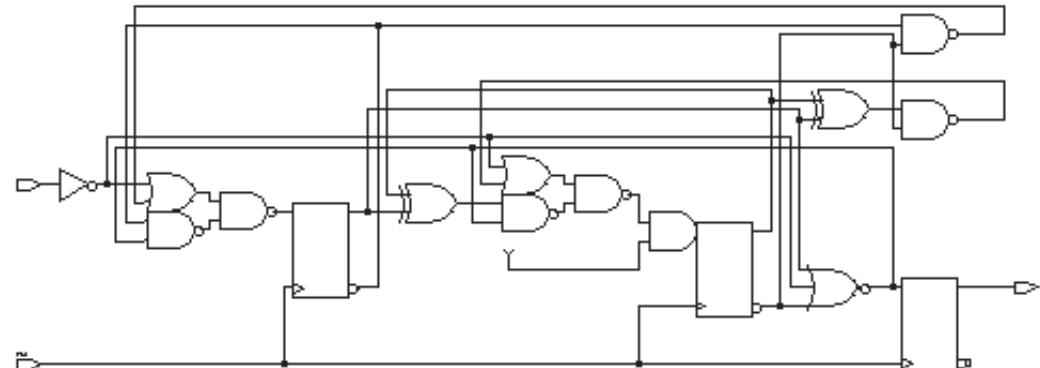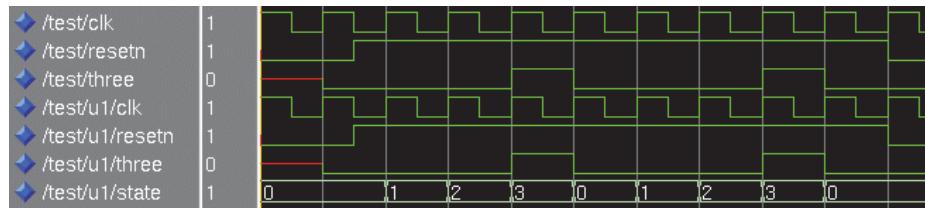// Another version to build the process
process begin
  wait on clk until clk='1';
  three <= '0';
  if resetn='0' then      state <= 0;
  else
    -- and so on...
```



38 gates / 5.68 ns



TTÜ1918



Using generics

```
entity AND_N is
    generic (N: POSITIVE);
    port      (DIN: in BIT_VECTOR(1 to N); R: out BIT);
end AND_N;

architecture A1 of AND_N is
    signal INTER: BIT_VECTOR(1 to N);
begin
    INTER(1) <= DIN(1);
    L: for I in 1 to N-1 generate
        INTER(I+1) <= DIN(I+1) and INTER(I);
    end generate;
    R <= INTER(N);
end A1;

C1: AND_N generic map (N=>12) port map(IN_DATA, OUT_DATA);
```



for-loop versus while-loop?

- **May be tool dependent!**
 - Design Compiler (Synopsys): *for* - parallel, *while* - sequential
 - ISE (Xilinx): *for* / *while* - both parallel
 - Leonardo (Mentor Graphics): depending on the timing constructs
- **for-loop**
 - parallel implementation
 - no timing control (wait) in the loop body
- **while-loop**
 - sequential implementation
 - timing control (wait) required in the loop body

```
for i in 0 to 7 loop
    x(i) := a(i) and b(i);
end loop;
```

```
i := 0;
while i<7 loop
    data(i) := in_port;
    wait on clk until clk='1';
    i := i + 1;
end loop;
```



Multiple wait statements

- VHDL semantics must be preserved
 - different interpretations possible
- Distributing operations over multiple clock steps
- Algorithm
 - Inputs: a, b, c, d
 - Output: x
 - Coefficients: c1, c2
 - $x = a + b*c1 + c*c2 + d$
 - Timing constraint - 3 clock periods

```
process
    variable av, bv, cv, dv: ...;
begin
    av:=a; bv:=b; cv:=c; dv:=d;
    wait on clk until clk='1';
    wait on clk until clk='1';
    x <= av + bv * c1 + cv * c2 + dv;
    wait on clk until clk='1';
end process;
```



Multiple wait statements

- Behavioral interpretation may lead to an unoptimal solution

```
process
    variable av, bv, cv, dv: ...;
begin
    av:=a; bv:=b; cv:=c; dv:=d;
    wait on clk until clk='1';
    wait on clk until clk='1';
    x <= av + bv * c1 + cv * c2 + dv;
    wait on clk until clk='1';
end process;
```

2 multipliers & 3 adders

```
process
    variable av, bv, cv, dv: ...;
    variable r1, r2: ...;
begin
    av:=a; bv:=b; cv:=c; dv:=d;
    r1 := av + dv;    r2 := bv * c1;
    wait on clk until clk='1';
    r1 := r1 + r2;   r2 := cv * c2;
    wait on clk until clk='1';
    x <= r1 + r2;
    wait on clk until clk='1';
end process;
```

1 multiplier & 1 adder

*Behavioral Synthesis
(High-Level Synthesis)*



Inserting wait statements

- VHDL semantics preserved for inputs/outputs
 - targeting as-fast-as-possible (AFAP) schedules
- 16-tap FIR filter
 - new input and output data at every rising flank of sys_clk (sampling clock)
 - internal clock can be added
- How to implement loops?
 - 1st - in parallel (shift-register)
 - 2nd - sequentially
 - multiply-and-accumulate (MAC)
 - ROM for coefficients

```
process
    variable sum: ...;
    variable buff: ...; -- array (0 to 15)
begin
    for i in 15 downto 1 loop
        buff(i) := buff(i-1);
    end loop;
    buff(0) := data_in;      sum := 0;
    for i in 0 to 15 loop
        sum := sum + buff(i) * coeff(i);
    end loop;
    x <= sum;
    wait on sys_clk until sys_clk='1';
end process;
```




TTÜ 1918



Verilog/SystemVerilog – synthesis rules

- Guidelines in priority order:
 - the target signal(s) will be synthesized as flip-flops when there is a signal edge expression, e.g. “`@(posedge CLK)`”, in the behavioral statement
 - only one edge expression is allowed per behavioral statement
 - different statements can have different clocks (tool depending)
 - the target signal will infer three-state buffer(s) when it can be assigned a value 'Z'
 - example: `q = sel == 1 ? d : 'bz;`
 - the target signal will infer a latch (latches) when the target signal is not assigned with a value in every conditional branch, and the edge expression is missing
 - a combinational circuit will be synthesized otherwise
- It is a good practice to isolate flip-flops, latches and three-state buffers inferences to ensure design correctness

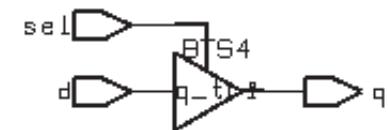



TTÜ1918



Combinational circuit

- A process is combinational, i.e. does not infer memorization, if:
 - the behavioral statement has a sensitivity list in the beginning (waiting for changes on all input values); ¹⁾
 - signals are assigned before being read;
 - all signals, which values are read, are part of the sensitivity list; ²⁾ and
 - all output signals are targets of signal assignments independent on the branch of the process, i.e. all signal assignments are covered by all conditional combinations.

¹⁾ waiting on a clock signal, e.g., “ @(posedge clk) ”, implies buffered outputs (FF-s)

²⁾ interpretation may differ from tool to tool

- SystemVerilog has three new *always* constructs
 - **always_comb** – explicit combinational circuit
 - **always_latch** – explicit latch
 - **always_ff** – explicit flip-flop



Sensitivity list

- Equivalent statements:

```
always
  @ (a or b or c or x or y)
begin
  if (x==1)      s=a;
  else if (y==1) s=b;
  else           s=c;
end
```

==

```
always begin
  @ (a or b or c or x or y);
  if (x==1)      s=a;
  else if (y==1) s=b;
  else           s=c;
end
```

- In case of single synchronization process there is no need to “remember” at which synchronization point it was stopped -> such behavior does not imply memorization



TTÜ1918



Complex assignments

- No memory



```
assign s = x==1 ? a : y==1 ? b : c;
```

```
always
```

```
  @ (a or b or c or x or y)
    if (x==1)      s=a;
    else if (y==1) s=b;
    else           s=c;
```

```
always_comb
```

```
  if (x==1)      s=a;
  else if (y==1) s=b;
  else           s=c;
```

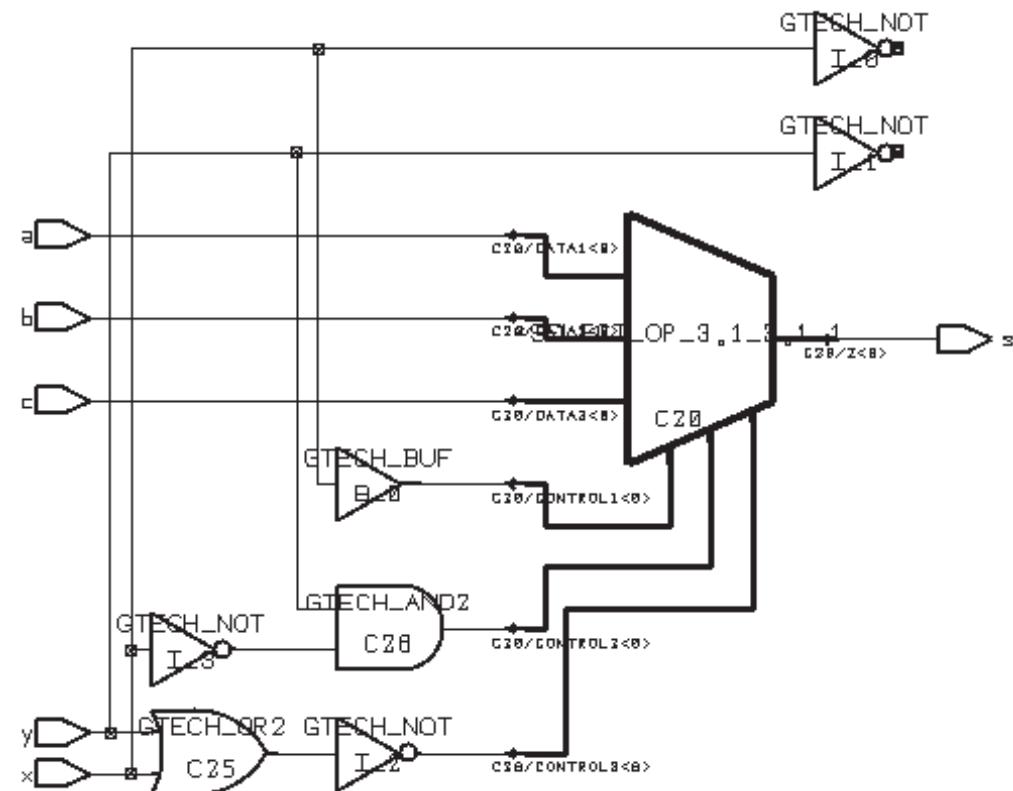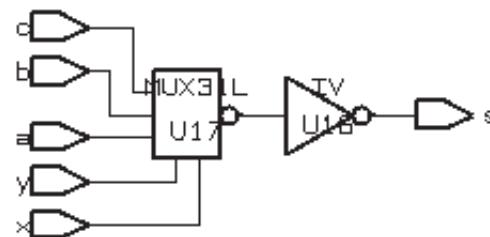





TTÜ1918



Complex assignments (#2)

- **Memory element generated!**

```
always begin
  @ (a or b or x or y);
    if (x==1)      s=a;
    else if (y==1) s=b;
  end
```

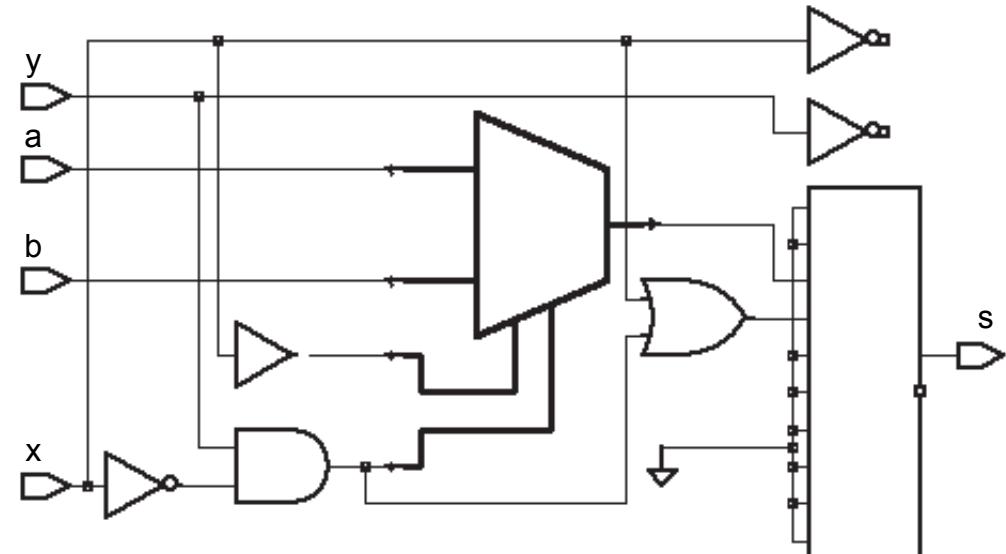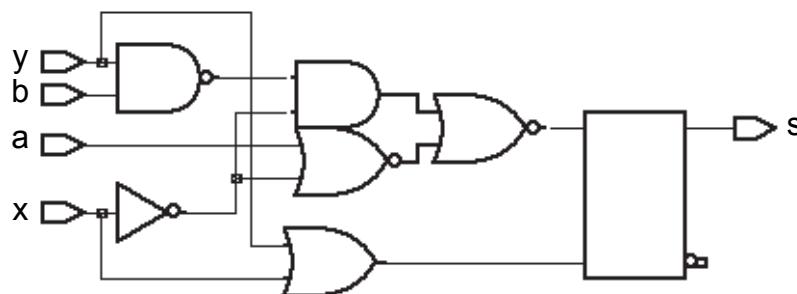





TTÜ1918



Complex assignments (#3)

- **Memory element generated!**

```
always begin
  @ (a or b or x or y);
    if (x==1)      s=a;
    else if (y==1) s=b;
    else           s=s;
end
```

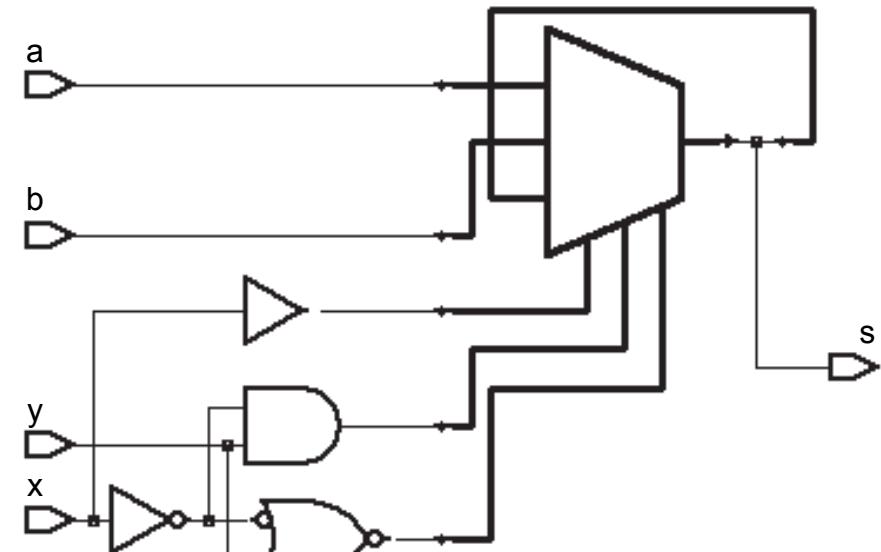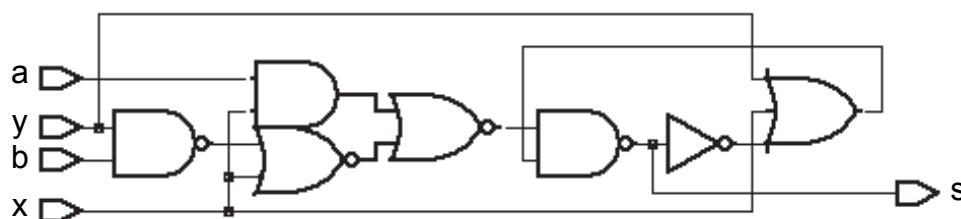



TTÜ 1918





Default values

- The default values inherited from type or subtype definitions
- The explicit initialization that is given when the object is declared
- A value assigned using a statement at the beginning of a process
- Only the last case is supported by synthesis tools!
- Usually, a part of the synthesizable code is devoted to set/reset constructions
- Default values can be used to guarantee that the signal always gets a new value

```
always begin
  @ (a or b or x or y);
  s = 0;
  if (x == 1)      s = a;
  else if (y == 1) s = b;
end
```
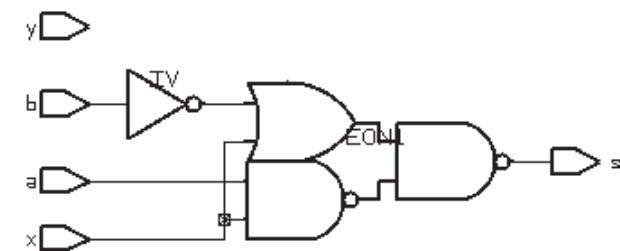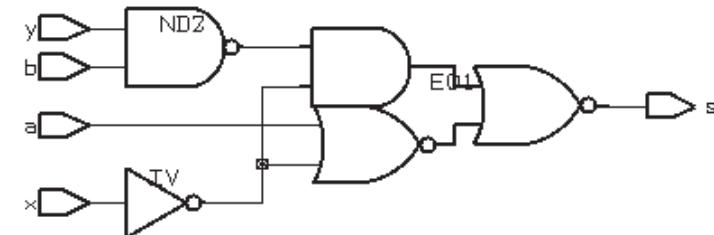
```
always begin
  @ (a or b or x or y);
  s = 'bx;
  if (x == 1)      s = a;
  else if (y == 1) s = b;
end
```





Latches & flip-flops


```
always @ (clk or d) if (clk) q = d; /* Latch */
```

```
always @ (posedge clk) q = d; /* Flip-flop */  
always @ (posedge clk) q <= d;
```

- **synchronous reset**

```
always @ (posedge clk)
  if (res==1) q = 0;
  else         q = d;
```

```
always begin  
    @ (posedge clk) ;  
    if (res==1) q = 0;  
    else q = d;  
end
```

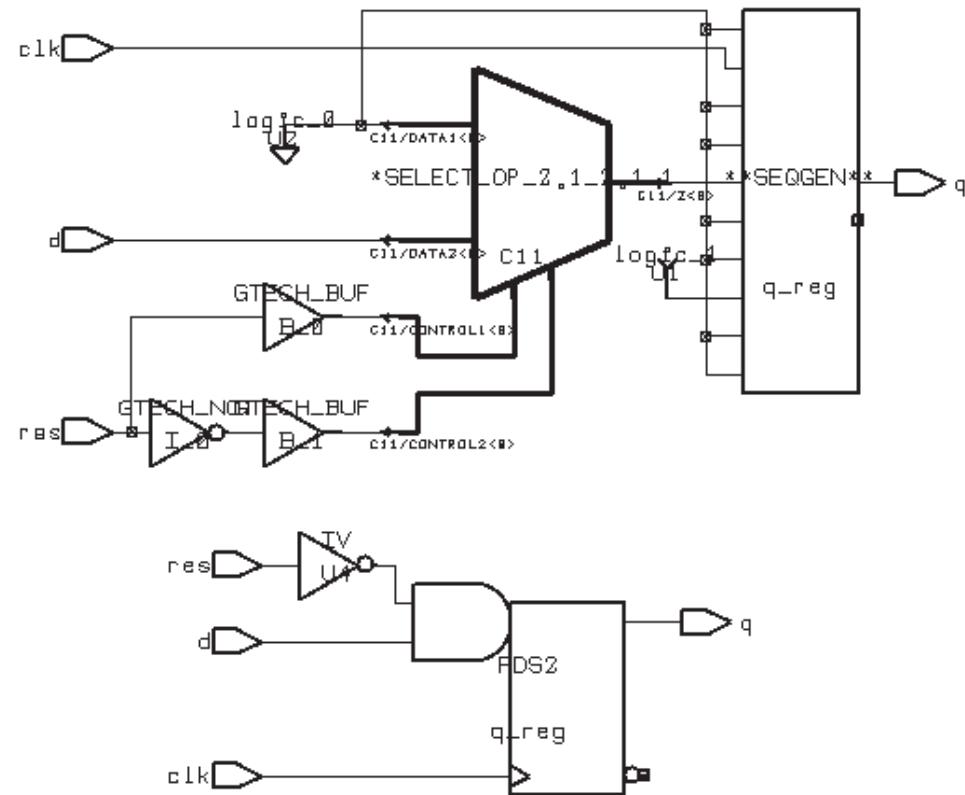



TTÜ1918




Flip-flops

- asynchronous reset

```
always
  @ (posedge res or
       posedge clk)
    if (res==1) q = 0;
    else         q = d;
```
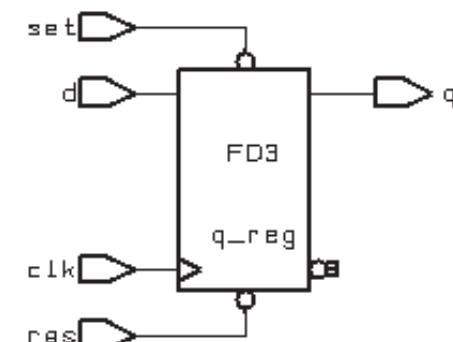
```
always
  @ (negedge res or
       negedge set or
       posedge clk)
    if (res==0)      q = 0;
    else if (set==0) q = 1;
    else             q = d;
```






Flip-flops

- asynchronous reset - the order of signals!

```
always @ (posedge res or posedge set or posedge clk)
    if (clk==1)      q = d;
    else if (set==1) q = 1;
    else             q = 0;
```

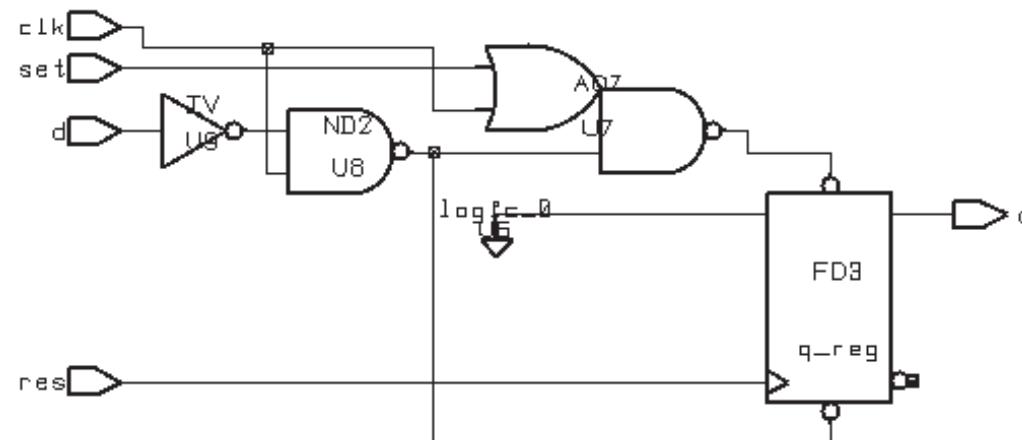




TTÜ1918




Blocking versus non-blocking
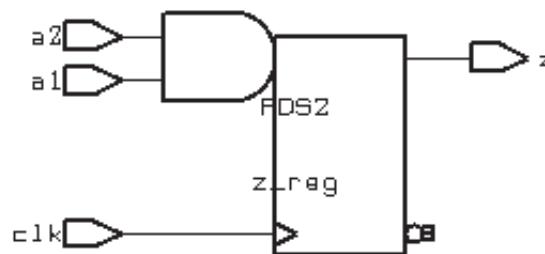
```
module sig_var_b (clk, a1, a2, z);
    input clk, a1, a2;
    output z;    reg z;    reg a3;
    always @ (posedge clk) begin
        a3 = a1 & a2;
        z <= a3;
    end
endmodule // sig_var_b
```


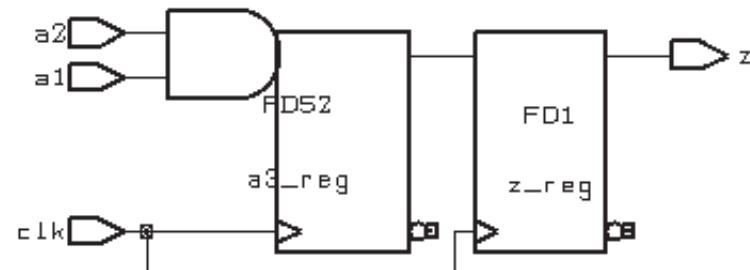
```
module sig_var_n (clk, a1, a2, z);
    input clk, a1, a2;
    output z;    reg z;    reg a3;
    always @ (posedge clk) begin
        a3 <= a1 & a2;
        z <= a3;
    end
endmodule // sig_var_n
```




Compare – signal versus variable in VHDL

```
process (CLK)
    variable A3 : BIT;
begin
    if CLK'event and CLK='1' then
        A3 := A1 and A2;
        Z <= A3;
    end if;
end process;
```

```
signal A3 : BIT;
-- ...
process (CLK) begin
    if CLK'event and CLK='1' then
        A3 <= A1 and A2;
        Z <= A3;
    end if;
end process;
```

Data-part, control-part & FSM

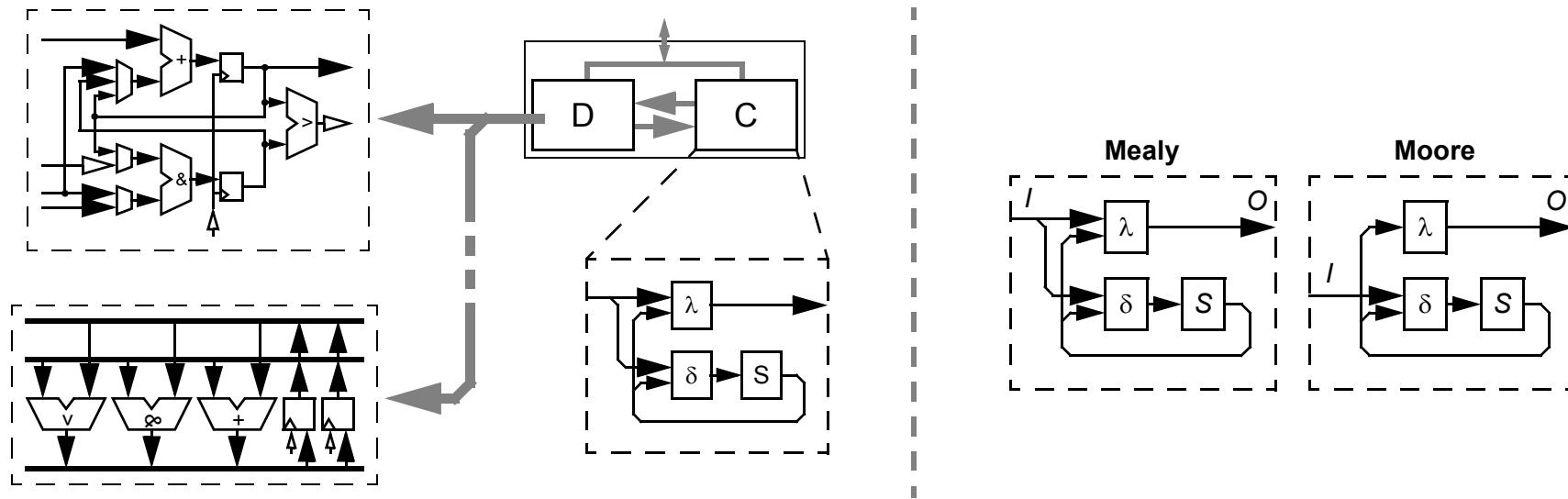


- **one unit – one process**
 - functional units – combinational processes [all inputs in the sensitivity list]
 - storage units – clocked processes [activation at clock edge]
- **FSM: $M = (S, I, O, \delta, \lambda)$** – process per block
- **Three processes** – (1) transition function, (2) output function, (3) state register
- **Two processes** – (1) merged transition and output functions, (2) state register [Mealy]
- **One process** – buffered outputs! [Moore]




FSM - description styles

Three processes (modulo-4 counter)

```
module counter03 ( clk, resetn, three );
    input clk, resetn;
    output three;    reg three;
    reg [1:0] pres_state, next_state;
    always @(posedge clk) // State memory
        pres_state <= next_state;
    // Next state function
    always @ (resetn or pres_state) begin
        if (resetn==0) next_state = 0;
        else case (pres_state)
            0, 1, 2: next_state = pres_state + 1;
            3:       next_state = 0;
        endcase
    end
    always @ (pres_state) // Output function
        if (pres_state==3) three = 1;
        else               three = 0;
endmodule
```

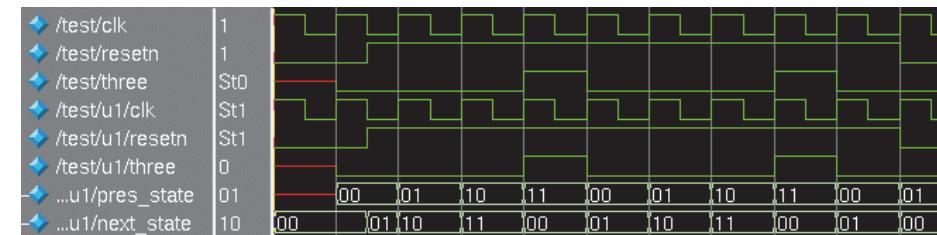

23 gates / 4.36 ns

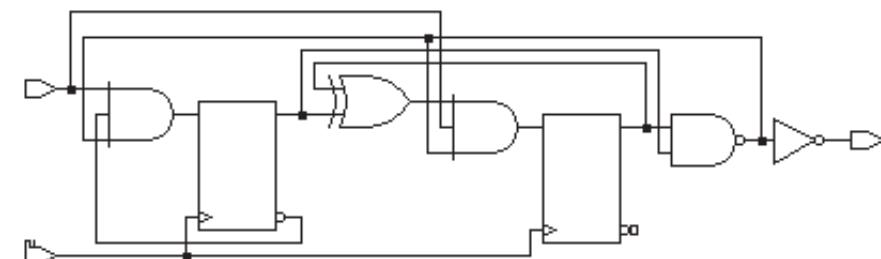




TTÜ1918




FSM - description styles

Two processes (modulo-4 counter)

```
module counter03 ( clk, resetn, three );
    input clk, resetn;
    output three;    reg      three;
    reg [1:0] pres_state, next_state;
    always @ (posedge clk) // State memory
        pres_state = next_state;
    // Next state & output functions
    always @ (resetn or pres_state) begin
        three = 0;
        if (resetn==0)   next_state = 0;
        else
            case (pres_state)
                0, 1, 2: next_state = pres_state + 1;
                3: begin next_state = 0; three = 1; end
            endcase
    end
endmodule
```

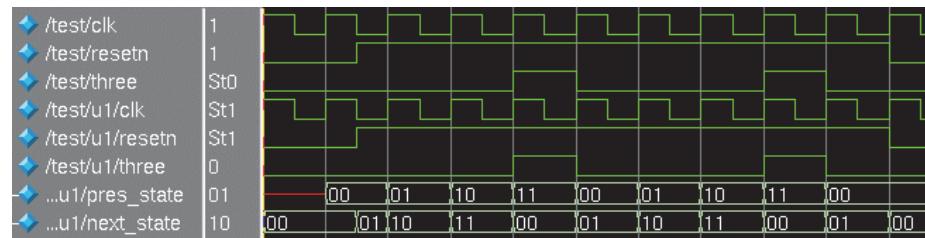

24 gates / 4.36 ns

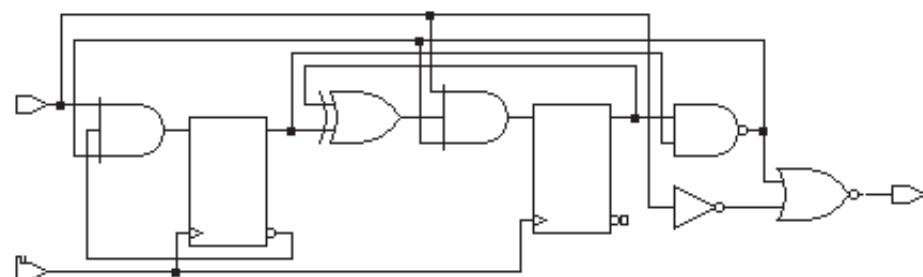



TTÜ1918




FSM - description styles


One process (modulo-4 counter)

```
module counter03 ( clk, resetn, three );
    input clk, resetn;
    output three;    reg three;
    reg [1:0] state;
    always @(posedge clk) begin
        three = 0;
        if (resetn==0) state = 0;
        else case (state)
            0, 1: state = state + 1;
            2: begin state = state + 1; three = 1; end
            3: state = 0;
        endcase
    end
endmodule

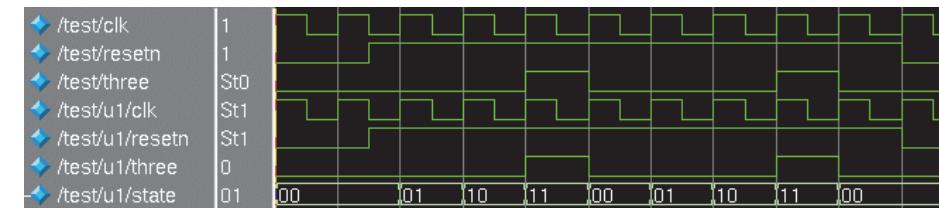// Another version
// to begin the always block
always begin @(posedge clk);
    three = 0; // and so on...
```



38 gates / 5.68 ns

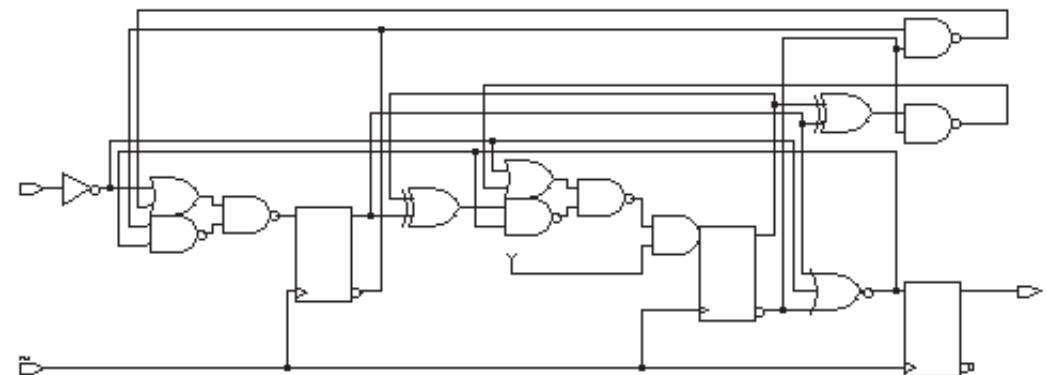



TTÜ1918




for-loop versus while-loop?

- Is tool dependent!
 - Design Compiler (Synopsys) & ISE (Xilinx): *for* - parallel, *while* - parallel
 - No multiple waits!

```
always @ (a or b) begin
    for (i=0;i<4;i=i+1)
        x[i] = a[i] & b[i];
end
```
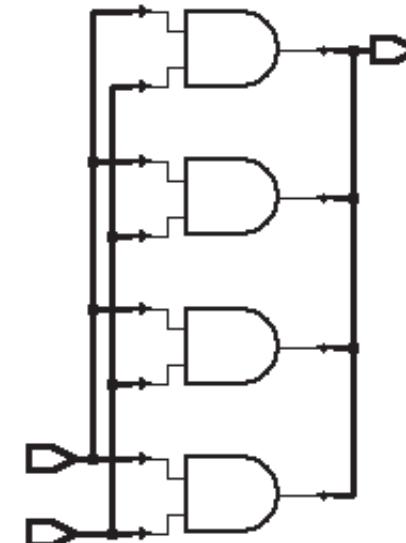
```
always @ (a or b) begin
    i = 0;
    while (i<4) begin
        x[i] = a[i] & b[i];
        i = i + 1;
    end
end
```





Behavioral RTL vs. “pure” RTL

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_arith.all;
entity test is
    port ( a, b, c: in unsigned(7 downto 0);
           x: in unsigned(2 downto 0);
           o: out unsigned(7 downto 0) );
end test;
architecture bhv of test is begin
process (a, b, c, x)
    constant x2: unsigned(2 downto 0):="010";
    constant x3: unsigned(2 downto 0):="011";
    constant x6: unsigned(2 downto 0):="110";
begin
    if      x=x2 then   o <= a+b;
    elsif  x=x3 then   o <= a+c;
    elsif  x=x6 then   o <= b+c;
    else               o <= (others=>'0');
    end if;
end process;
end architecture bhv;

module test (a, b, c, x, o);
    input [7:0] a, b, c;
    input [2:0] x;
    output [7:0] o; reg [7:0] o;
    always @ (a or b or c or x)
        if      (x==2)   o <= a+b;
        else if (x==3)   o <= a+c;
        else if (x==6)   o <= b+c;
        else               o <= 0;
endmodule // test
```




TTÜ1918




Behavioral RTL vs. “pure” RTL


VHDL

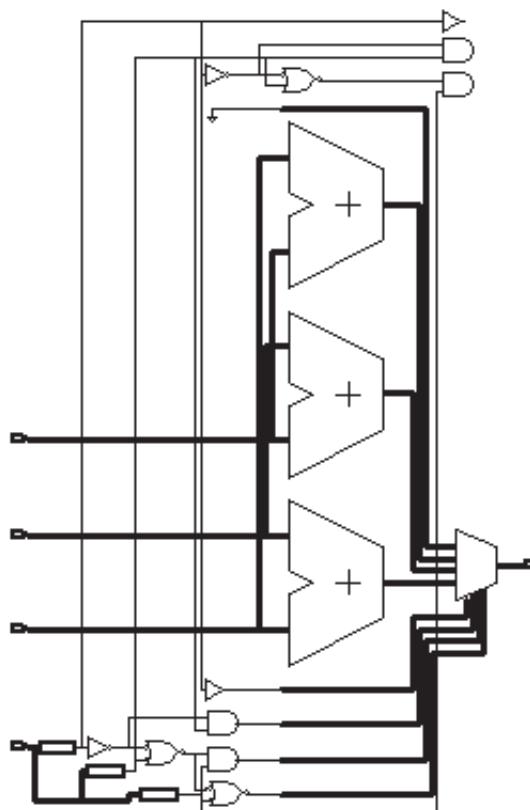

Verilog

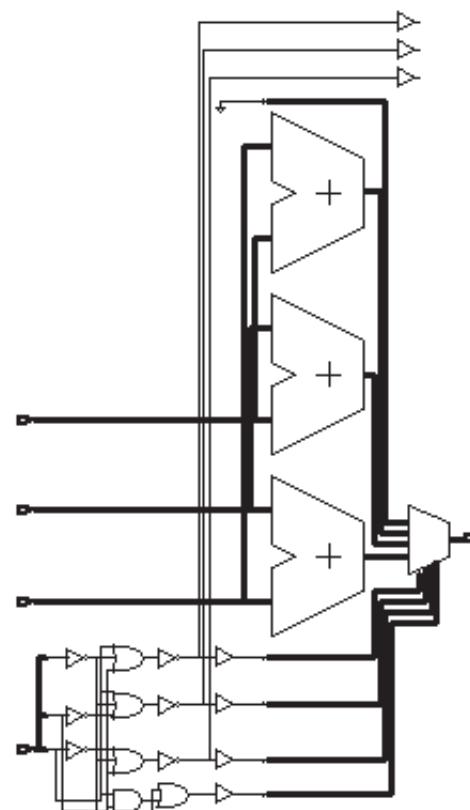

220 gates / 11.57 ns

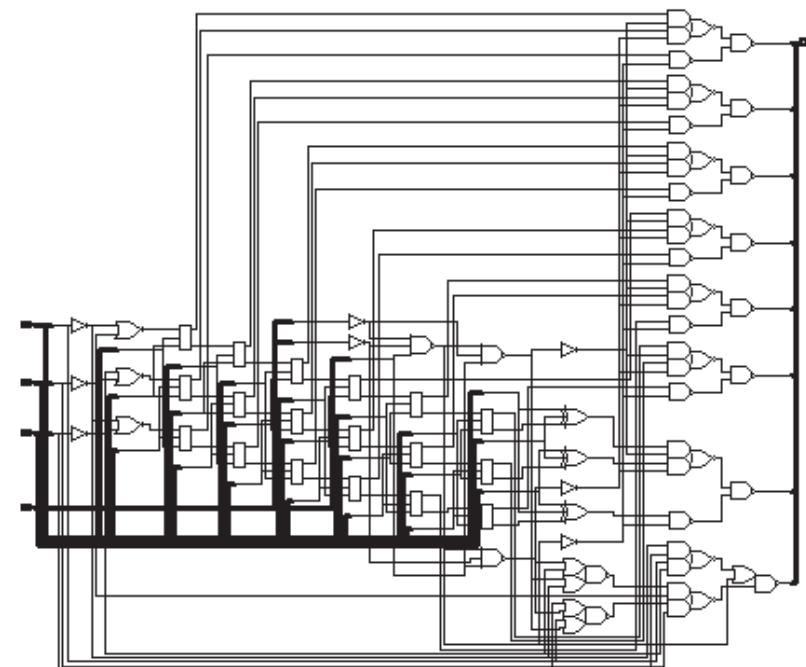




TTÜ1918




Behavioral RTL vs. “pure” RTL
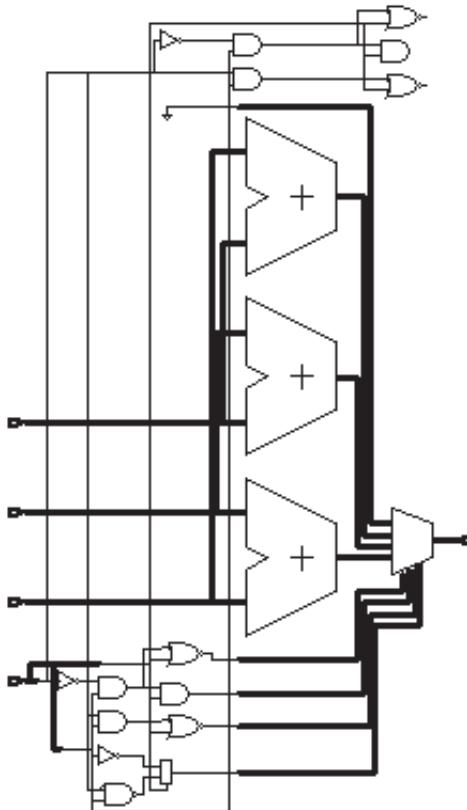
```
architecture bhv2 of test is begin
process (a, b, c, x) begin
  case x is
    when "010" => o <= a+b;
    when "011" => o <= a+c;
    when "110" => o <= b+c;
    when others => o <= (others=>'0');
  end case;
end process;
end architecture bhv2;
```



220 gates / 11.57 ns

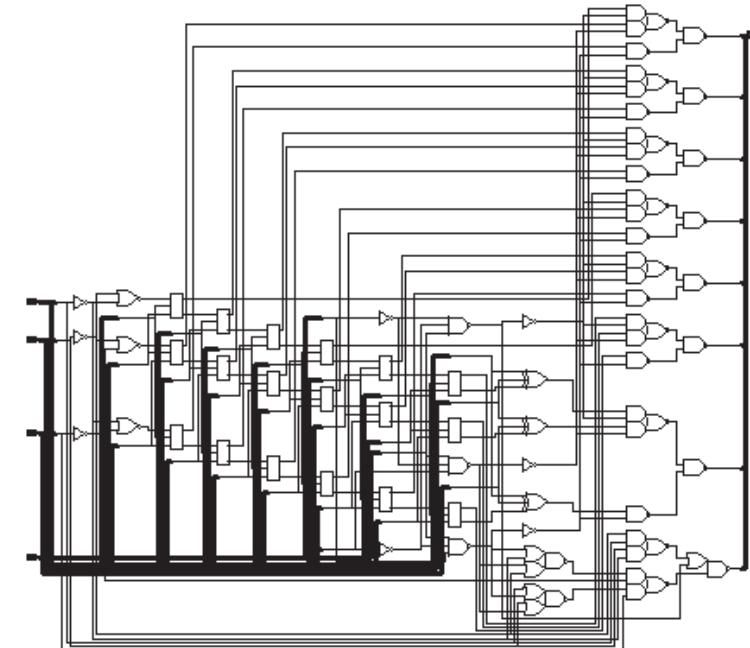



Behavioral RTL vs. “pure” RTL

```
architecture rtl of test is
    signal a1, a2: unsigned(7 downto 0);
    signal dc: unsigned(1 downto 0);
begin
dec: process (x) begin
    case x is
        when "010" => dc <= "01";
        when "011" => dc <= "10";
        when "110" => dc <= "11";
        when others => dc <= "00";
    end case;
end process dec;
m1: process (a, b, dc) begin
    case dc is
        when "01" => a1 <= a;
        when "10" => a1 <= a;
        when "11" => a1 <= b;
        when others => a1 <= (others=>'0');
    end case;
end process m1;
m2: process (b, c, dc) begin
    -- ...
end process m2;
o <= a1 + a2;
end architecture rtl;


module test (a, b, c, x, o);
    input [7:0] a, b, c;
    input [2:0] x;
    output [7:0] o;
    reg [7:0] a1, a2;
    reg [2:0] dc;
    always @ (x)
        if (x==2) dc = 1;
        else if (x==3) dc = 2;
        else if (x==6) dc = 3;
        else dc = 0;
    always @ (a or b or dc)
        if (dc==1) a1 = a;
        else if (dc==2) a1 = a;
        else if (dc==3) a1 = b;
        else a1 = 0;
    always @ (b or c or dc)
        if (dc==1) a2 = b;
        else if (dc==2) a2 = c;
        else if (dc==3) a2 = c;
        else a2 = 0;
    assign o = a1+a2;
endmodule // test
```



TTÜ1918



Behavioral RTL vs. “pure” RTL

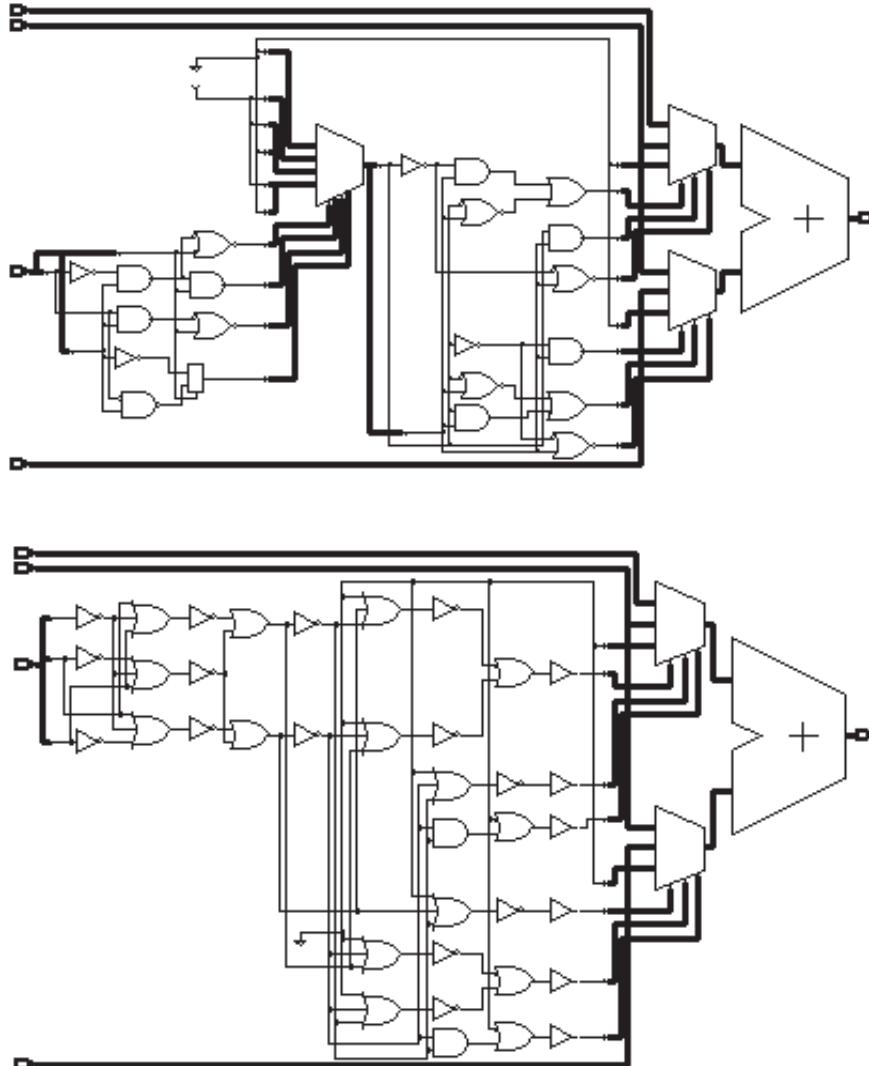

VHDL

117 gates / 19.2 ns

Verilog



TTÜ1918



Adder / Subtractor

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_arith.all;
entity add_sub is
  port ( a, b: in unsigned(7 downto 0);
         x: in std_logic;
         o: out unsigned(7 downto 0) );
end add_sub;
architecture bhv of add_sub is begin
process (a, b, x) begin
  if x='0' then o <= a+b;
  else          o <= a-b;  end if;
end process;
end architecture bhv;
```


```
module add_sub (a, b, x, o);
  input [7:0] a, b;
  input x;
  output [7:0] o;
  assign o = x==0 ? a+b : a-b;
endmodule // add_sub
```

145 gates / 11.64 ns

```
architecture dfl of test5 is
  signal a1, b1, o1: unsigned(8 downto 0);
begin
  a1 <= a & '1';
  b1 <= b & '0' when x='0' else
    unsigned(not std_logic_vector(b)) &
    '1';
  o1 <= a1+b1;
  o <= o1(8 downto 1);
end architecture dfl;

/* ... */
assign {o,t} = {a,1'b1} +
  ( x==0 ? {b,1'b0} : {~b,1'b1} );
```

87 gates / 12.45 ns

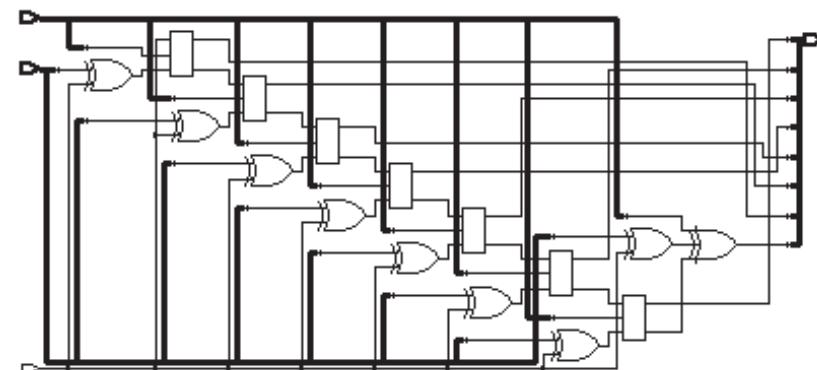



TTÜ1918




Adders & Subtracters

```
a1 <= '0' & a & '1';
b1 <= '0' & b & ci;
o1 <= a1 + b1;
o <= o1(8 downto 1);
co <= o1(9);

assign {co,o,t} = {1'b0,a,1'b1} +
{1'b0,b,ci};
```

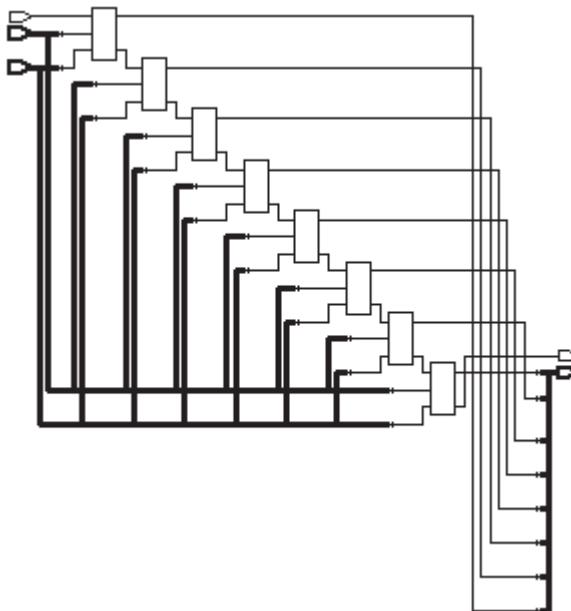
64 g. / 10.66 ns [60 g. / 10.08 ns w/o ci/co]



```
a1 <= '0' & a & '1';
b1 <= '0' &
unsigned(not std_logic_vector(b)) & ci;
o1 <= a1 + b1;
o <= o1(8 downto 1);
co <= o1(9);

assign {co,o,t} = {1'b0,a,1'b1} +
{1'b0,~b,ci};
```

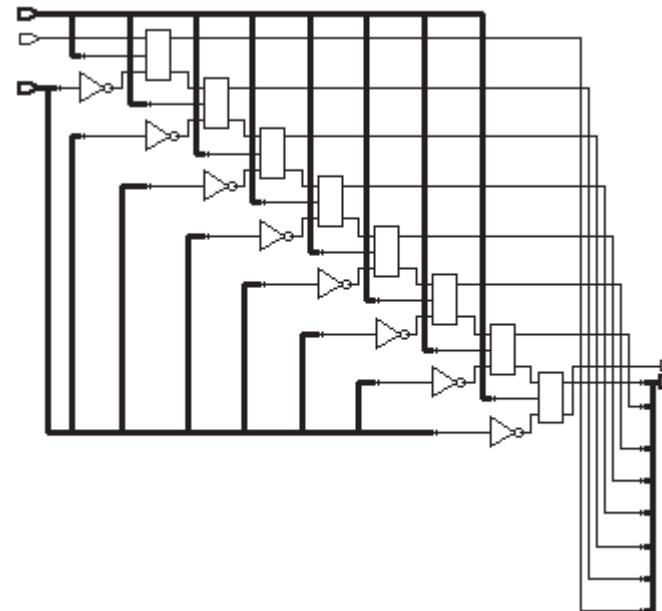72 g. / 10.62 ns [66 g. / 10.35 ns w/o ci/co]





GCD (Greatest Common Divisor) example

- Specification ~~ behavioral description
 - input/output timing fixed – handshaking signals & clock

```
process -- gcd-bhv.vhdl
    variable x, y: unsigned(15 downto 0);
begin
    -- Wait for the new input data
    wait on clk until clk='1' and rst='0';
    x := xi;    y := yi;    rdy <= '0';
    wait on clk until clk='1';
    -- Calculate
    while x /= y loop
        if x < y then y := y - x;
        else           x := x - y;    end if;
    end loop;
    -- Ready
    xo <= x;    rdy <= '1';
    wait on clk until clk='1';
end process;
```

Problems

- inner loop not clocked
- complex wait statement
 - (- multiple wait statements)

What to look for?

- different synthesis tools
- minimizing resources
- maximizing performance

Target technologies – ASIC, FPGA

VHDL code & testbenches

<http://mini.pld.ttu.ee/~lrv/gcd/>



GCD example – synthesizable code?

- Clocked behavioral style

```
process -- gcd-bhvc.vhdl
  variable x, y: unsigned(15 downto 0);
begin
  -- Wait for the new input data
  while rst = '1' loop
    wait on clk until clk='1';
  end loop;
  x := xi;    y := yi;    rdy <= '0';
  wait on clk until clk='1';
  -- Calculate
  while x /= y loop
    if x < y then y := y - x;
    else           x := x - y;    end if;
    wait on clk until clk='1';
  end loop;
  -- Ready
  xo <= x;    rdy <= '1';
  wait on clk until clk='1';
end process;
```

ASIC: synthesizable

961 e.g. / 20.0 ns

2 sub-s, 2 comp-s

FPGA: non-synthesizable

wait statements in loops :(
explicit FSM needed :(:(

Possible trade-offs

- functional unit sharing
- universal functional units
- out-of-order execution



GCD example – behavioral FSM

```
process begin -- gcd-bfsm.vhdl
    wait on clk until clk='1';
    case state is
        -- Wait for the new input data
        when S_wait =>
            if rst='0' then
                x<=xi; y<=yi; rdy<='0'; state<=S_start;
            end if;
        -- Calculate
        when S_start =>
            if x /= y then
                if x < y then y <= y - x;
                else x <= x - y; end if;
                state<=S_start;
            else
                xo<=x; rdy<='1'; state<=S_ready;
            end if;
        -- Ready
        when S_ready => state<=S_wait;
    end case;
end process;
```

ASIC: synthesizable

911 e.g. / 19.4 ns

2 sub-s, 2 comp-s

FPGA: synthesizable

108 SLC / 9.9 ns

2 sub-s, 2 comp-s

Can it be made better?

Again the possible trade-offs

- functional unit sharing

one operation per clock step

- universal functional units

$A < B \equiv A - B < 0$ / $A = B \equiv A - B = 0$

- out-of-order execution

subtracting first then deciding



GCD example – universal functional units?


- $A < B \Rightarrow A - B < 0$ / $A = B \Rightarrow A - B = 0$

```
-- Three operations:  
-- subtraction, and  
-- comparisons not-equal &  
-- less-than  
xo <= xi - yi;  
  
ne <= '1' when xi /= yi else '0';  
  
lt <= '1' when xi < yi else '0';
```

ASIC: 209 e.g. / 19.9 ns


FPGA: 20 SLC / 12.1 ns

three adder chains!

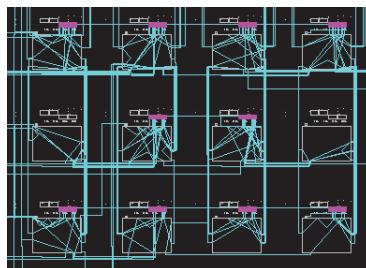

```
-- ALU - subtracting and then comparing  
x_out <= xi - yi;      xo <= x_out;  
process (x_out)  
    variable or_tmp: unsigned(15 downto 0);  
begin  
    or_tmp(15) := x_out(15);  
    for i in 14 downto 0 loop  
        or_tmp(i) := or_tmp(i+1) or x_out(i);  
    end loop;  
    ne <= to_bit(or_tmp(0));  
end process;  
lt <= to_bit(x_out(15));
```

ASIC: 148 e.g. / 21.8 ns / **FPGA:** 12 SLC / 14.6 ns

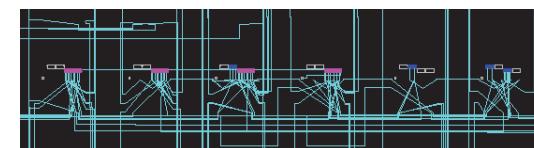



TTÜ1918



GCD example – design space exploration

- Different solutions – <http://mini.pld.ttu.ee/~lrv/gcd/>
 - gcd-bhv.vhdl – pure behavioral description, non-synthesizable
 - gcd-bhvc.vhdl – fully clocked behavioral style, some synthesis tools can handle
 - gcd-bfsm.vhdl – so called behavioral FSM (explicit FSM & behavioral data-path), synthesizable (but how efficient it is?)
 - gcd-rtl1.vhdl – single ALU, 3 clock cycles per iteration –
1) “not equal?”, 2) “less than?”, 3) subtract
 - gcd-rtl2.vhdl – single ALU, 2 clock cycles per iteration –
1) “not equal?” and “less than?”, 2) subtract
 - gcd-rtl3.vhdl – comparator (less than) controls subtraction, 1 clock cycle per iteration – small but slow (sequential) data-path
 - gcd-rtl4.vhdl – out-of-order execution – both subtractions are calculated first then the decision is made (one subtracter compares for “less than”, another for “not equal”)
 - gcd-rtl5.vhdl – out-of-order execution – both subtractions are calculated first then the decision is made (one subtracter compares for “less than” but separate “not equal”)



GCD example – single ALU, 2 clock cycles per iteration

gcd-rtl2.vhdl

```
-- Next state function of the FSM
process (state, rst, alu_ne, alu_lt) begin
    ena_x <= '0';      ena_y <= '0';      ena_r <= '0';
    set_rdy <= '0';    xi_yi_sel <= '0';    sub_y_x <= '0';
    next_state <= state;
    case state is
        when S_wait =>      -- Wait for the new input data
            if rst='0' then
                xi_yi_sel <= '1';  ena_x <= '1';  ena_y <= '1';
                next_state <= S_start;
            end if;
        when S_start =>      -- Loop: ready?
            if alu_ne='1' then
                if alu_lt='1' then  next_state <= S_sub_y_x;
                else             next_state <= S_sub_x_y;  end if;
            else               next_state <= S_ready;
            end if;
        when S_sub_y_x =>    -- Loop: y-x
            ena_y <= '1';      sub_y_x <= '1';
            next_state <= S_start;
        when S_sub_x_y =>    -- Loop: x-y
            ena_x <= '1';      sub_y_x <= '0';
            next_state <= S_start;
        when S_ready =>      -- Ready
            ena_r <= '1';      set_rdy <= '1';
            next_state <= S_wait;
    end case;
end process;

-- ALU: subtract / less-than / not-equal
alu_o <= alu_1 - alu_2;
alu_lt <= to_bit(alu_o(15));
process (alu_o)
    variable or_tmp: unsigned(15 downto 0);
begin
    or_tmp(15) := alu_o(15);
    for i in 14 downto 0 loop
        or_tmp(i) := or_tmp(i+1) or alu_o(i);
    end loop;
    alu_ne <= to_bit(or_tmp(0));
end process;

-- Multiplexers
x_i <= xi when xi_yi_sel='1' else alu_o;
y_i <= yi when xi_yi_sel='1' else alu_o;
alu_1 <= y when sub_y_x='1' else x;
alu_2 <= x when sub_y_x='1' else y;

-- Registers
process begin
    wait on clk until clk='1';
    state <= next_state;
    if ena_x='1' then x <= x_i; end if;
    if ena_y='1' then y <= y_i; end if;
    if ena_r='1' then xo <= x; end if;
    rdy <= set_rdy;
end process;
```



GCD example – out-of-order execution (2 sub-s)

gcd-rtl5.vhdl

```
-- Next state function of the FSM
process (state, rst, alu_ne) begin
    ena_xy <= '0';      ena_r <= '0';
    set_rdy <= '0';      xi_yi_sel <= '0';
    next_state <= state;
    case state is
        -- Wait for the new input data
        when S_wait =>
            if rst='0' then
                xi_yi_sel <= '1';    ena_xy <= '1';
                next_state <= S_start;
            end if;
        -- Calculate
        when S_start =>
            if alu_ne='1' then
                ena_xy <= '1';
                next_state <= S_start;
            else
                ena_r <= '1';      set_rdy <= '1';
                next_state <= S_ready;
            end if;
        -- Ready
        when S_ready =>
            ena_r <= '1';      set_rdy <= '1';
            next_state <= S_wait;
        end case;
    end process;

-- Subtracter (x-y) / comparator (x<y)
alu_o1 <= x - y;
sub_y_x <= '1' when alu_o1(alu_o1'high)='1' else '0';

-- Subtracter (y-x)
alu_o2 <= y - x;

-- Comparator (y=/=x)
alu_ne <= '1' when x /= y else '0';

-- Multiplexers
x_i <= xi when xi_yi_sel='1' else alu_o1;
y_i <= yi when xi_yi_sel='1' else alu_o2;
ena_x <= '1' when (sub_y_x='0' and ena_xy='1') or
                  xi_yi_sel='1' else '0';
ena_y <= '1' when (sub_y_x='1' and ena_xy='1') or
                  xi_yi_sel='1' else '0';

-- Registers
process begin
    wait on clk until clk='1';
    state <= next_state;
    if ena_x='1' then    x <= x_i;    end if;
    if ena_y='1' then    y <= y_i;    end if;
    if ena_r='1' then    xo <= x;    end if;
    rdy <= set_rdy;
end process;
```



TTÜ 1918



GCD example – synthesis results

Technology	FPGA				ASIC			
	50 MHz		100 MHz		50 MHz		25 MHz	
	[SLC]	[ns]	[SLC]	[ns]	[e.g.]	[ns]	[e.g.]	[ns]
gcd-bhv ²⁾	93	17.3	-	-	1141	20.0	-	-
gcd-bhvc	-	-	-	-	961	20.0	977	31.1
gcd-bfsm	108	9.9	108	9.4	911	19.4	984	30.8
gcd-rtl1	50	10.8	50	9.7	986	19.8	883	32.4
gcd-rtl2	48	10.8	48	10.0	931	19.9	882	32.3
gcd-rtl3	58	17.0	58	14.6	1134	20.0	928	40.0
gcd-rtl4	78	12.6	78	9.0	976	19.9	928	29.0
gcd-rtl5	58	8.0	58	7.6	915	20.0	932	26.9

¹⁾ Clock period was the only constraint


²⁾ gcd-bhv was synthesized using the help of prototype HLS tool xTractor



TTÜ1918



GCD example – why such differences?

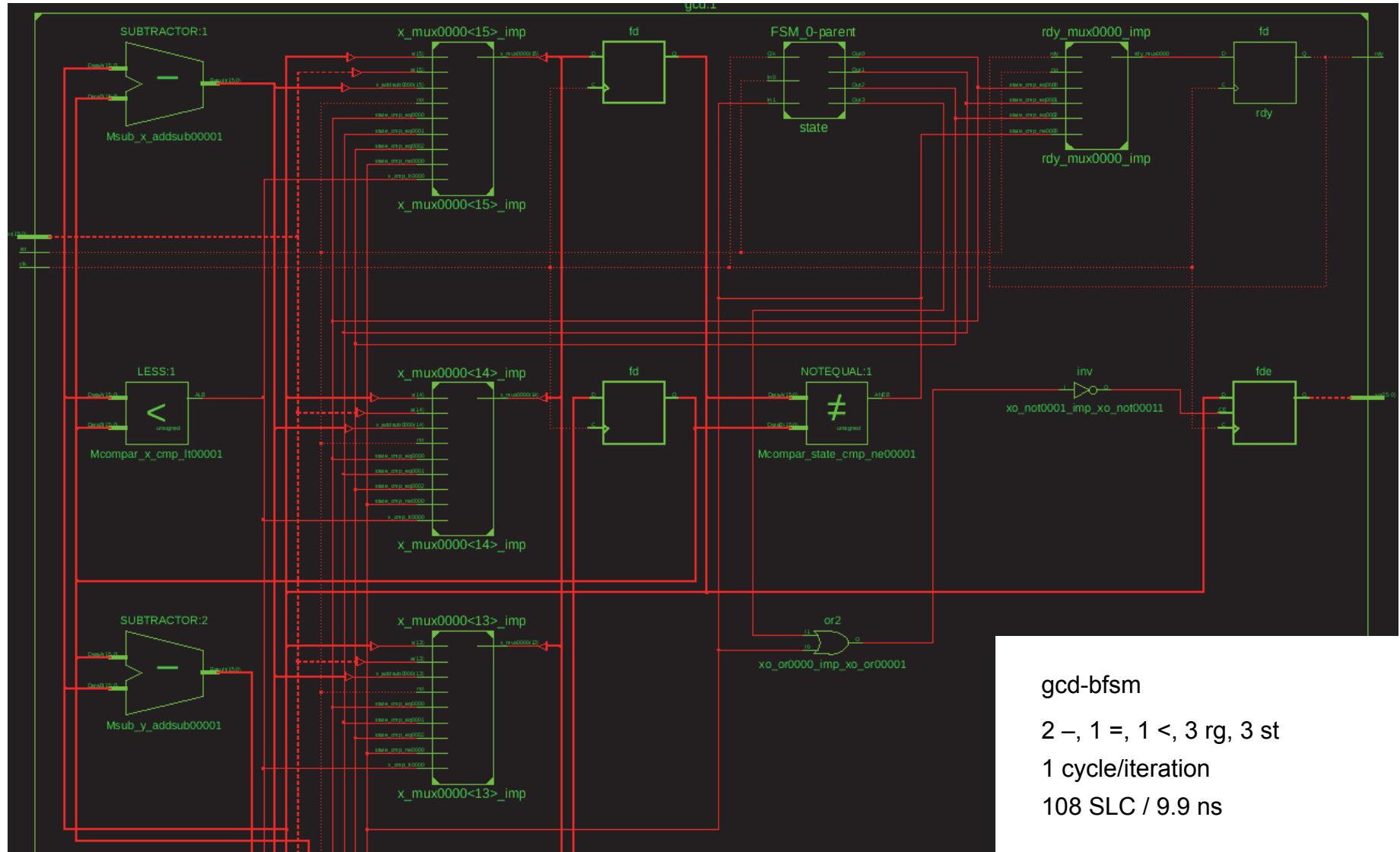




TTÜ1918




GCD example – why such differences?

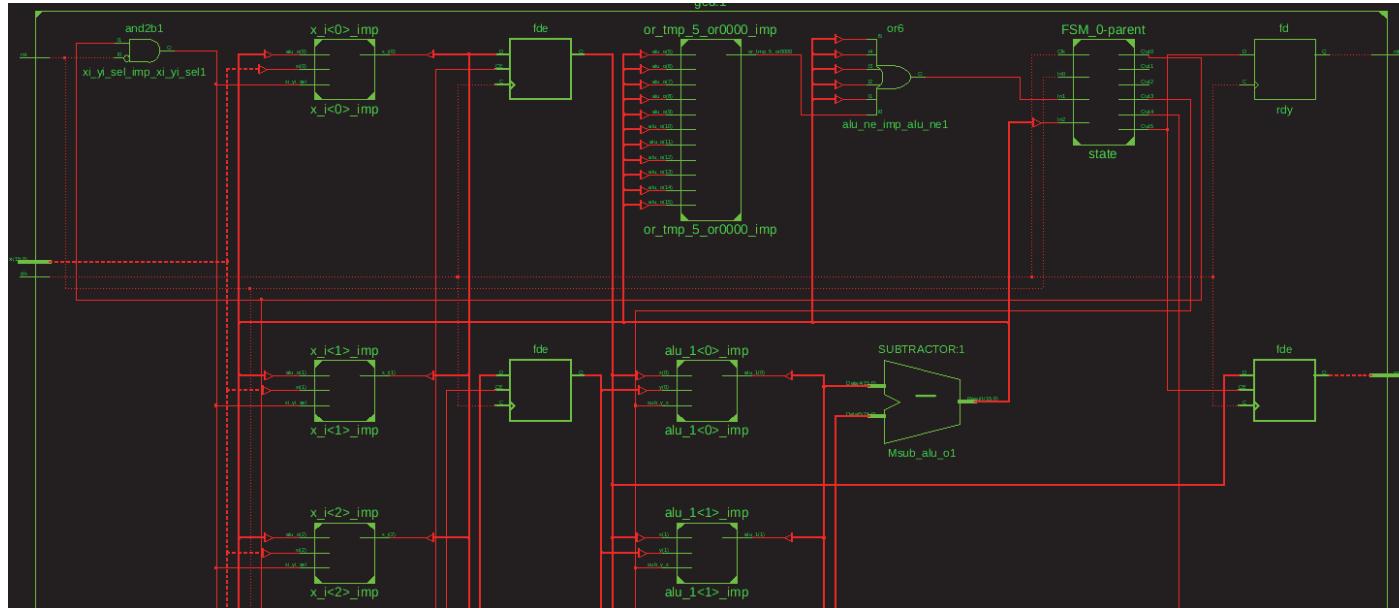

gcd-rtl1

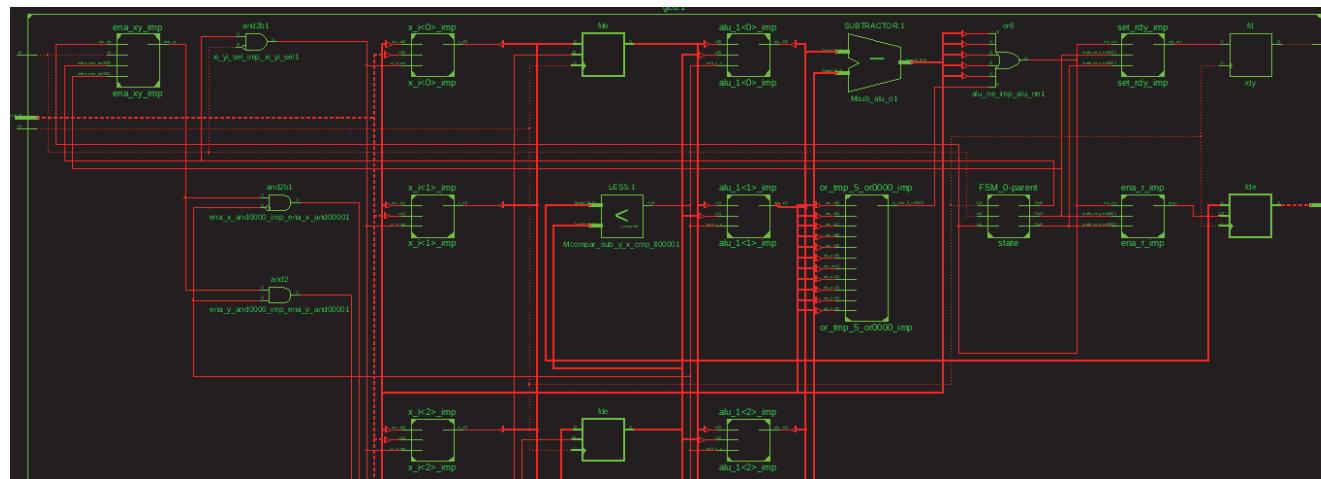1 ALU, 3 rg, 6 st
3 cycles/iteration
50 SLC / 10.8 ns



gcd-rtl2

1 ALU, 3 rg, 5 st
2 cycles/iteration
48 SLC / 10.8 ns

gcd-rtl3


1 –, 1 <, 3rg, 3st
1 cycle/iteration
58 SLC / 17.0 ns



TTÜ1918



GCD example – why such differences?

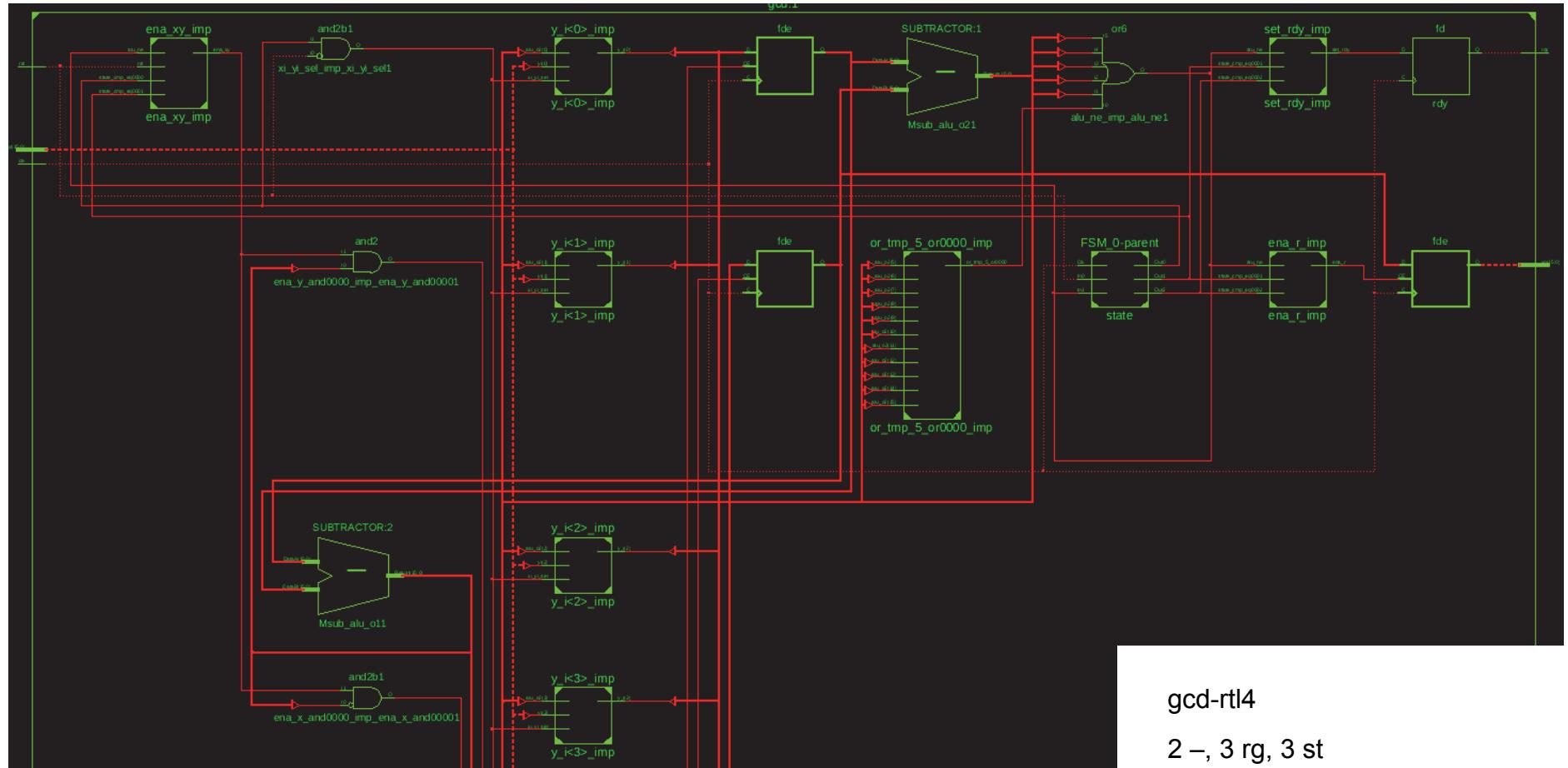

gcd-rtl4

2 –, 3 rg, 3 st

1 cycle/iteration


78 SLC / 12.6 ns



TTÜ1918



GCD example – why such differences?

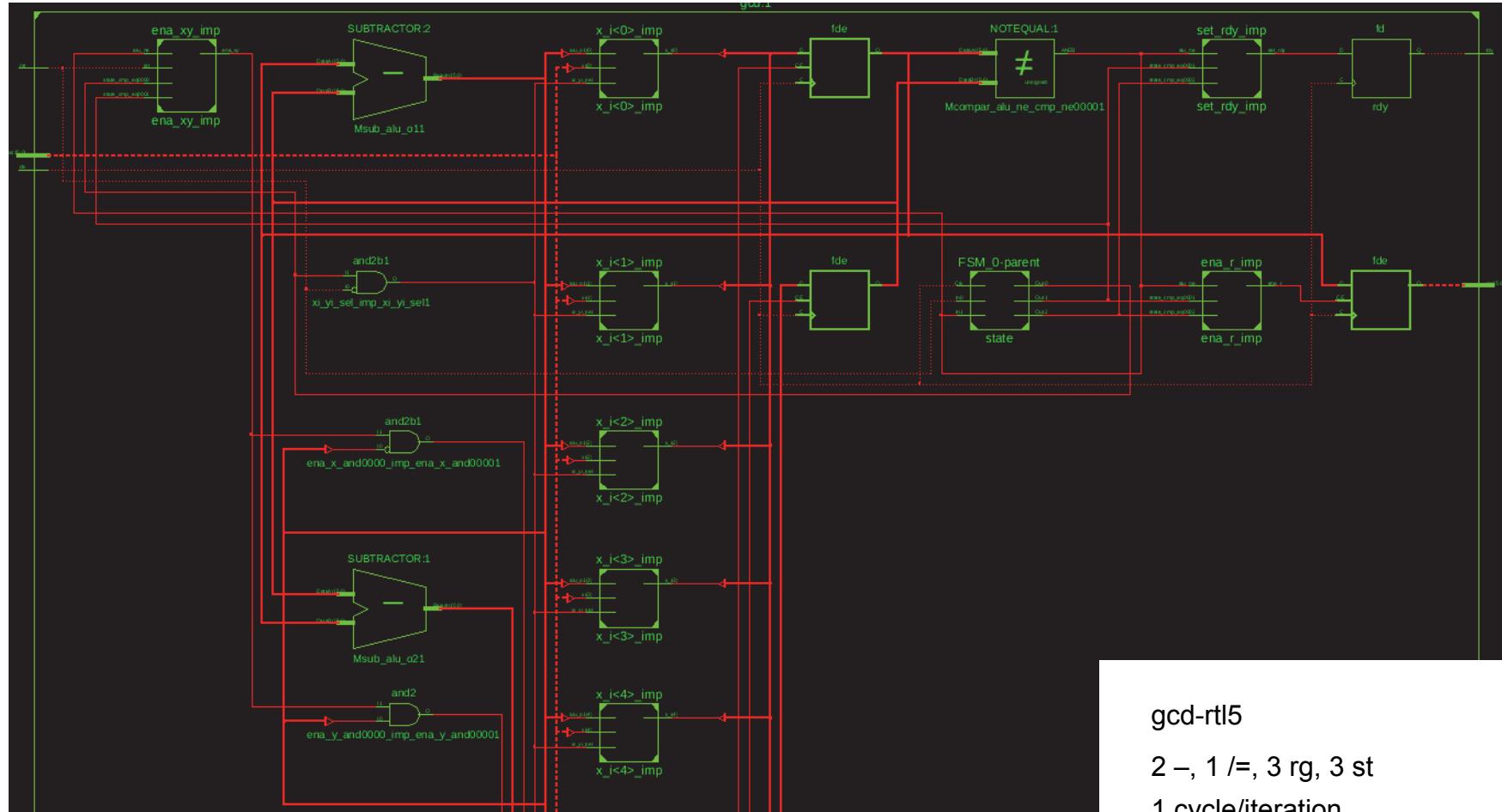

gcd-rtl5

2 –, 1 !=, 3 rg, 3 st

1 cycle/iteration

58 SLC / 8.0 ns