



Implementing an example algorithm

- **Algorithm as a program**
 - operations – data-part
 - sequence and conditions – control-part
- **GCD (Greatest Common Divisor)**

```
while ( x != y ) {
    if ( x < y ) y = y - x;
    else      x = x - y;
}
```

 - operations – comparisons and subtraction
 - implementing an operation?
 - $A < B \implies A - B < 0$ / $A \neq B \implies A - B \neq 0$ – only subtractor is needed?!
 - the same hardware for all operations or calculating in parallel?
 - speed or size? [and is it a problem at all?]



GCD (Greatest Common Divisor)

- Specification ~~ behavioral description
 - input/output timing fixed – control signals & clock

```
process -- gcd-bhv.vhdl
  variable x, y: unsigned(15 downto 0);
begin
  -- Wait for the new input data
  wait on clk until clk='1' and rst='0';
  x := xi;    y := yi;    rdy <= '0';
  wait on clk until clk='1';
  -- Calculate
  while x /= y loop
    if x < y then y := y - x;
    else        x := x - y;    end if;
  end loop;
  -- Ready
  xo <= x;    rdy <= '1';
  wait on clk until clk='1';
end process;
```

Problems

- inner loop not clocked
- complex wait statement
- (- multiple wait statements)

What to look for?

- different synthesis tools
- minimizing resources
- maximizing performance

Target technologies – ASIC, FPGA

VHDL code & testbenches

<https://ati.ttu.ee/~lrv/gcd/gcd.html>

GCD – synthesizable code?

- Clocked behavioral style

```
process -- gcd-bhvc.vhdl
    variable x, y: unsigned(15 downto 0);
begin
    -- Wait for the new input data
    while rst = '1' loop
        wait on clk until clk='1';
    end loop;
    x := xi;    y := yi;    rdy <= '0';
    wait on clk until clk='1';
    -- Calculate
    while x /= y loop
        if x < y then y := y - x;
        else          x := x - y;    end if;
        wait on clk until clk='1';
    end loop;
    -- Ready
    xo <= x;    rdy <= '1';
    wait on clk until clk='1';
end process;
```

ASIC: synthesizable

961 e.g. / 20.0 ns

2 sub-s, 2 comp-s

FPGA: non-synthesizable

wait statements in loops :(
explicit FSM needed :(

Possible trade-offs

- functional unit sharing
- universal functional units
- out-of-order execution

GCD – behavioral FSM

```
process begin -- gcd-bfsm.vhdl
    wait on clk until clk='1';
    case state is
        -- Wait for the new input data
    when S_wait =>
        if rst='0' then
            x<=xi; y<=yi; rdy<='0'; state<=S_start;
        end if;
        -- Calculate
    when S_start =>
        if x /= y then
            if x < y then y <= y - x;
            else x <= x - y; end if;
            state<=S_start;
        else
            xo<=x; rdy<='1'; state<=S_ready;
        end if;
        -- Ready
    when S_ready => state<=S_wait;
    end case;
end process;
```

ASIC: synthesizable

911 e.g. / 19.4 ns

2 sub-s, 2 comp-s

FPGA: synthesizable

108 SLC / 9.9 ns

2 sub-s, 2 comp-s

Can it be made better?

Again the possible trade-offs

- functional unit sharing
 - one operation per clock step
- universal functional units
 - $A < B \implies A - B < 0$ / $A \neq B \implies A - B \neq 0$
- out-of-order execution
 - subtracting first then deciding

GCD example – universal functional units?

- $A < B \implies A - B < 0$ / $A = B \implies A - B = 0$

-- Three operations:

-- subtraction, and

-- comparisons not-equal &

-- less-than

$x_o \leq x_i - y_i$;


$ne \leq '1'$ when $x_i \neq y_i$ else $'0'$;

$lt \leq '1'$ when $x_i < y_i$ else $'0'$;

ASIC: 209 e.g. / 19.9 ns

FPGA: 20 SLC / 12.1 ns

three adder chains!

 

-- ALU - subtracting and then comparing

$x_out \leq x_i - y_i$; $x_o \leq x_out$;

process (x_out)

 variable or_tmp: unsigned(15 downto 0);

begin

 or_tmp(15) := x_out(15);

 for i in 14 downto 0 loop

 or_tmp(i) := or_tmp(i+1) or x_out(i);


 end loop;

 ne <= to_bit(or_tmp(0));

end process;

lt <= to_bit(x_out(15));

 ASIC: 148 e.g. / 21.8 ns / FPGA: 12 SLC / 14.6 ns





GCD example – design space exploration

- Different solutions – <https://ati.ttu.ee/~lrv/gcd/gcd.html>
 - gcd-bhv.vhdl – pure behavioral description, non-synthesizable
 - gcd-bhvc.vhdl – fully clocked behavioral style, some synthesis tools can handle
 - gcd-bfsm.vhdl – so called behavioral FSM (explicit FSM & behavioral data-path), synthesizable (but how efficient it is?)
 - gcd-rtl1.vhdl – single ALU, 3 clock cycles per iteration –
 - 1) “not equal?”, 2) “less than?”, 3) subtract

```
#1#    a=x-y;    a!=0 ? #2# : #ready#
#2#    a=x-y;    a<0 ? #3# : #4#
#3#    y=y-x    /    #4#    x=x-y
```

- gcd-rtl2.vhdl – single ALU, 2 clock cycles per iteration –
 - 1) “not equal?” and “less than?”, 2) subtract

```
#1#    a=x-y;    a!=0 ? ( a<0 ? #2# : #3# ) : #ready#
#2#    y=y-x    /    #3#    x=x-y
```

GCD example – design space exploration (2)

- Different solutions – <https://ati.ttu.ee/~lrv/gcd/gcd.html>
- gcd-rtl3.vhdl – comparator (less than) controls subtraction, 1 clock cycle per iteration – small but slow (sequential) data-path

```
#1#    x<y ? y=y-x : ( a=x-y;    a!=0 ? x=x-y : #ready# )
```

- gcd-rtl4.vhdl – out-of-order execution – both subtractions are calculated first then the decision is made (one subtractor compares for “less than”, another for “not equal”)

```
#1#    a1=x-y;    a2=y-x;    a2!=0 ? ( a1<0 ? y=a2 : x=a1 ) : #ready#
```

- gcd-rtl5.vhdl – out-of-order execution – both subtractions are calculated first then the decision is made (one subtractor compares for “less than” but separate “not equal”)

```
#1#    a1=x-y;    a2=y-x;    x!=y ? ( a1<0 ? y=a2 : x=a1 ) : #ready#
```

GCD example – single ALU, 2 clock cycles per iteration

gcd-rtl2.vhdl

```
-- Next state function of the FSM
process (state, rst, alu_ne, alu_lt) begin
    ena_x <= '0';      ena_y <= '0';      ena_r <= '0';
    set_rdy <= '0';    xi_yi_sel <= '0';    sub_y_x <= '0';
    next_state <= state;
    case state is
    when S_wait =>      -- Wait for the new input data
        if rst='0' then
            xi_yi_sel <= '1';    ena_x <= '1';    ena_y <= '1';
            next_state <= S_start;
        end if;
    when S_start =>     -- Loop: ready?
        if alu_ne='1' then
            if alu_lt='1' then    next_state <= S_sub_y_x;
            else                  next_state <= S_sub_x_y;    end if;
        else                    next_state <= S_ready;
        end if;
    when S_sub_y_x =>    -- Loop: y-x
        ena_y <= '1';    sub_y_x <= '1';
        next_state <= S_start;
    when S_sub_x_y =>    -- Loop: x-y
        ena_x <= '1';    sub_y_x <= '0';
        next_state <= S_start;
    when S_ready =>     -- Ready
        ena_r <= '1';    set_rdy <= '1';
        next_state <= S_wait;
    end case;
end process;

-- ALU: subtract / less-than / not-equal
alu_o <= alu_1 - alu_2;
alu_lt <= to_bit(alu_o(15));
process (alu_o)
    variable or_tmp: unsigned(15 downto 0);
begin
    or_tmp(15) := alu_o(15);
    for i in 14 downto 0 loop
        or_tmp(i) := or_tmp(i+1) or alu_o(i);
    end loop;
    alu_ne <= to_bit(or_tmp(0));
end process;

-- Multiplexers
x_i <= xi when xi_yi_sel='1' else alu_o;
y_i <= yi when xi_yi_sel='1' else alu_o;
alu_1 <= y when sub_y_x='1' else x;
alu_2 <= x when sub_y_x='1' else y;

-- Registers
process begin
    wait on clk until clk='1';
    state <= next_state;
    if ena_x='1' then    x <= x_i;    end if;
    if ena_y='1' then    y <= y_i;    end if;
    if ena_r='1' then    xo <= x;    end if;
    rdy <= set_rdy;
end process;
```




GCD – comparator+subtractor, 1 clock cycle

gcd-rtl3.vhdl

```
-- Next state function of the FSM
process (state, rst, alu_ne) begin
    ena_xy <= '0';    ena_r <= '0';
    set_rdy <= '0';    xi_yi_sel <= '0';
    next_state <= state;
    case state is
        when S_wait =>    -- Wait for the new input data
            if rst='0' then
                xi_yi_sel <= '1';    ena_xy <= '1';
                next_state <= S_start;
            end if;
        when S_start =>    -- Calculate
            if alu_ne='1' then
                ena_xy <= '1';    next_state <= S_start;
            else
                ena_r <= '1';    set_rdy <= '1';
                next_state <= S_ready;
            end if;
        when S_ready =>    -- Ready
            ena_r <= '1';    set_rdy <= '1';
            next_state <= S_wait;
        end case;
    end process;

-- Comparator (less-than)
sub_y_x <= '1' when x < y else '0';

-- Subtractor (+not-equal)
alu_o <= alu_1 - alu_2;
process (alu_o)
    variable or_tmp: unsigned(15 downto 0);
begin
    or_tmp(15) := alu_o(15);
    for i in 14 downto 0 loop
        or_tmp(i) := or_tmp(i+1) or alu_o(i);
    end loop;
    alu_ne <= to_bit(or_tmp(0));
end process;

-- Multiplexers
x_i <= xi when xi_yi_sel='1' else alu_o;
y_i <= yi when xi_yi_sel='1' else alu_o;
alu_1 <= y when sub_y_x='1' else x;
alu_2 <= x when sub_y_x='1' else y;
ena_x <= '1' when (sub_y_x='0' and ena_xy='1') or
                  xi_yi_sel='1' else '0';
ena_y <= '1' when (sub_y_x='1' and ena_xy='1') or
                  xi_yi_sel='1' else '0';

-- Registers
process begin
    wait on clk until clk='1';
    state <= next_state;
    if ena_x='1' then    x <= x_i;    end if;
    if ena_y='1' then    y <= y_i;    end if;
    if ena_r='1' then    xo <= x;    end if;
    rdy <= set_rdy;
end process;
```

GCD example – out-of-order execution (2 sub-s)

gcd-rtl5.vhdl

```
-- Next state function of the FSM
process (state, rst, alu_ne) begin
    ena_xy <= '0';      ena_r <= '0';
    set_rdy <= '0';     xi_yi_sel <= '0';
    next_state <= state;
    case state is
        -- Wait for the new input data
        when S_wait =>
            if rst='0' then
                xi_yi_sel <= '1';      ena_xy <= '1';
                next_state <= S_start;
            end if;
        -- Calculate
        when S_start =>
            if alu_ne='1' then
                ena_xy <= '1';
                next_state <= S_start;
            else
                ena_r <= '1';      set_rdy <= '1';
                next_state <= S_ready;
            end if;
        -- Ready
        when S_ready =>
            ena_r <= '1';      set_rdy <= '1';
            next_state <= S_wait;
        end case;
    end process;
```

```
-- Subtractor (x-y) / comparator (x<y)
alu_o1 <= x - y;
sub_y_x <= '1' when alu_o1(alu_o1'high)='1' else '0';

-- Subtractor (y-x)
alu_o2 <= y - x;

-- Comparator (y/=x)
alu_ne <= '1' when x /= y else '0';

-- Multiplexers
x_i <= xi when xi_yi_sel='1' else alu_o1;
y_i <= yi when xi_yi_sel='1' else alu_o2;
ena_x <= '1' when (sub_y_x='0' and ena_xy='1') or
    xi_yi_sel='1' else '0';
ena_y <= '1' when (sub_y_x='1' and ena_xy='1') or
    xi_yi_sel='1' else '0';

-- Registers
process begin
    wait on clk until clk='1';
    state <= next_state;
    if ena_x='1' then      x <= x_i;      end if;
    if ena_y='1' then      y <= y_i;      end if;
    if ena_r='1' then      xo <= x;      end if;
    rdy <= set_rdy;
end process;
```


GCD example – synthesis results

Technology	FPGA				ASIC			
Constraint ¹⁾	50 MHz		100 MHz		50 MHz		25 MHz	
	[SLC]	[ns]	[SLC]	[ns]	[e.g.]	[ns]	[e.g.]	[ns]
<i>gcd-bhv²⁾</i>	93	17.3	-	-	1141	20.0	-	-
gcd-bhvc	-	-	-	-	961	20.0	977	31.1
gcd-bfsm	108	9.9	108	9.4	911	19.4	984	30.8
gcd-rtl1	50	10.8	50	9.7	986	19.8	883	32.4
gcd-rtl2	48	10.8	48	10.0	931	19.9	882	32.3
gcd-rtl3	58	17.0	58	14.6	1134	20.0	928	40.0
gcd-rtl4	78	12.6	78	9.0	976	19.9	928	29.0
gcd-rtl5	58	8.0	58	7.6	915	20.0	932	26.9


¹⁾ Clock period was the only constraint

²⁾ gcd-bhv was synthesized using the help of prototype HLS tool xTractor

GCD example – why such differences?

 

GCD example – why such differences?

 


gcd-rtl1

1 ALU, 3 rg, 6 st
3 cycles/iteration
50 SLC / 10.8 ns

gcd-rtl2

 
1 ALU, 3 rg, 5 st
2 cycles/iteration
48 SLC / 10.8 ns



gcd-rtl3

1 –, 1 <, 3rg, 3st
1 cycle/iteration
58 SLC / 17.0 ns

GCD example – why such differences?

 


gcd-rtl4

2 –, 3 rg, 3 st

1 cycle/iteration

78 SLC / 12.6 ns

GCD example – why such differences?

 

gcd-rtl5

2 –, 1 /=, 3 rg, 3 st

1 cycle/iteration

58 SLC / 8.0 ns